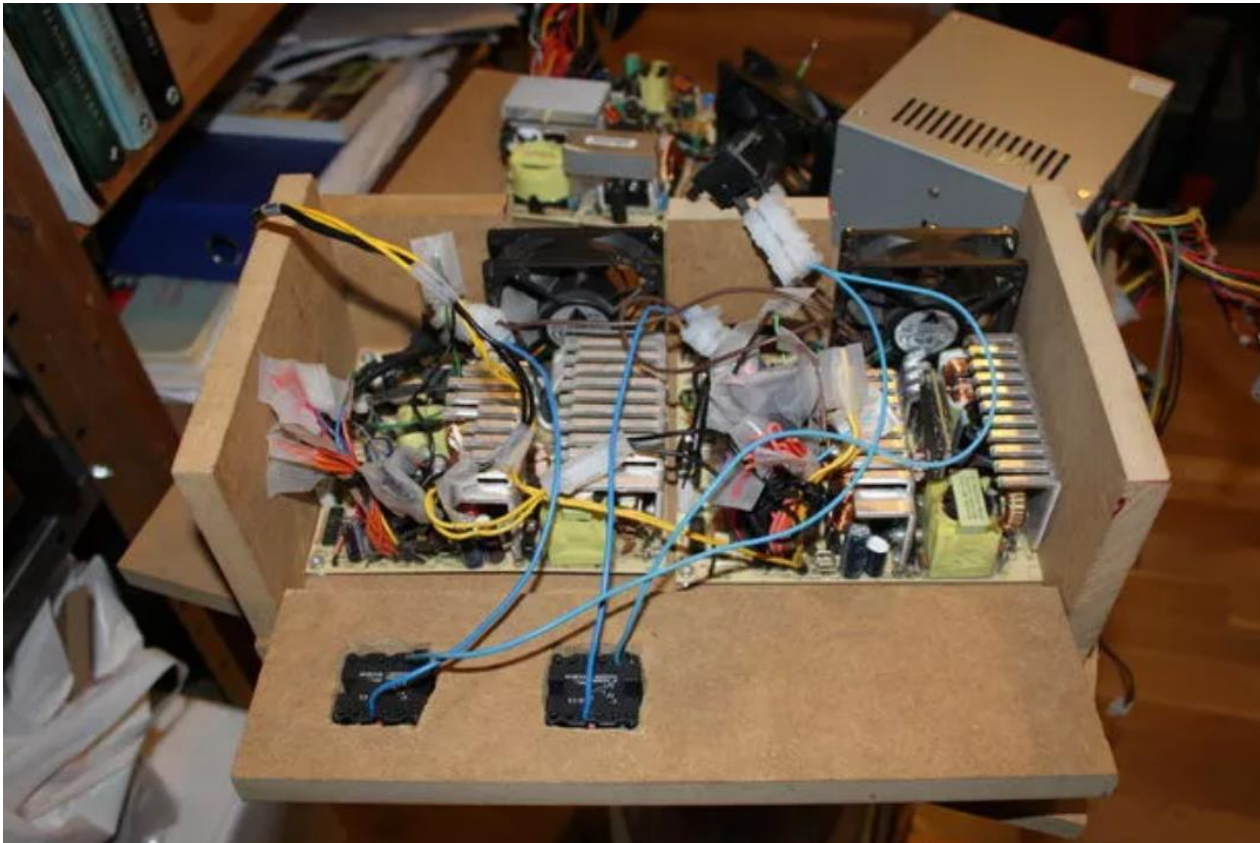


# Power Supplies 101

## DC-DC Converters

10-Feb-2018



# Tonight's Agenda

---

- Quick primer on circuit components and basic calculations
- Examples of unregulated linear supplies
- How regulated linear supplies work
- How switching supplies work
- Some notes on capacitors
- Cover related issues that you're likely to encounter

# Quick circuit component primer

---

Wire – carries electrical current like a pipe carries water



Voltage – like the pressure of water in a pipe or air in a tire

Current – the amount of water flowing through a specific cross section of the pipe

Resistor – resists the flow of current, like a constriction in a pipe

Capacitor – stores energy like a hydraulic accumulator

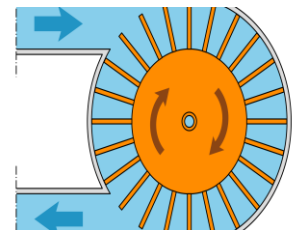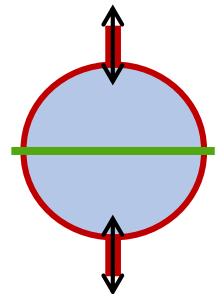Inductor – stores energy like a heavy paddlewheel



# Power supply math primer

---

**Power** (P, watts, W) = **Voltage** (volts, V) x **Current** (amps, A)

$$\text{Power} = 5\text{V} \times 2\text{A} = 10\text{W}$$

Ohm's Law:

$$V = I \times R$$

$$\text{or: } I = V / R$$

$$\text{or: } R = V / I$$

V = voltage, volts, V

I = current, amps, A

R = resistance, Ohms,  $\Omega$

Units:

$$1000 \text{ milli} = 1.0$$

$$400\text{mA} = 0.4\text{A}$$

$$10\text{mV} = 0.01\text{V}$$


$$2000 \text{ m}\Omega = 2\Omega$$

# Examples

What is the power rating of a 5V, 2A power supply?

Power = Voltage x Current


$$5V \times 2A = 10W$$

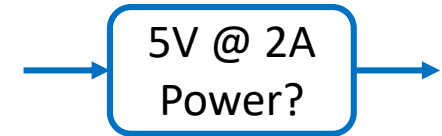

How much current does a 60W light bulb draw?

Current = Power / Voltage

$$60W / 120V = 0.5A$$

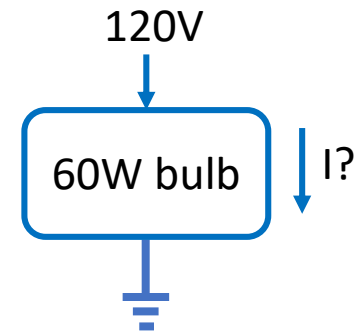

A 100Ω resistor is connected between a 12V supply and ground, how much current does it draw?


$$I = V / R$$

$$= 12V / 100\Omega = 0.12A = 120mA$$


How much power does it dissipate?

Power = Voltage x Current

$$= 12V \times 120mA = 1.44W$$

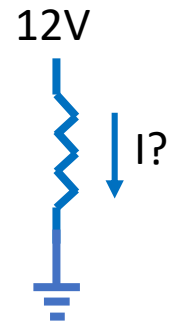

# Simple Voltage Converter/Supply

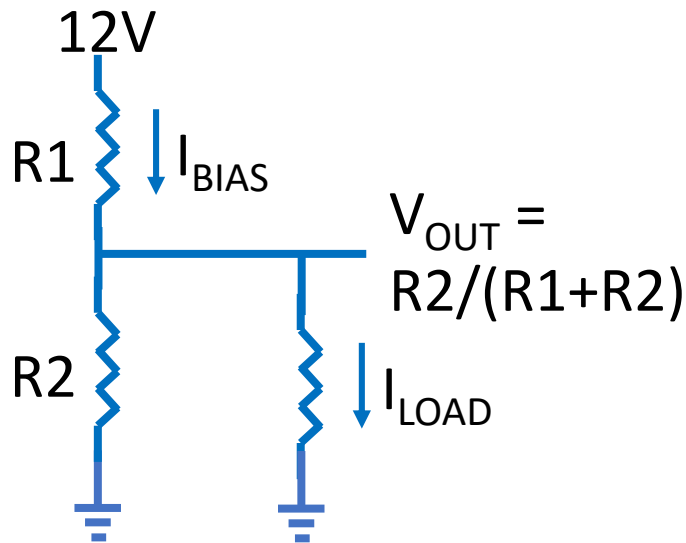

Example: 12V to 5V, 10mA load

$R1 = 70\Omega$

$R2 = 50\Omega$

$I_{BIAS} = 100\text{mA}$

$V_{OUT, NO\ LOAD} = 5.0\text{V}$

$V_{OUT, 10\text{mA}\ LOAD} = 4.7\text{V}$


Load regulation = 6%

Efficiency = 9.6%
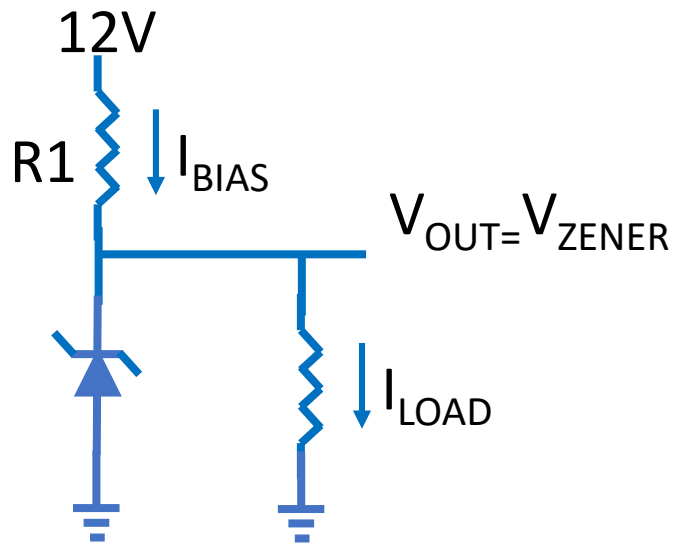
# Zener Voltage Reference/Supply



---

Decent load regulation ~2-5%  
Efficiency ~30%



# More unregulated supplies


---

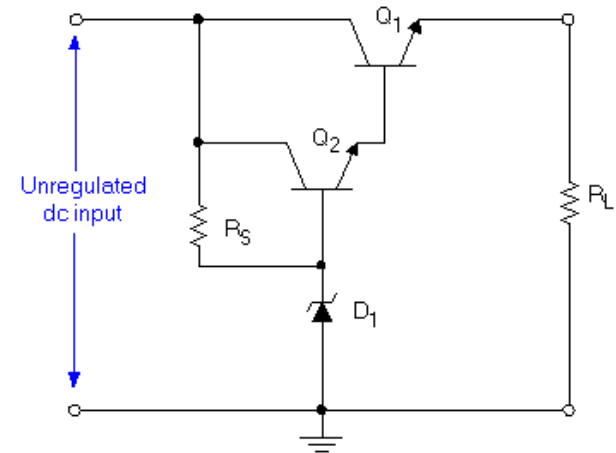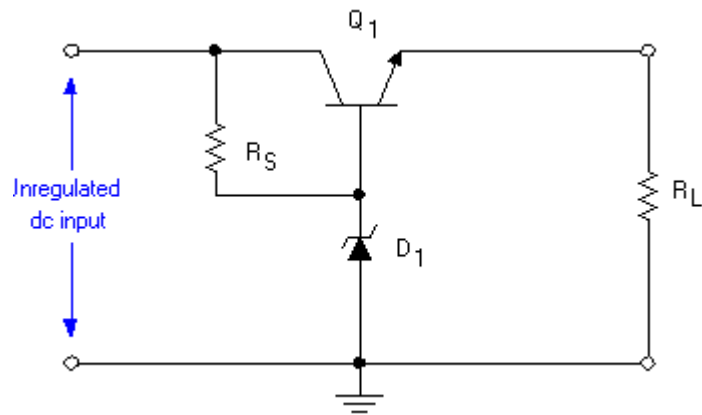



# How does a linear regulator work?

---

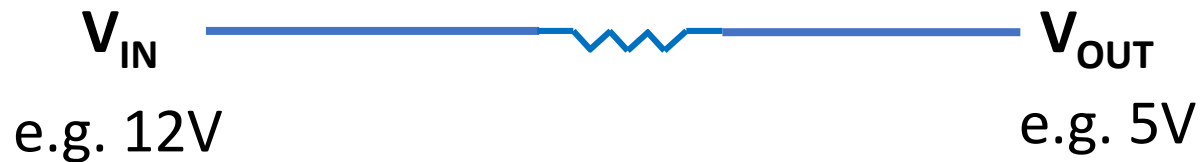

Resistor converts extra voltage into heat

$V_{OUT}$  will be less than  $V_{IN}$


Efficiency =  $V_{OUT}/V_{IN}$

$5V / 12V = 42\%$

$3.3V / 5V = 66\%$


# Add a control loop

---

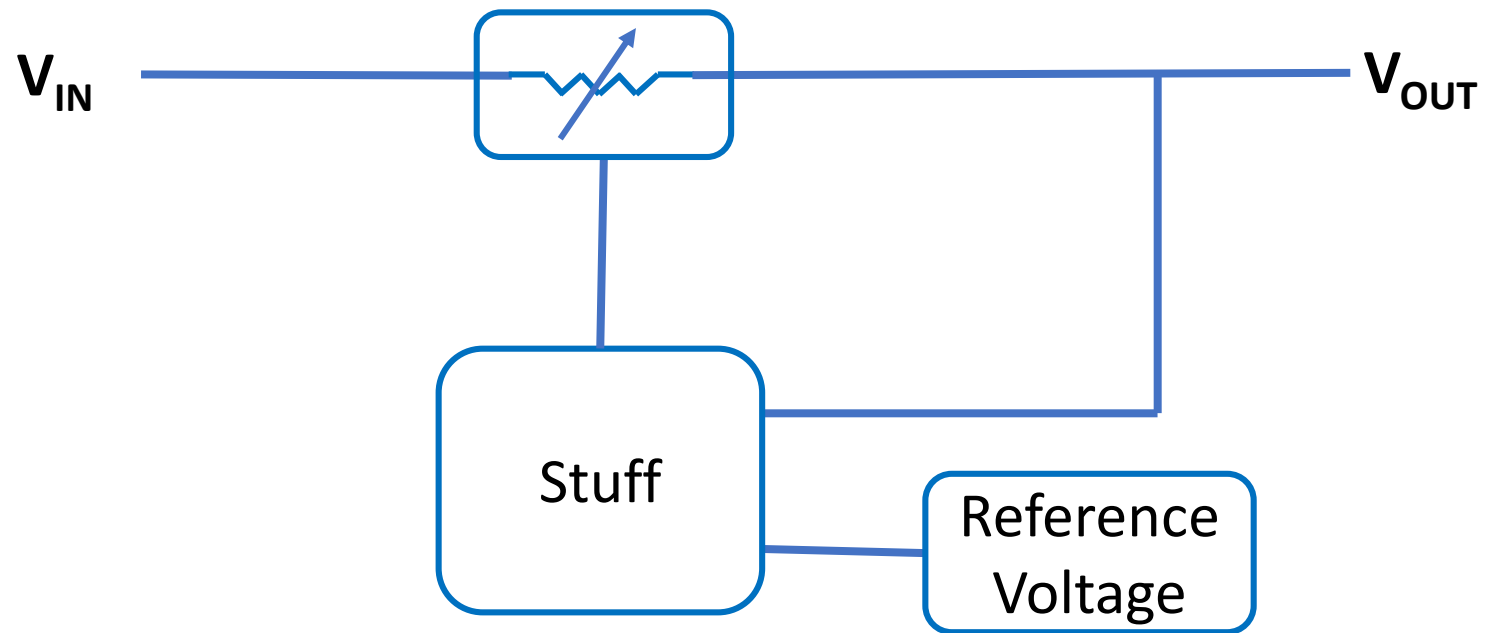


# Make it more real

---


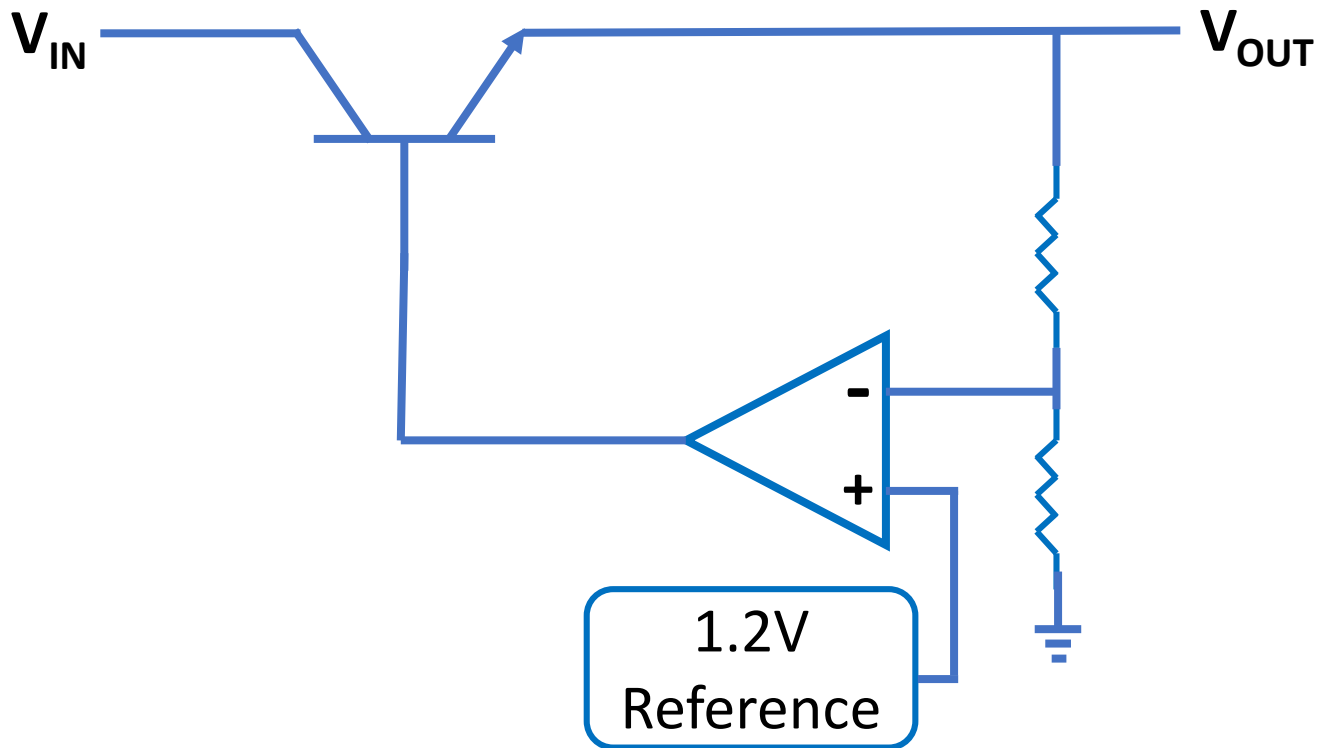


# Linear regulator in action

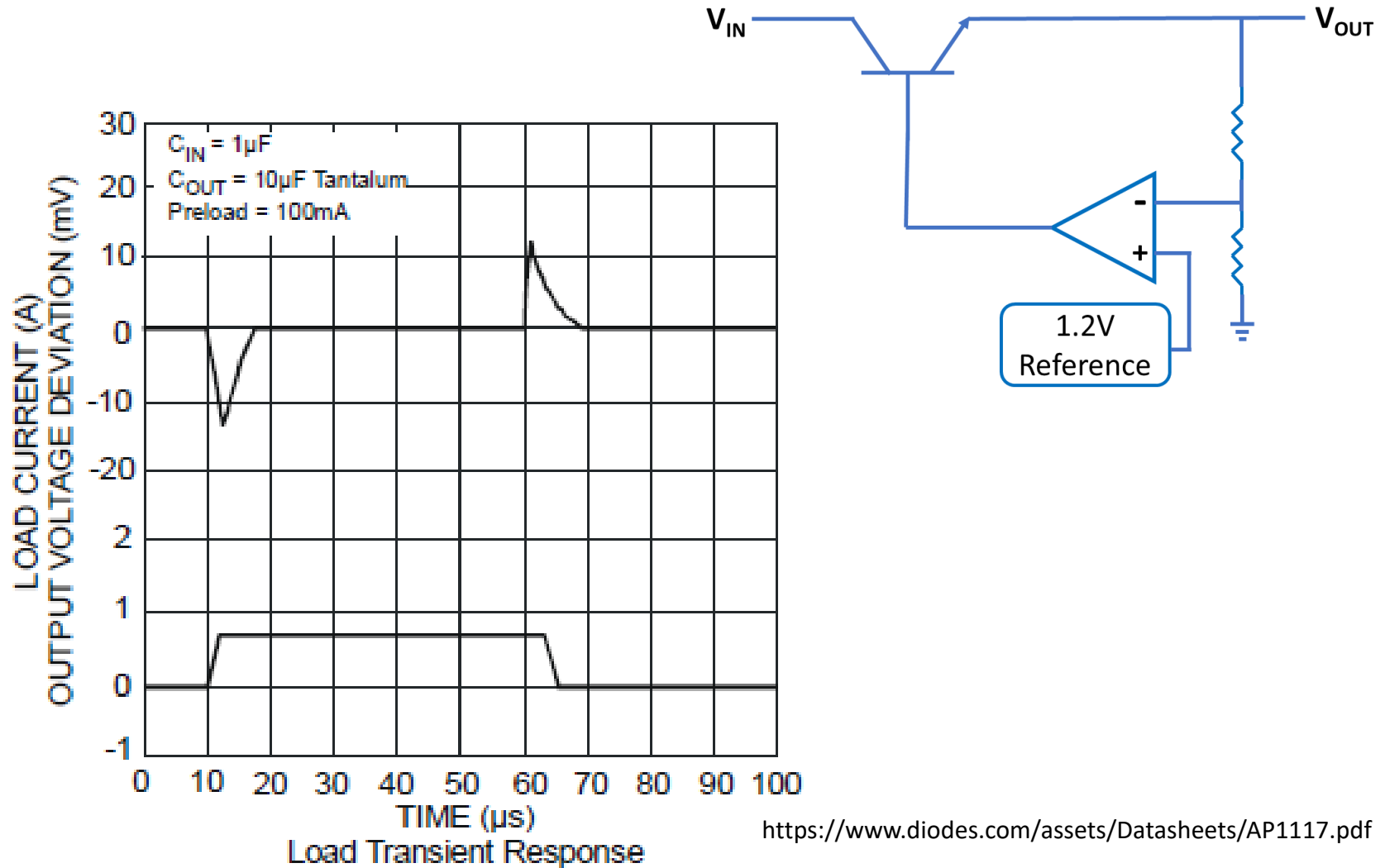

<https://www.diodes.com/assets/Datasheets/AP1117.pdf>

# Power Supply Rejection

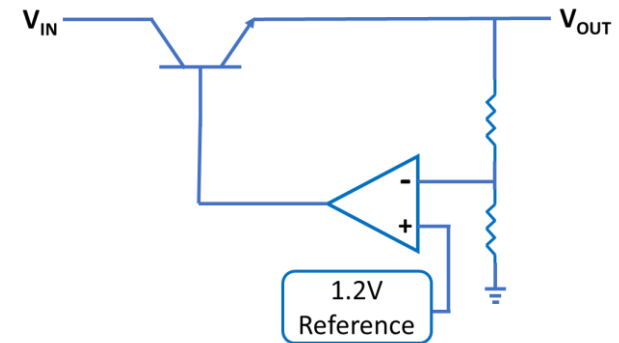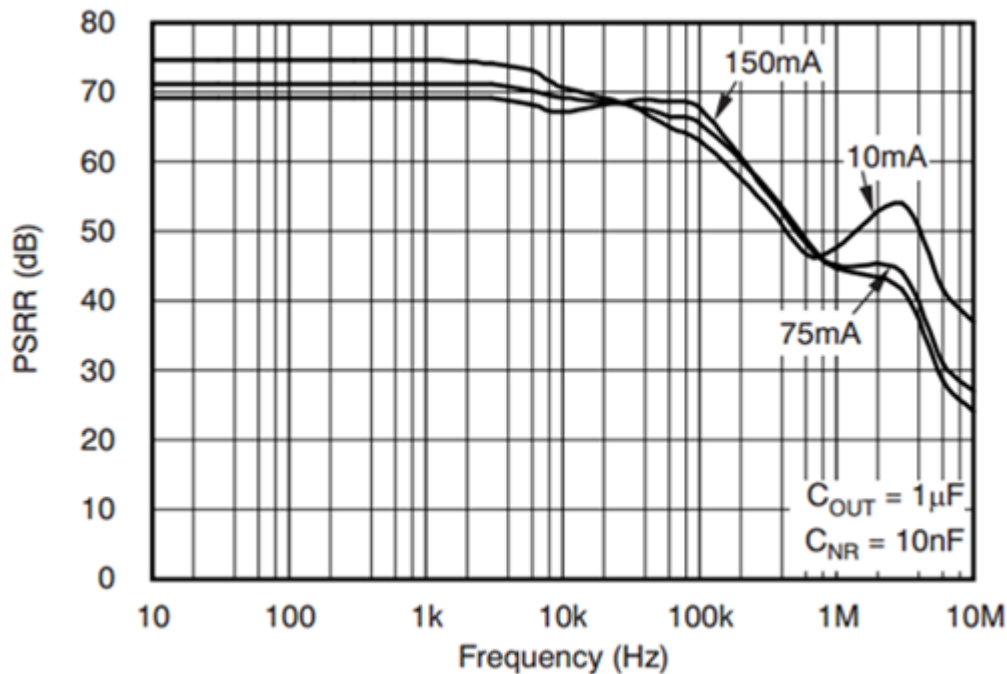

$$PSRR (dB) = 20 \log \frac{V_{ripple (in)}}{V_{ripple (out)}}$$

$$20dB = 1/10$$

$$40dB = 1/100$$


$$60dB = 1/1000$$

$$70dB = 1/3162 \rightarrow V_{in} \text{ ripple of } 1V \text{ results in } 0.3mV \text{ at } V_{out}$$

# Typical Hardware



\$1.60

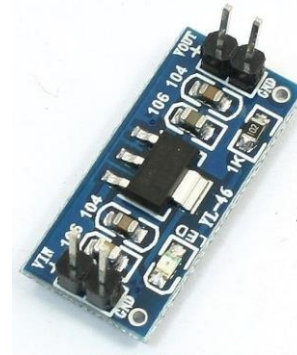

\$0.99




\$1.50



\$1.70

@mikew

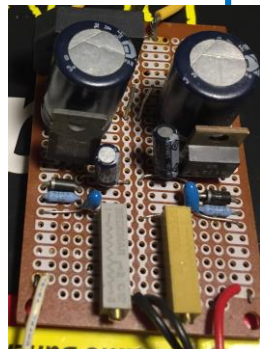

\$0.50




\$0.50-  
\$1.00



\$0.05



\$1.00

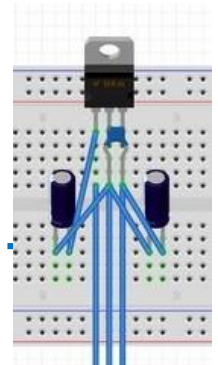

# Workhorse linear regulators ICs

---

	$V_{IN}$ Max	$V_{OUT}$ Range	$V_{DO}$ Dropout	Peak $I_{OUT}$
LM317	$V_{OUT} + 40V$	1.25V to 37V	3V	1.5A
LM1117	15V	1.25V to 13.8V	1.3V	1A
LM7812	35V	12.0V	2V	2.2A
LM7805	35V	5.0V	2V	2.4A
LM7833	36V	3.3V	2V	1.8A

These regulators are available from multiple manufacturers. Check the data sheet for the specific part you're looking at.


# DC-DC Switching Supplies

---

- Buck converter:  $V_{OUT} < V_{IN}$ 
  - Very plentiful selection of products
- Boost converter:  $V_{OUT} > V_{IN}$ 
  - Inductor-less Charge Pump, typically 10's of mA
  - Inductor based boost converter, any current
- Buck/Boost converter:  $V_{OUT} \geq$  or  $\leq V_{IN}$ 
  - Useful in battery powered circuits where the battery voltage starts above the required voltage but ends below it
    - e.g. LED flashlight




# How does a buck regulator work?

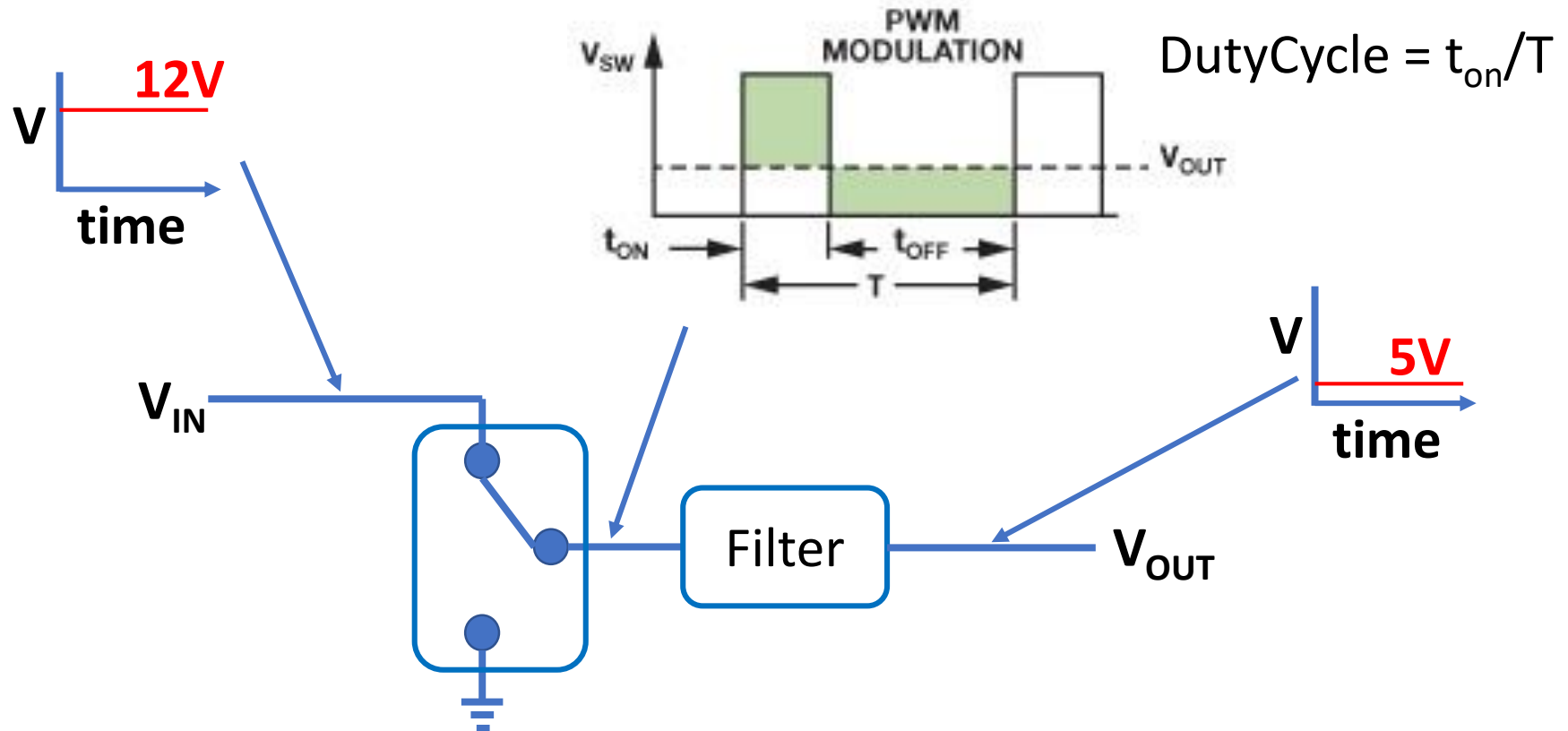


$$V_{OUT} = V_{IN} \times \text{DutyCycle}$$

# Add a control loop (regulation)

---

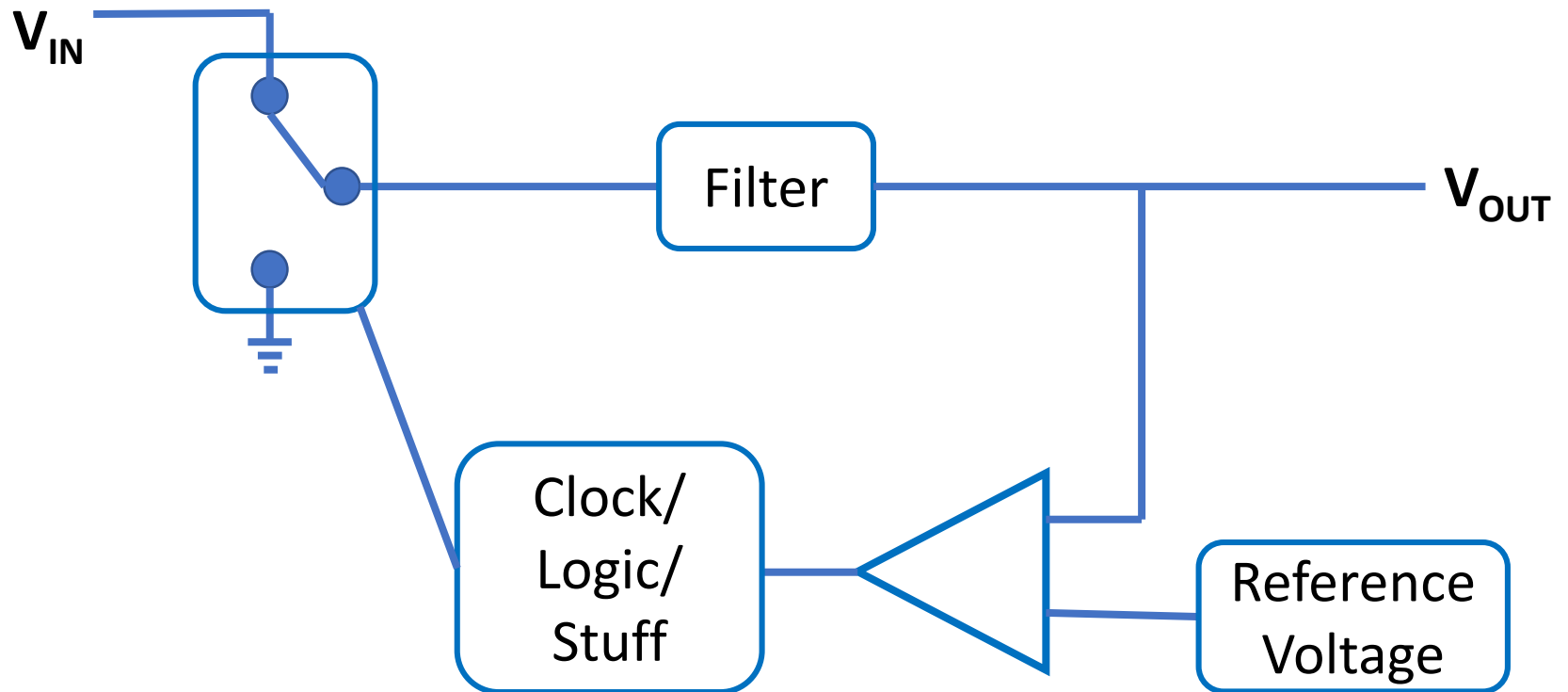


# Make it more real

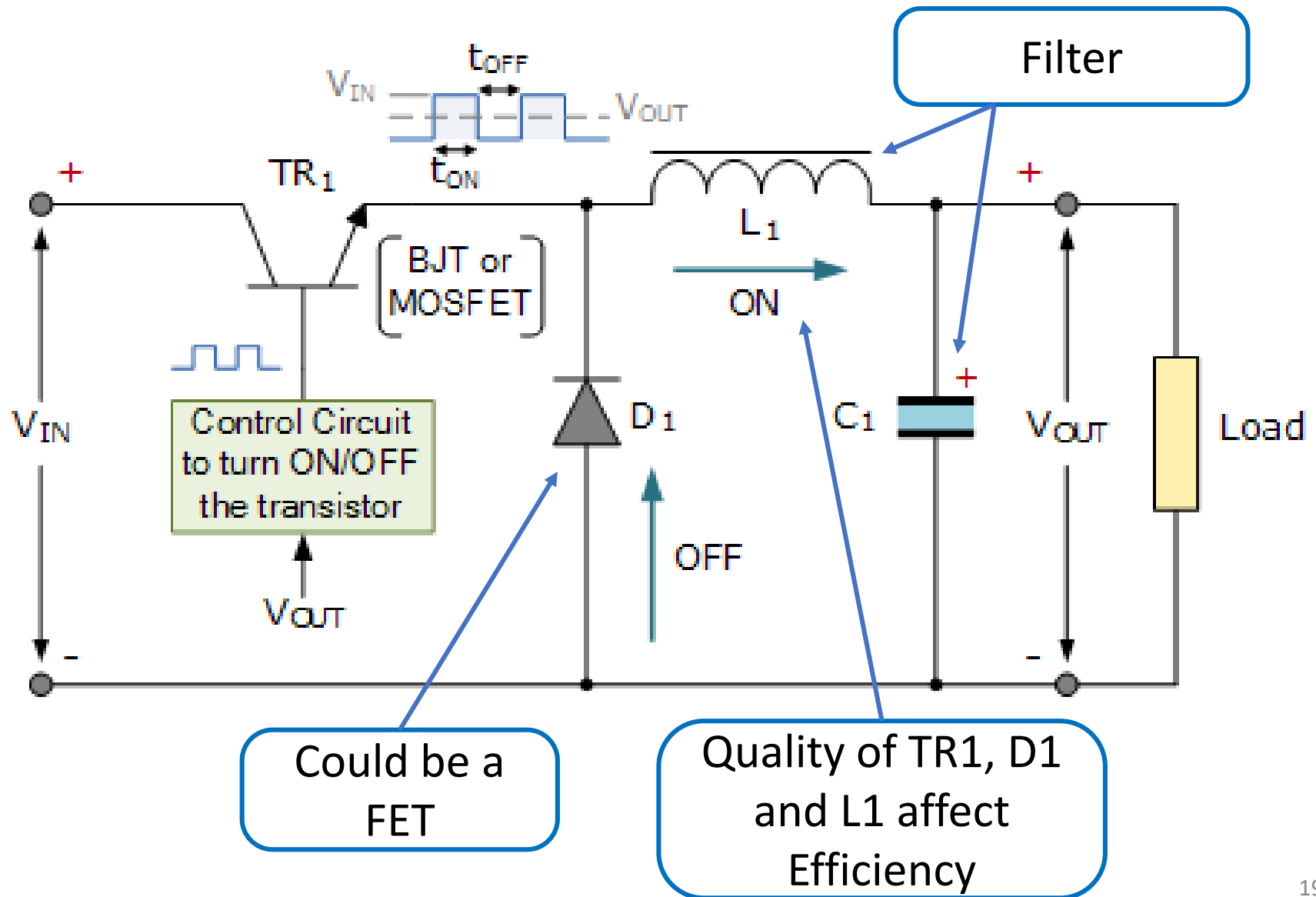


# Buck, Boost, Buck/Boost


---

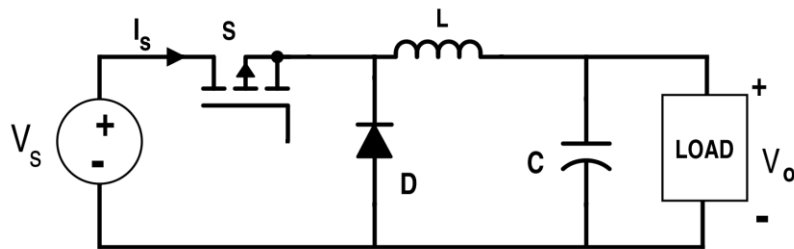

Buck Converter

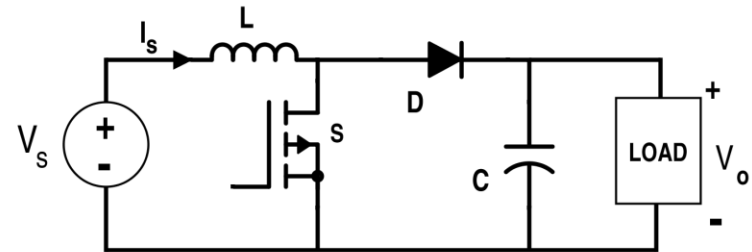


Boost Converter

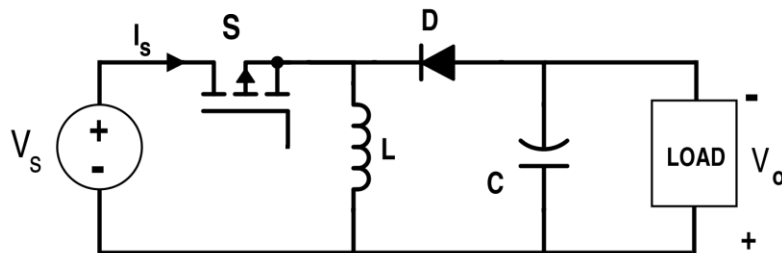


Buck-Boost Converter

Slight modifications in the schematic, operation is quite different from the earlier buck explanation

# Flyback Converter

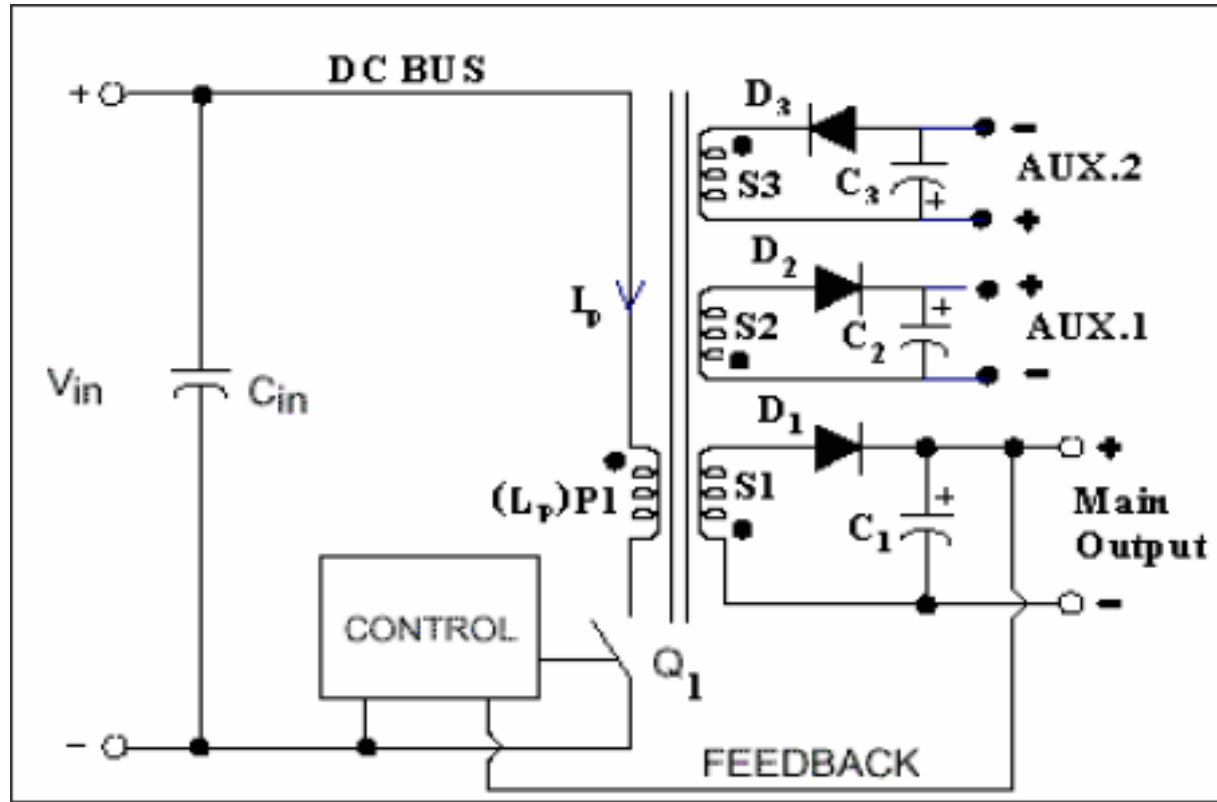

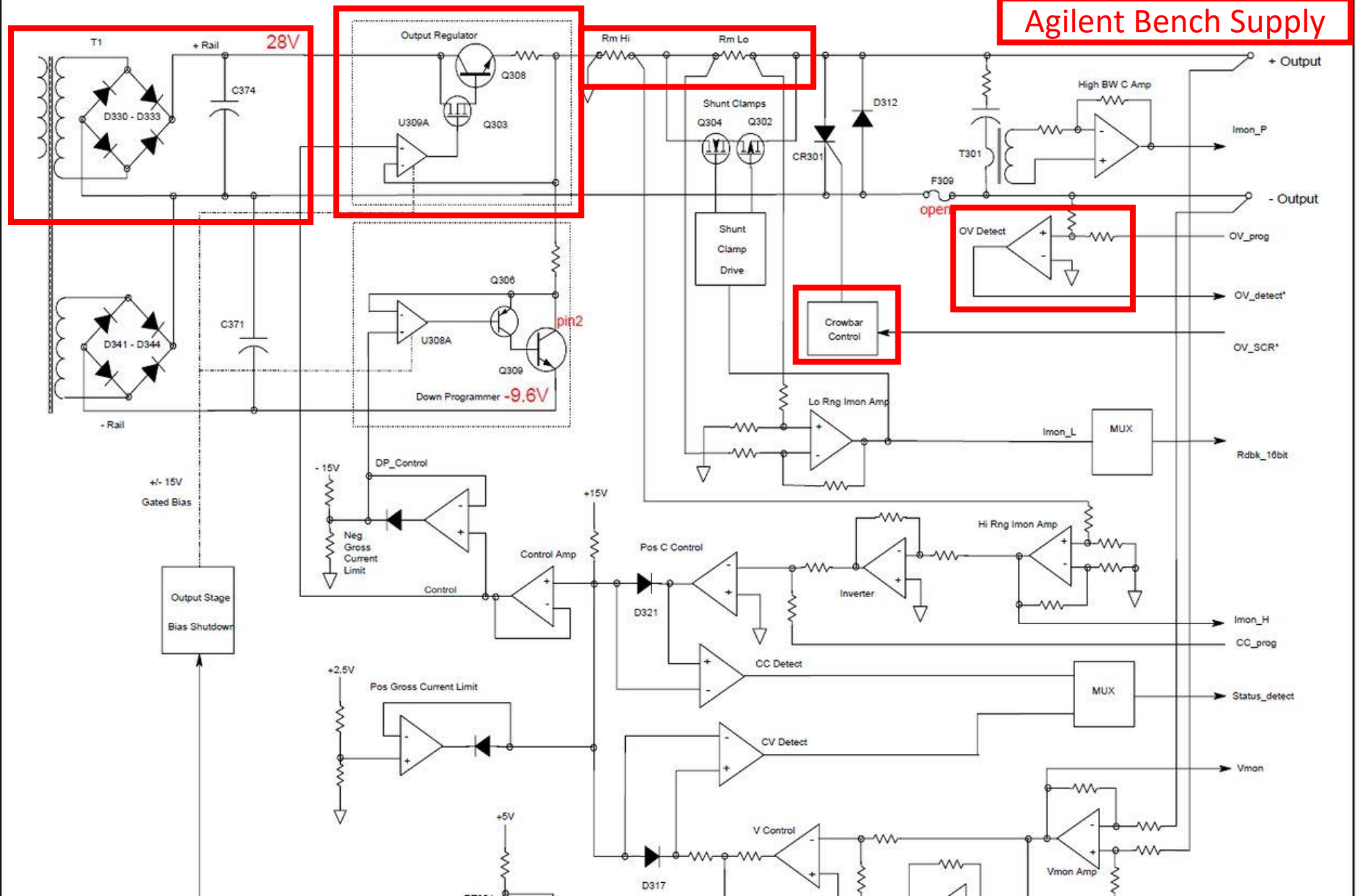- Transformer is used in place of an inductor
- One or many outputs
- Feedback loop (regulation) based on one output or some weighted average of multiple outputs



# DC-DC linear vs switching supplies

---

	Pros/Cons
Switching (Regulated)	<ul style="list-style-type: none"><li>• Easy to buy/use</li><li>• Typically preferred over ~1A of output current</li><li>• Typically overly-complicated for low power circuits (100's of mW)</li></ul>
Linear Regulators	<ul style="list-style-type: none"><li>• Easy to build, easy to buy</li><li>• Easy to integrate onto proto boards</li><li>• Becomes more difficult as <math>P_{DISS}</math> increases beyond a few watts</li><li>• Off-the-shelf options above 1A are limited</li></ul>

# About Capacitors

## Capacitance value

## Physical size

## Lead configuration (axial, radial)

## Voltage rating

# Polarized

## Equivalent Series Resistance (ESR)

## Equivalent Series Inductance (ESL)

## Appropriate frequency range






# Electrolytic Capacitors

## Electrolytic (Aluminum)

- Primarily used for bulk capacitance, up to 10,000's of  $\mu\text{F}$
- Lots of disadvantages:
  - Polarized (typically)
  - Need to check voltage rating, derate 20%
  - Physically large
  - High equivalent series resistance
  - High equivalent series inductance
  - Doesn't look like a capacitor much above 100k
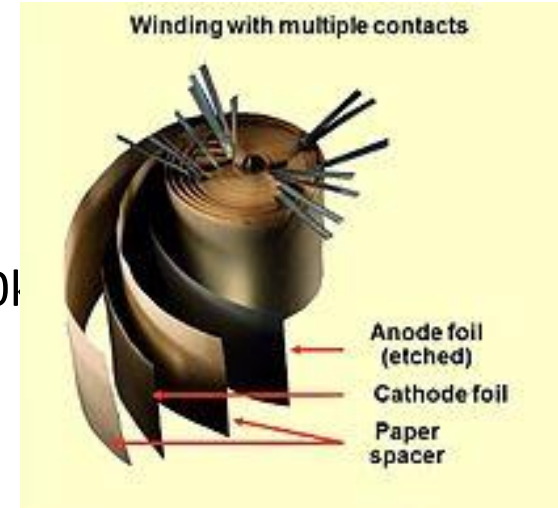
## Electrolytic (solid tantalum)

- Similar to aluminum electrolytic except:
  - Smaller
  - Better (lower) ESR, ESL
  - Frequency response to  $\sim 500\text{kHz}$ , maybe  $1\text{MHz}$
- Derate voltage by 50%
- Overvoltage or wrong polarity can cause a fire




# Ceramic Capacitors

---
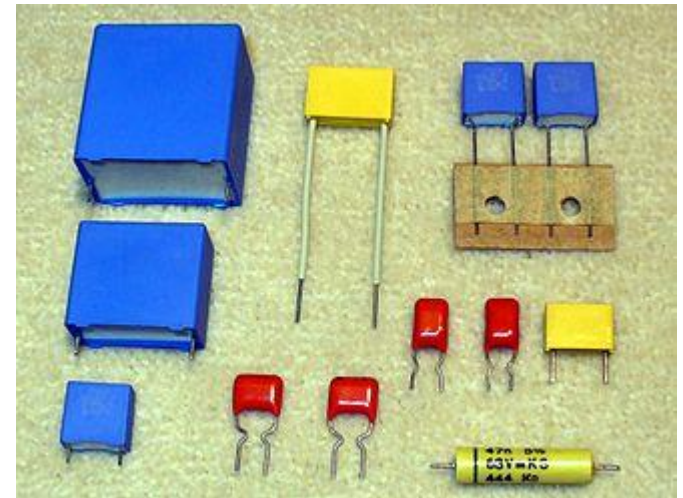
## Film




- Often thought of as an alternative to ceramics for audio
- Benefits:
  - Linear response
  - No microphonics
  - Slightly higher capacitance than ceramics
  - Good heat and vibration tolerance



# Film Capacitors
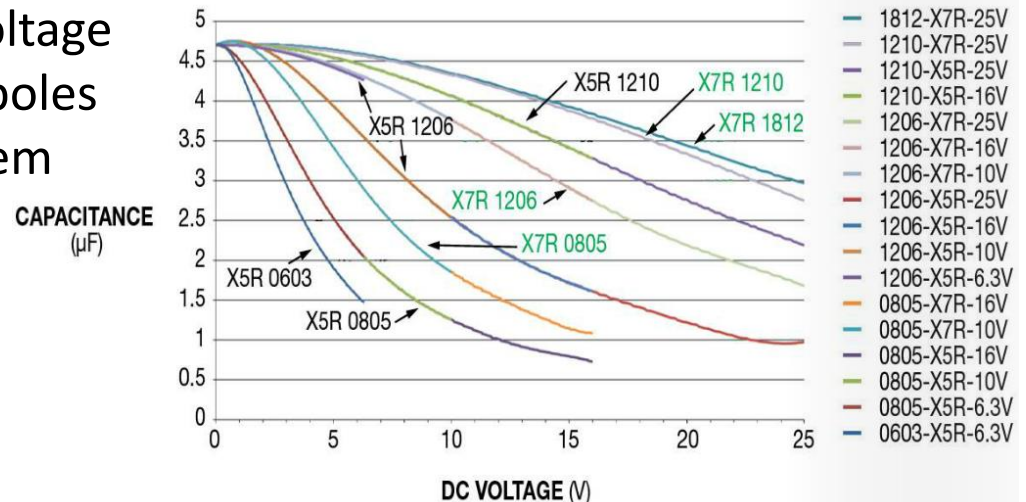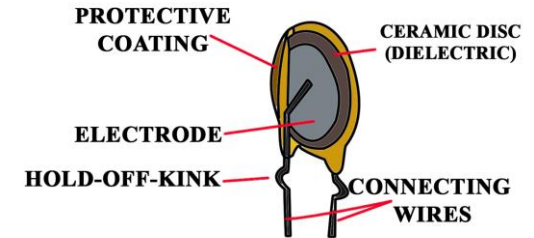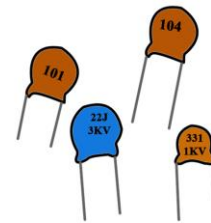
## Ceramic

- Looks the most like an ideal capacitor
- Low capacitance value (1 $\mu$ F is a large value)
- Not polarized
- High voltage ratings (typ 100V)
- Very low equivalent series resistance
- Very low equivalent series inductance
- Frequency range, 10's or 100's of MHz
- Capacitance is highly voltage dependent
  - ~80% lower at rated voltage
  - Due to ferroelectric dipoles
  - Nonlinearity makes them less desirable in hifi audio
- Piezoelectric



# Bypass caps, rules of thumb

---

*Where to put them*

- *Where power enters a board*
- *Near the  $V_{CC}$  pin of each IC*
- *Input and output of linear regulator ICs*

*Values and types:*

- *0.1uF ceramic is the workhorse for typical digital/analog*
- *Maybe add a 10μF or so where power enters the board*
- *AC rectifier circuits tend to use 1000's of uF*


*Larger bypass caps are needed with:*

- *Larger current swings*
- *Lower frequency*
- *Power supply feed lengths get longer*

*Star feed is better than daisy chain feed*

*Typical low current circuits -> 0.1uF ceramic cap every several inches*

# Measuring Current Draw of a Circuit

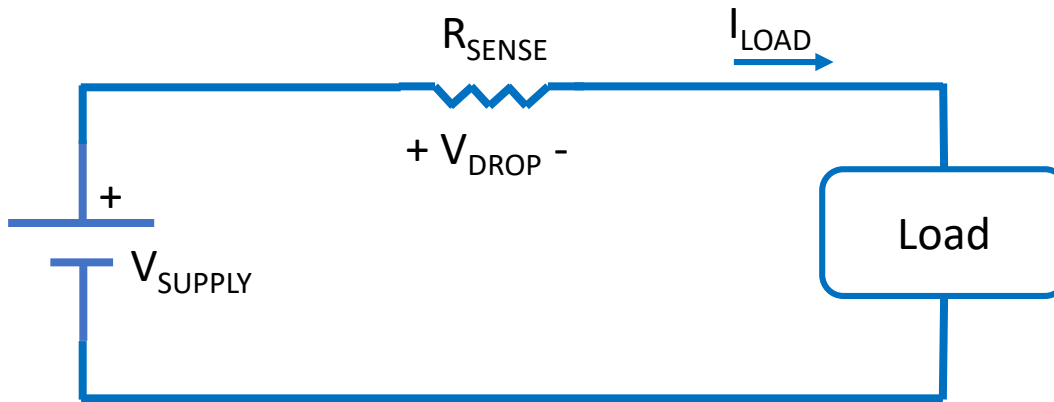

$$I_{LOAD} = V_{DROP} / R_{SENSE}$$

$V_{DROP}$  should be large enough for a multimeter to measure it accurately but not so large that it affects the circuit being powered

- $0.1V < V_{DROP} < V_{SUPPLY} / 10$

Check that resistor is rated for dissipated power

- If it's too hot to touch, measure fast
- $P_{DISS} = V_{DROP} \times I_{LOAD}$



# Determining if you'll run too hot

---


Build it, feel the device, if it's too hot to touch for 0.5 seconds, add a heat sink, choose a larger regulator or do something else about it



Or, rules of thumb->

# Thermal Rules of thumb based on packaging

---

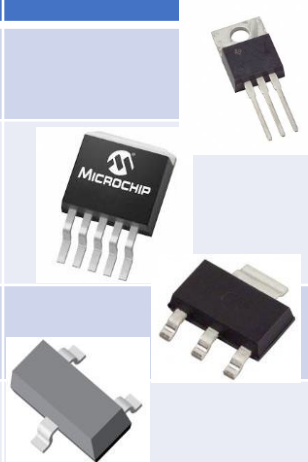Package	$R_{JA}$	Max Power No Heat Sink	Accommodates Heat Sink?	Picture
TO-220	~20	~2-4W	Yes	
DDPAK	44	~1-1.5W	No	
SOT223	90	~0.5-0.7W	No	
SOT23	200	~0.25W	No	

Or, get your calculator out->

# Calculate thermal limit for TO-220

## absolute maximum ratings

Operating virtual junction temperature,  $T_J$  ... 150°C

40°C

PACKAGE	$\theta_{JA}$
POWER-FLEX (KTE)	23°C/W
TO-220 (KC/KCS)	19°C/W

- $P_{DISS,MAX} = (T_{J,MAX} - T_{AMBIENT,MAX}) / (R_{JA})$
- $P_{DISS,MAX} = (110) / (19) = 5.8W$
- You need some margin on this. 3-4W might be OK



# How much does a heat sink help?

PACKAGE	$\theta_{JC}$	$\theta_{JA}$
POWER-FLEX (KTE)	3°C/W	23°C/W
TO-220 (KC/KCS)	3°C/W	19°C/W



EV-T220-38E

Ohmite

Heat Sink Passive TO-220 Vertical Thru-Hole Aluminum 6063-T5 13°C/W

- $P_{DISS,MAX} = (T_{J,MAX} - T_{AMBIENT,MAX}) / (R_{JC} + R_{CA})$
- $P_{DISS,MAX} = (110) / (3+13) = 6.9W$  (compared to 5.8W bare)
- ~20% improvement, 4-5W

These numbers can be very rough:

- Air flow around part/heat sink
- Surface mount parts can be highly affected by PCB layout

## Rules of thumb:

- TO-220 is good for 2-4W of power w/o heat sink, can be improved to 4-5W easily, significantly more requires very large heat sinks and/or fan cooling
- SMT is good for 0.25W to 2.5W depending on part, package and PCB layout

# Appendix

---

# A Quick Battery Primer

## Important battery terms:

*Voltage, e.g. 1.5V*




*Voltage range, 0.9 to 1.5V*

*Capacity, e.g. 500mAh*

*Discharge rate, e.g. 10C*

*High current applications - Killswitch*

Proper schematic for a single cell

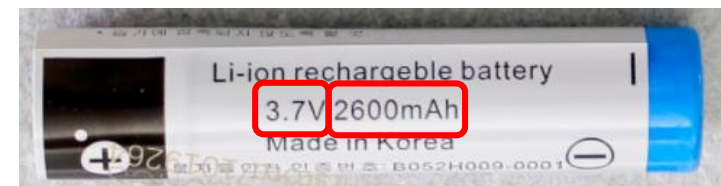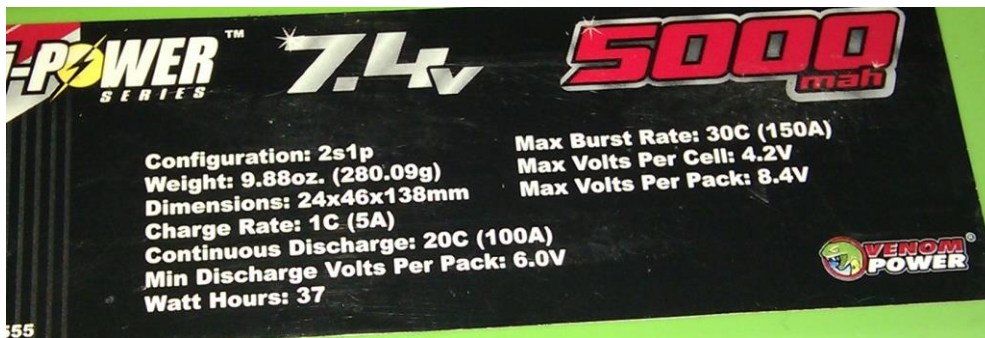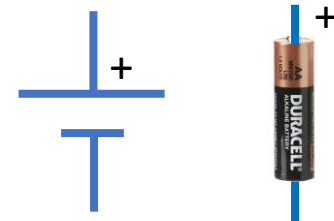

# Series vs Parallel Batteries


Batteries in series:

Multiply voltage, capacity stays the same


Batteries in parallel:

Multiply capacity, voltage stays the same

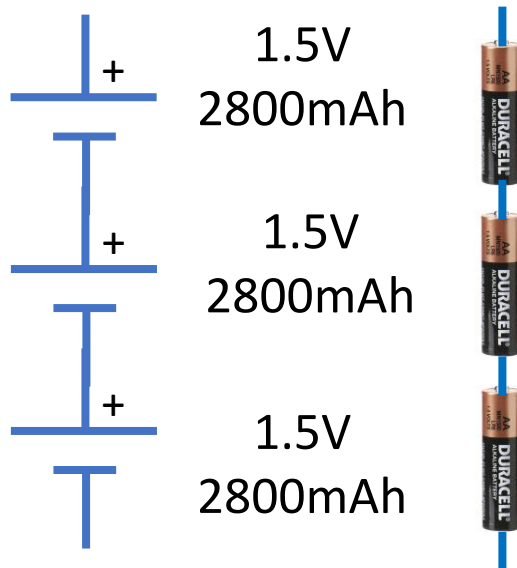**Series combination yields  
4.5V @ 2800mAh**



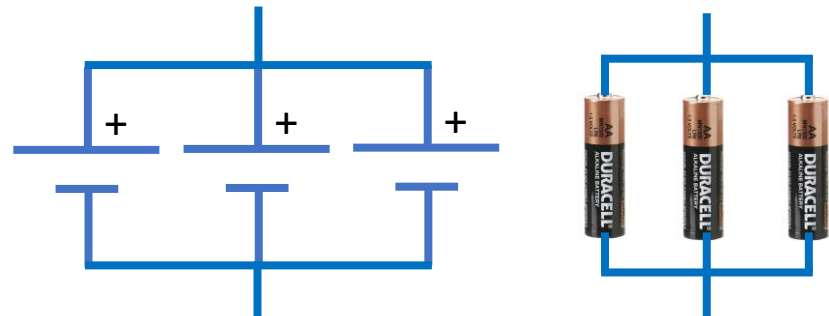
**Parallel combination yields  
1.5V @ 8400mAh**


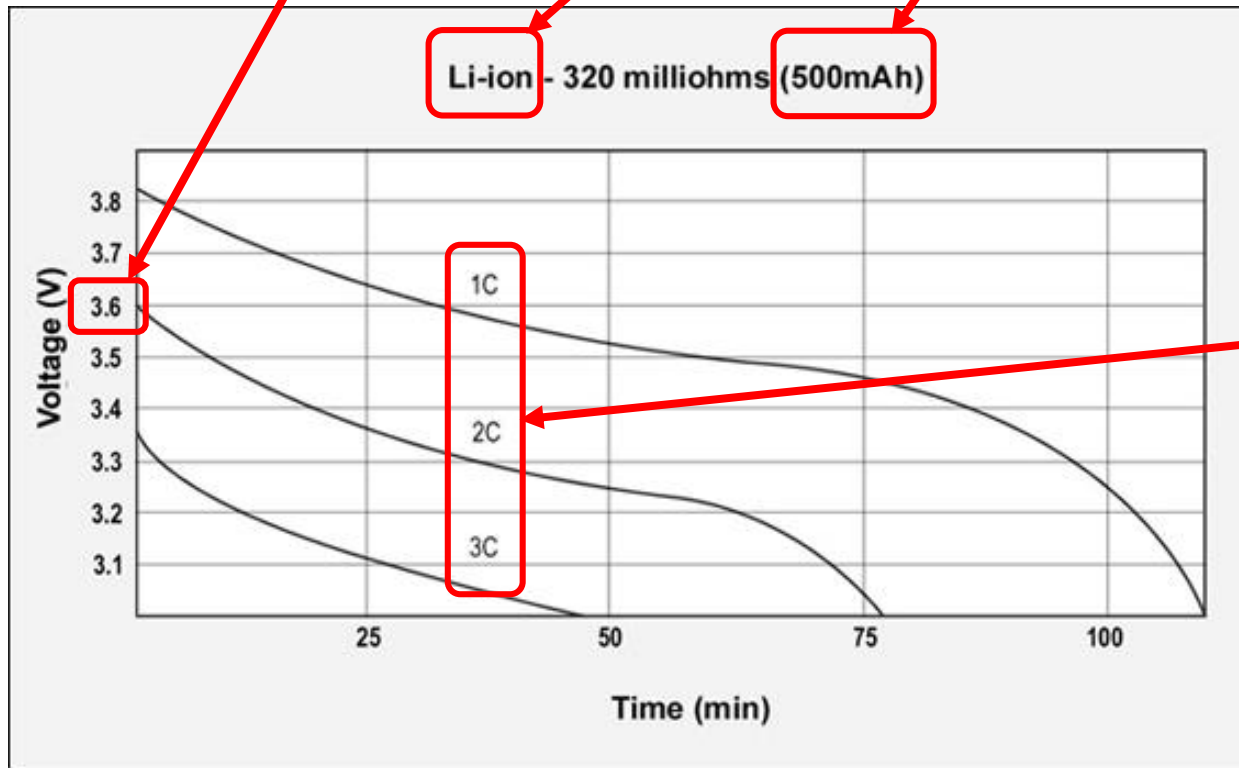
# Battery discharge curve

This is the primary challenge


Rated as "3.6V"      Chemistry      Capacity



## Discharge rates

- $1C = 500mA$
- $2C = 1000mA$
- $3C = 1500mA$

# Battery Chemistry Comparison

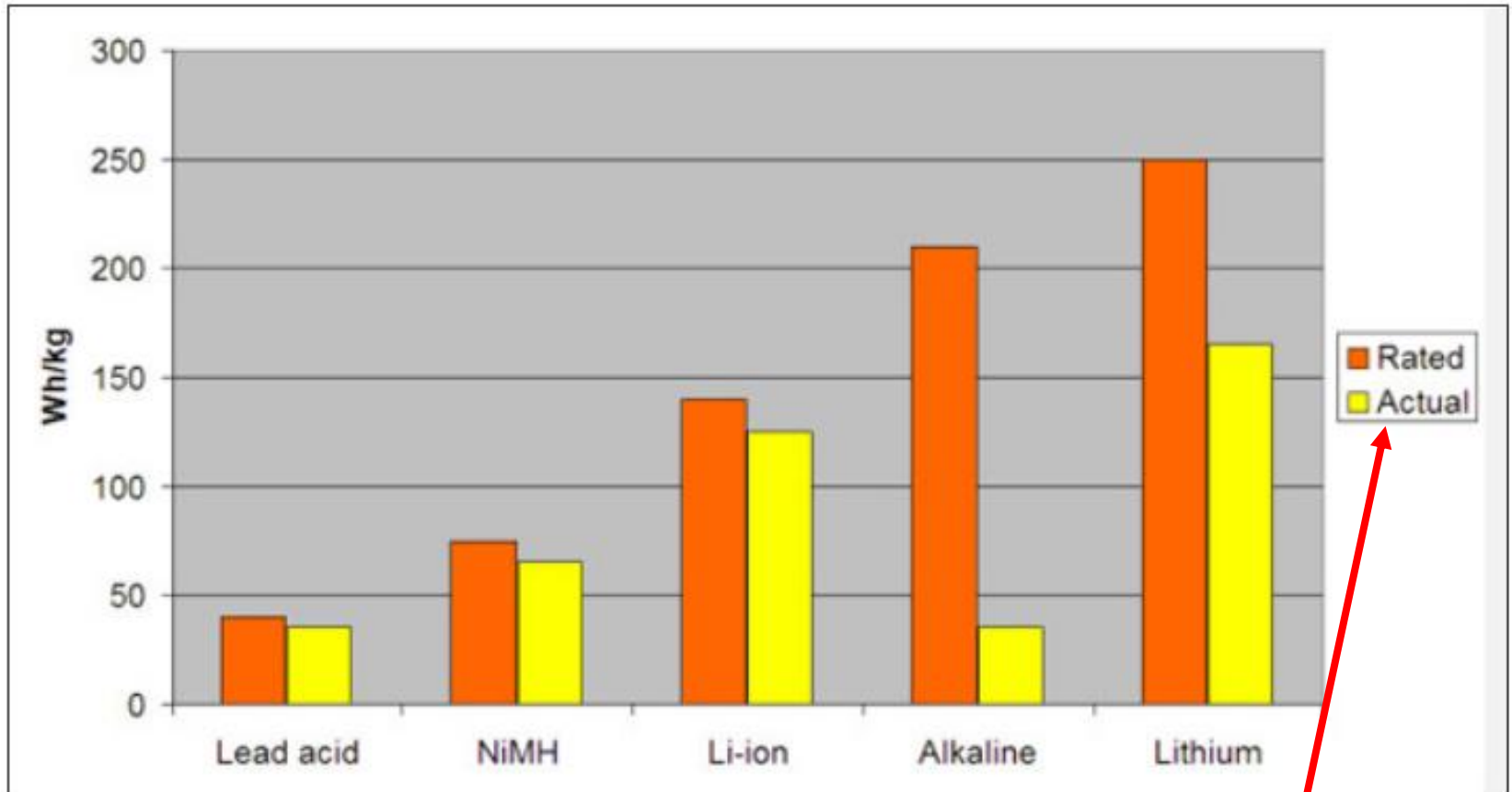

**Rated:** low discharge current  
**Actual:** 1C discharge current

# Battery internal resistance

Remember Ohm's law:

$$V = I \times R$$

Battery voltage depends on current

Might matter for higher current circuits

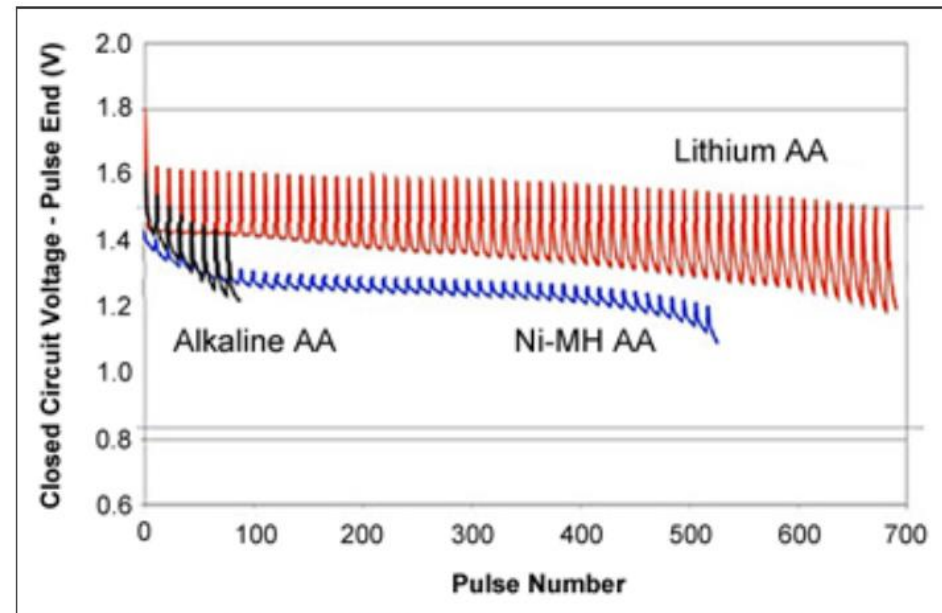
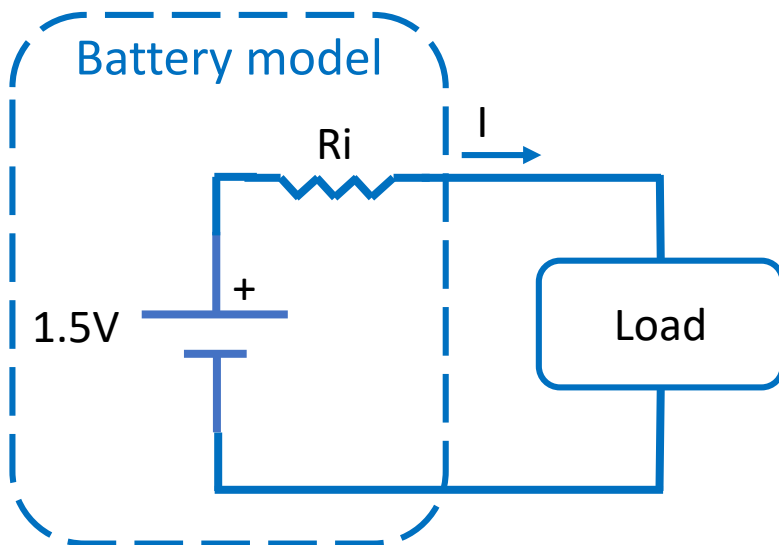


Figure 5: Number of shots a digital camera can take with alkaline NiMH and lithium.

# Powering off of Batteries

---

## Options:

- Operate directly off battery if circuit allows
- Stack batteries and regulate down to desired voltage
- Buck-boost regulator if battery voltage range straddles desired voltage
- Low dropout linear regulators (e.g. 0.2V vs 1.0V) can significantly improve battery life


Battery Configuration	Voltage Range
3 alkaline cells	2.7V to 4.5V
4 alkaline cells	3.6V to 6.0V
9v cell	4.8V to 9.0V
3 NiCd cells	3.3V to 4.2V
NiMH	Similar to alkaline
1 Li+ (Li ion) cell	2.8V to 4.2V




# Thermal Management

## First, a Fun Look Inside the LM7805


---

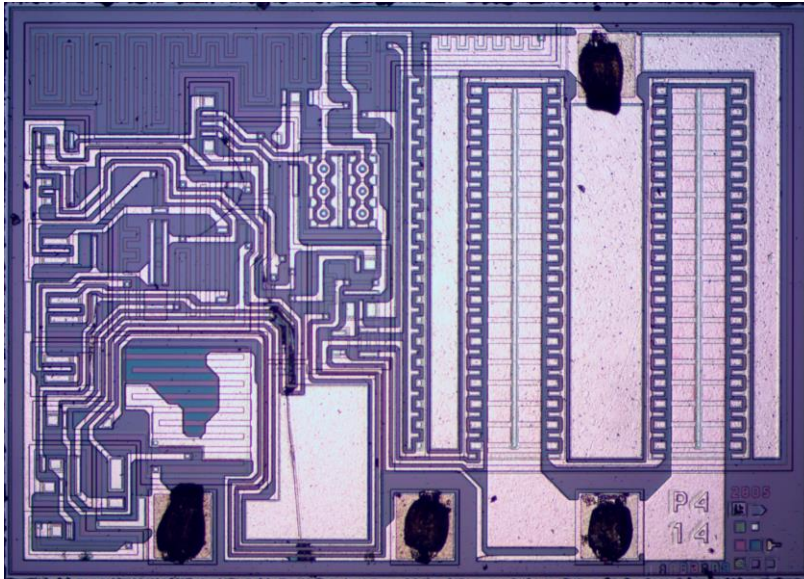

LM7805

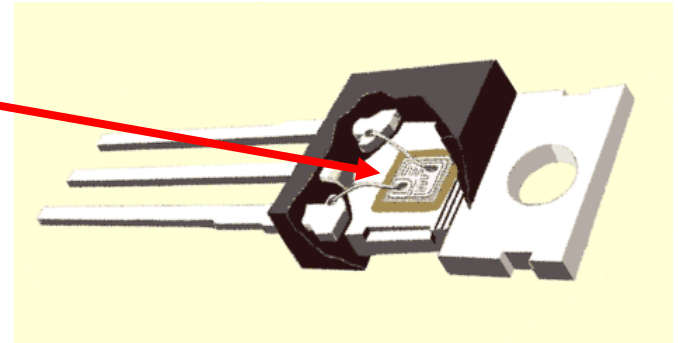


# LM7805 Die

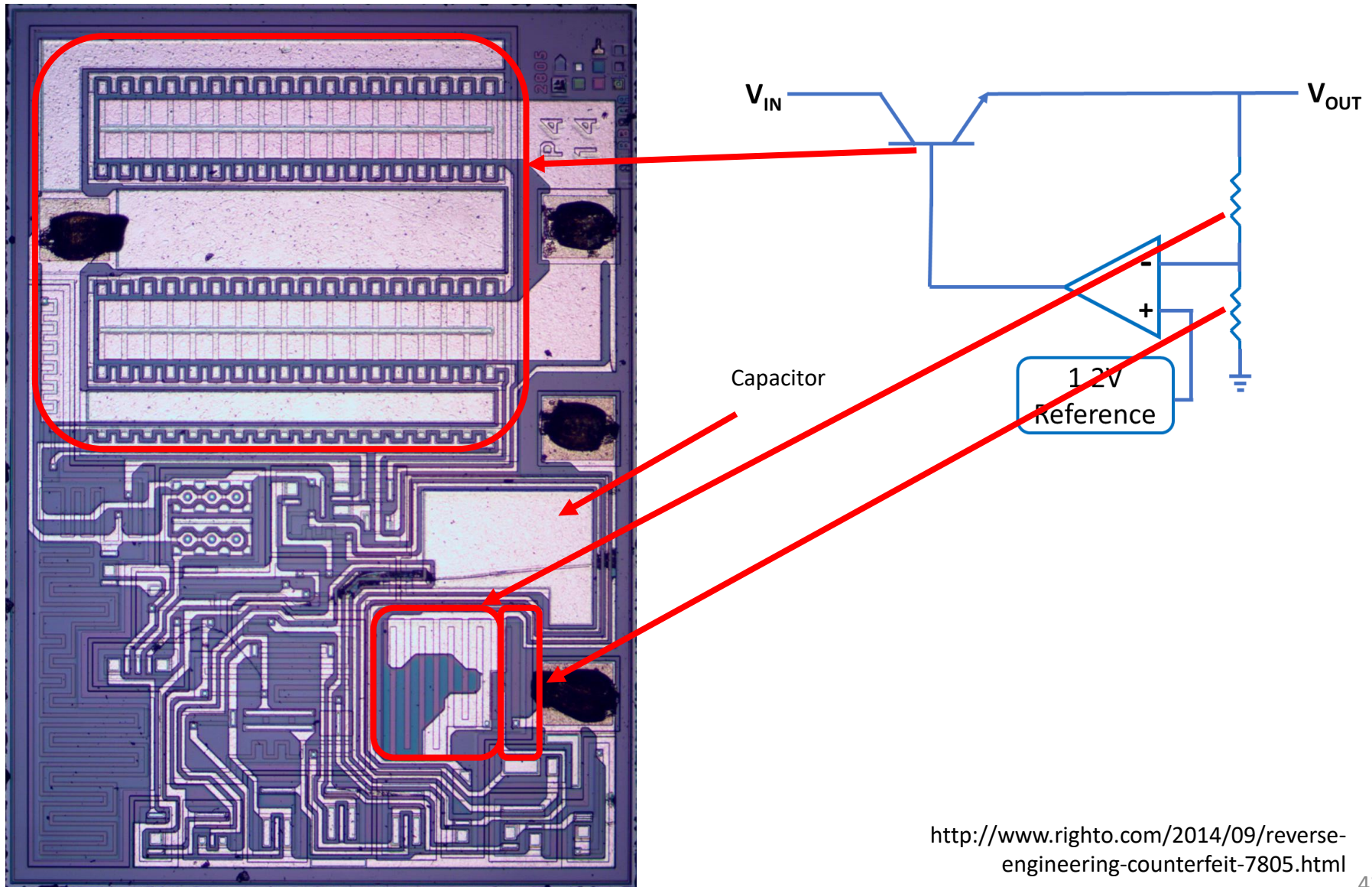


# Thermal Management

## What are we protecting?

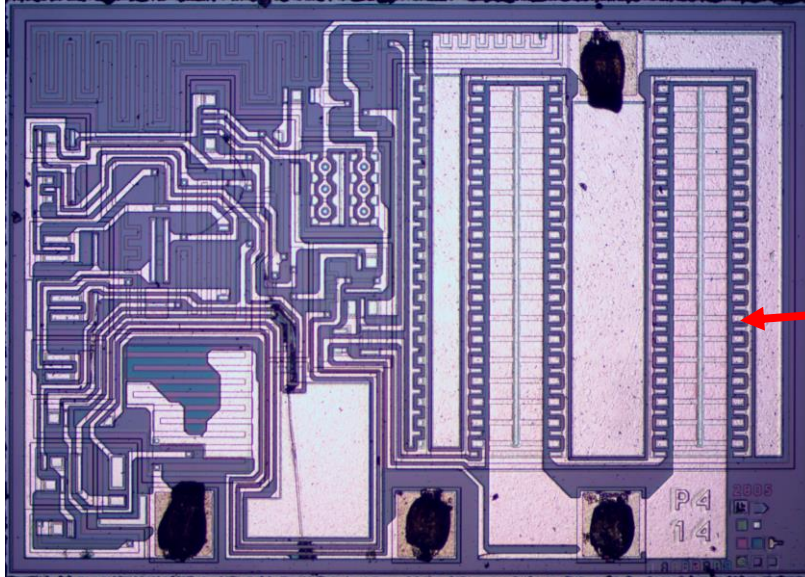

LM7805

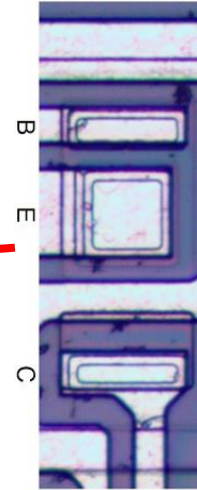

Thermal management is about protecting this from overheating