
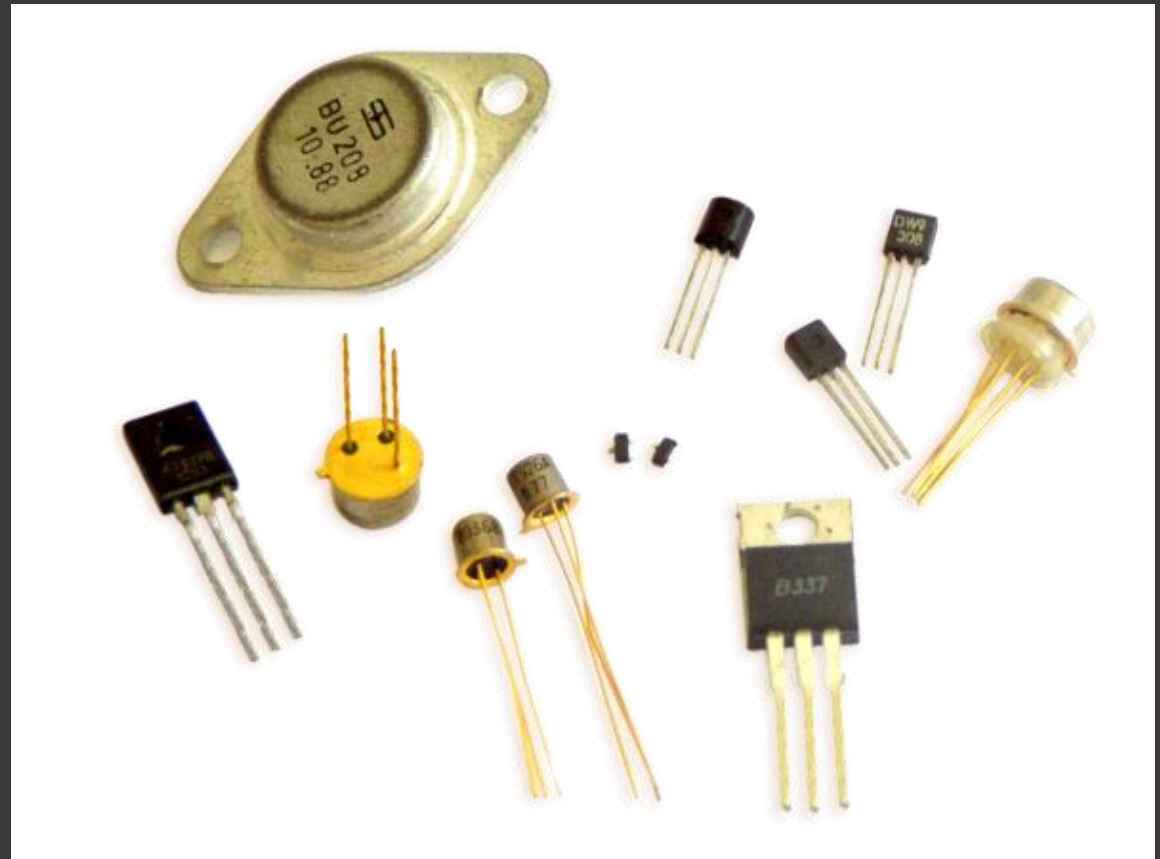


# Using, Choosing and Abusing Transistors

Ray Crampton, Feb 2019

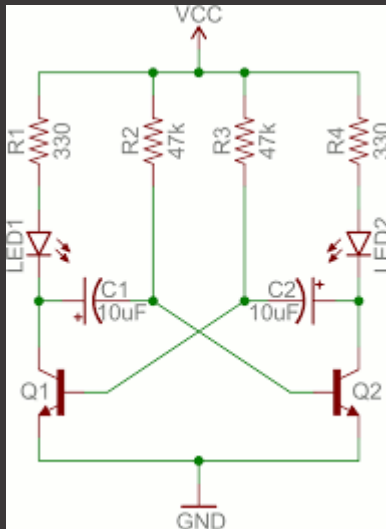

**WARNING**

**WARNING**

**WARNING**

**WARNING**

**WARNING**





**Rules of thumb, assumptions and mixed-quality  
analogies to come!**



# BAD ANALOGIES


**JUST BECAUSE ONE ARGUMENT RESEMBLES ANOTHER,  
DOESN'T MEAN THAT CATS CAN FLY IN SPACE.**

# Common Types of Transistors

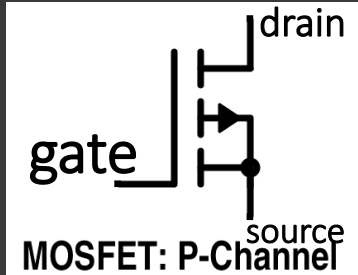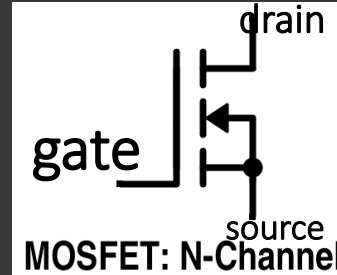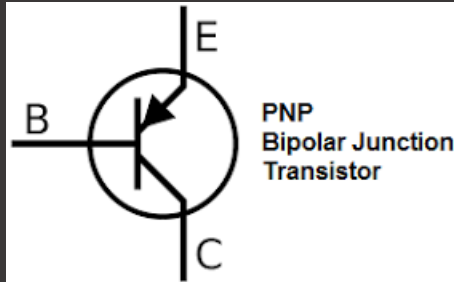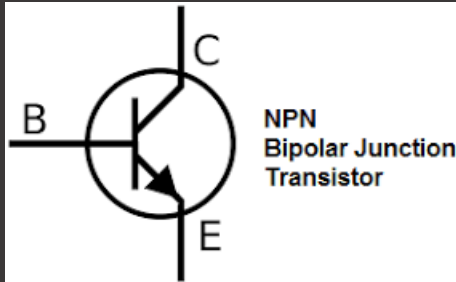





BJT – Base/Emitter/Collector  
FETs – Gate/Drain/Source

Control  
Terminal

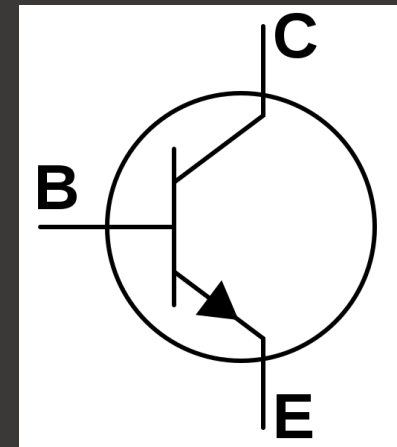


# Transistor as a Switch

## Plumbing Analogy

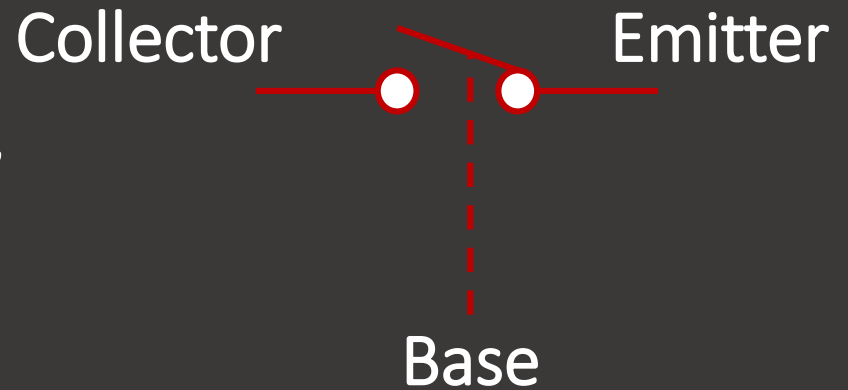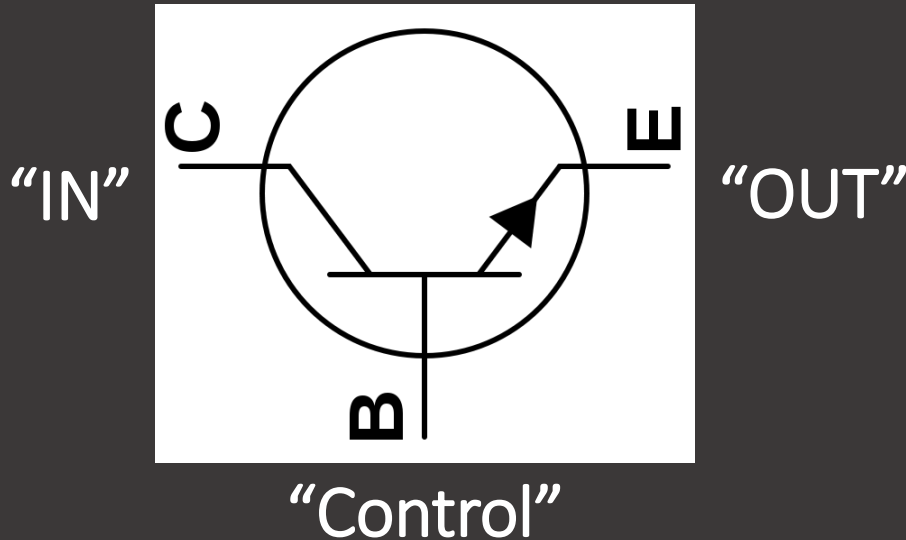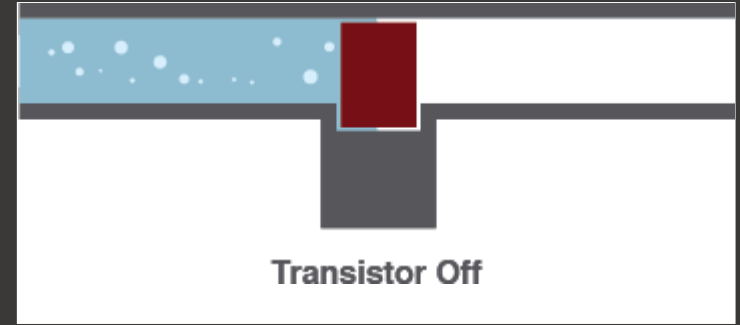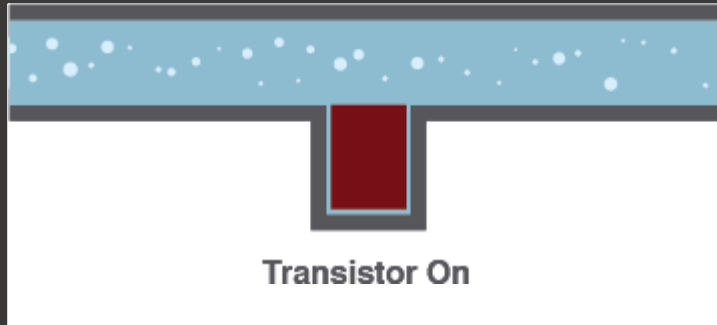


# Falstad.com simulation of NPN Switch

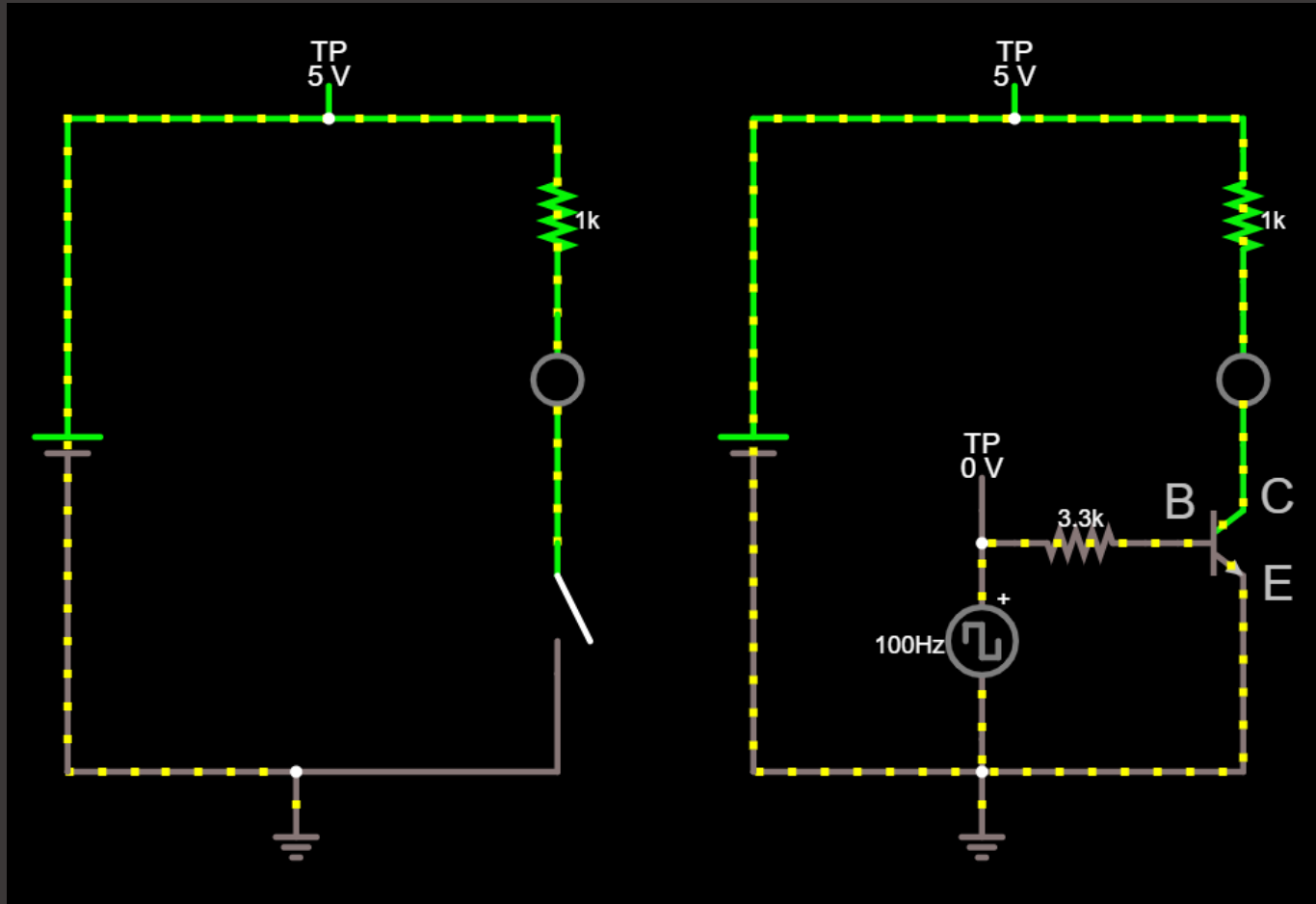

[5](http://falstad.com/circuit/circuitjs.html?cct=$+1+0.000005+3.9121283998153213+59+5+43%0Aw+80+80+192+80+0%0Aw+64+416+64+400+0%0Ag+64+416+64+432+0%0A368+80+80+48+0+0%0Aw+-48+400+64+400+0%0Aw+-48+80+80+80+0%0Av+-48+400+-48+80+0+0+40+5+0+0+0.5%0Aw+192+240+192+288+0%0Aw+192+160+192+176+0%0Ar+192+96+192+160+0+1000%0A162+192+176+192+240+2+default-led+1+0+0+0.01%0Aw+192+352+192+400+0%0Aw+192+400+64+400+0%0As+192+288+192+352+0+1+true%0Aw+192+80+192+96+0%0Aw+528+96+528+80+0%0Aw+416+80+528+80+0%0Aw+400+384+400+400+0%0Aw+400+272+400+288+0%0A368+400+272+400+240+0+0%0Aw+400+416+400+400+0%0Ag+400+416+400+432+0%0A368+416+80+416+48+0+0%0Aw+288+400+400+400+0%0Aw+288+80+416+80+0%0Av+288+400+288+80+0+0+40+5+0+0.5%0Aw+528+240+528+272+0%0Aw+528+160+528+176+0%0Ar+528+96+528+160+0+1000%0A162+528+176+528+240+2+default-led+1+0+0+0.01%0Aw+528+304+528+400+0%0Aw+528+400+400+400+0%0Av+400+384+400+288+0+2+100+2.5+2.5+0+0.5%0At+496+288+528+288+0+1+-4.9998025122489524+3.4649934824506973e-10+100%0Ar+416+288+480+288+0+3300%0Aw+480+288+496+288+0%0Aw+416+288+400+288+0%0Ax+489+276+505+279+4+24+B%0Ax+536+273+553+276+4+24+C%0Ax+537+316+553+319+4+24+E%0A</a></p></div><div data-bbox=)


# BJT: PNP vs NPN

## “High Side” vs “Low Side”

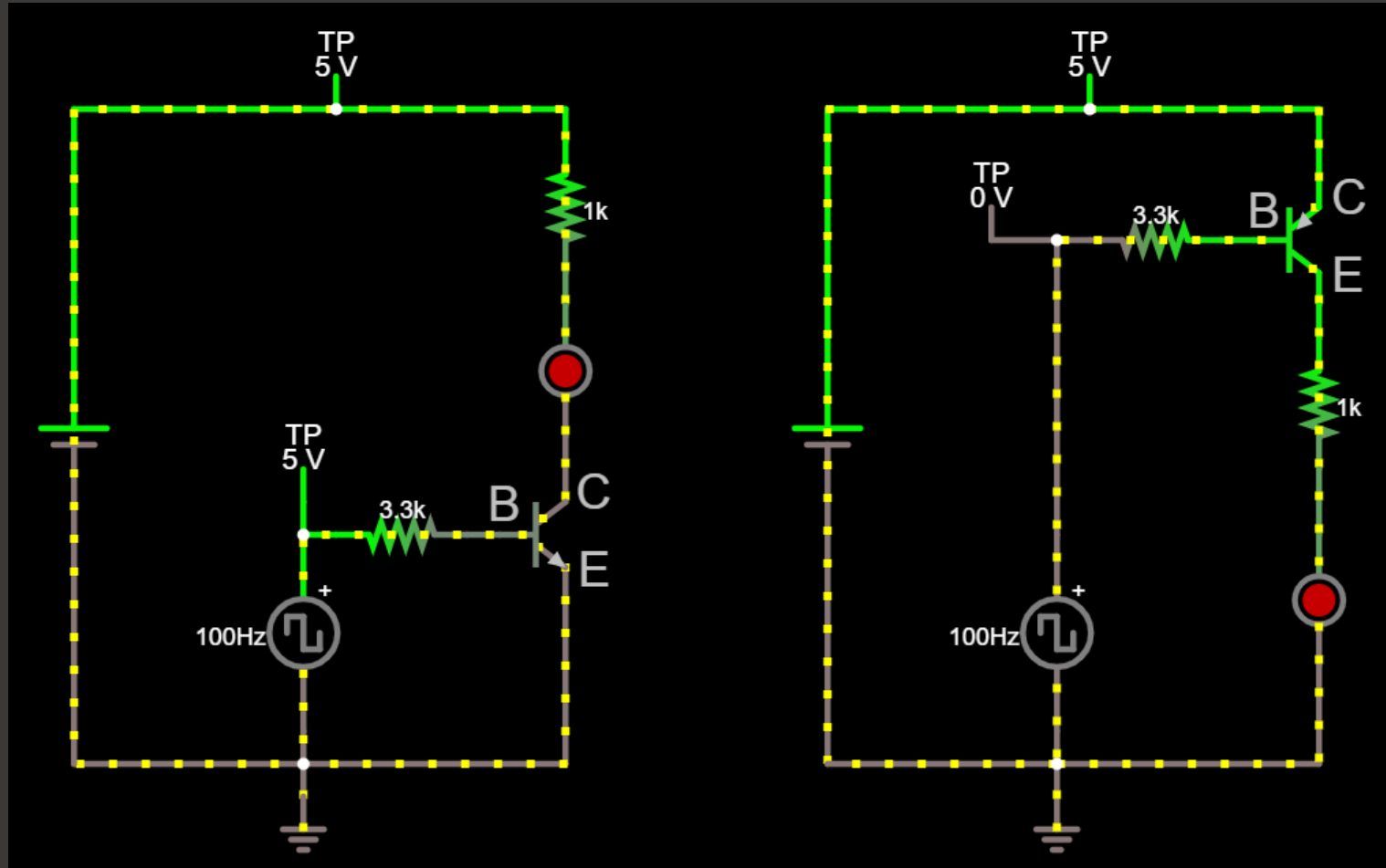



[http://falstad.com/circuit/circuitjs.html?cct=\\$+1+0.000005+3.9121283998153213+59+5+43%0Aw+176+128+176+112+0%0Aw+64+112+176+112+0%0Aw+48+416+48+432+0%0Aw+48+304+48+320+0%0A368+48+304+48+272+0+0%0Aw+48+448+48+432+0%0Ag+48+448+48+464+0%0A368+64+112+64+80+0+0%0Aw+-64+432+48+432+0%0Aw+-64+112+64+112+0%0Av+-64+432+-64+112+0+0+40+5+0+0+0.5%0Aw+176+272+176+304+0%0Aw+176+192+176+208+0%0Ar+176+128+176+192+0+1000%0A162+176+208+176+272+2+default-led+1+0+0+0.01%0Aw+176+336+176+432+0%0Aw+176+432+48+432+0%0Av+48+416+48+320+0+2+100+2.5+2.5+0+0.5%0At+144+320+176+320+0+1+-4.999811893634119+3.464993792036408e-10+100%0Ar+64+320+128+320+0+3300%0Aw+128+320+144+320+0%0Aw+64+320+48+320+0%0Aw+496+176+512+176+0%0Ar+432+176+496+176+0+3300%0Av+416+416+416+320+0+2+100+2.5+2.5+3.141592653589793+0.5%0Aw+544+432+416+432+0%0Aw+544+384+544+432+0%0A162+544+320+544+384+2+default-led+1+0+0+0.01%0Ar+544+224+544+288+0+1000%0Aw+544+192+544+208+0%0Av+304+432+304+112+0+0+40+5+0+0+0.5%0Aw+304+112+432+112+0%0Aw+304+432+416+432+0%0A368+432+112+432+80+0+0%0Ag+416+48+416+464+0%0Aw+416+448+416+432+0%0A368+384+176+384+144+0+0%0Aw+416+176+416+320+0%0Aw+416+416+416+432+0%0Aw+432+112+544+112+0%0Aw+544+128+544+112+0%0At+512+176+544+176+0+-1+4.999788025922517+-3.4649882962867196e-10+10000%0Aw+544+160+544+128+0%0Aw+544+208+544+224+0%0Aw+544+288+544+320+0%0Aw+416+176+432+176+0%0Aw+416+176+384+176+0%0A](http://falstad.com/circuit/circuitjs.html?cct=$+1+0.000005+3.9121283998153213+59+5+43%0Aw+176+128+176+112+0%0Aw+64+112+176+112+0%0Aw+48+416+48+432+0%0Aw+48+304+48+320+0%0A368+48+304+48+272+0+0%0Aw+48+448+48+432+0%0Ag+48+448+48+464+0%0A368+64+112+64+80+0+0%0Aw+-64+432+48+432+0%0Aw+-64+112+64+112+0%0Av+-64+432+-64+112+0+0+40+5+0+0+0.5%0Aw+176+272+176+304+0%0Aw+176+192+176+208+0%0Ar+176+128+176+192+0+1000%0A162+176+208+176+272+2+default-led+1+0+0+0.01%0Aw+176+336+176+432+0%0Aw+176+432+48+432+0%0Av+48+416+48+320+0+2+100+2.5+2.5+0+0.5%0At+144+320+176+320+0+1+-4.999811893634119+3.464993792036408e-10+100%0Ar+64+320+128+320+0+3300%0Aw+128+320+144+320+0%0Aw+64+320+48+320+0%0Aw+496+176+512+176+0%0Ar+432+176+496+176+0+3300%0Av+416+416+416+320+0+2+100+2.5+2.5+3.141592653589793+0.5%0Aw+544+432+416+432+0%0Aw+544+384+544+432+0%0A162+544+320+544+384+2+default-led+1+0+0+0.01%0Ar+544+224+544+288+0+1000%0Aw+544+192+544+208+0%0Av+304+432+304+112+0+0+40+5+0+0+0.5%0Aw+304+112+432+112+0%0Aw+304+432+416+432+0%0A368+432+112+432+80+0+0%0Ag+416+48+416+464+0%0Aw+416+448+416+432+0%0A368+384+176+384+144+0+0%0Aw+416+176+416+320+0%0Aw+416+416+416+432+0%0Aw+432+112+544+112+0%0Aw+544+128+544+112+0%0At+512+176+544+176+0+-1+4.999788025922517+-3.4649882962867196e-10+10000%0Aw+544+160+544+128+0%0Aw+544+208+544+224+0%0Aw+544+288+544+320+0%0Aw+416+176+432+176+0%0Aw+416+176+384+176+0%0A)

# Complementary Bipolar

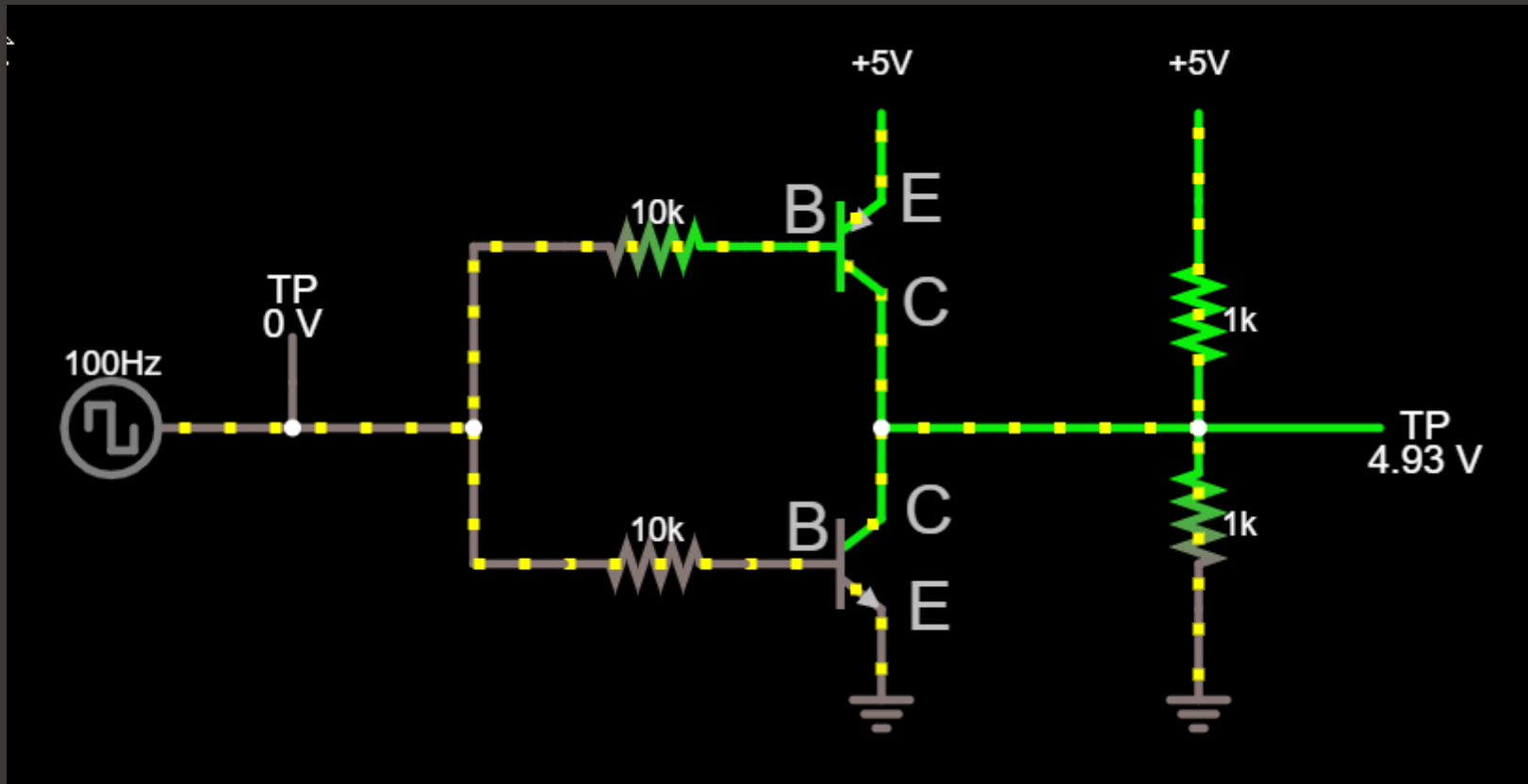


[http://falstad.com/circuit/circuitjs.html?cct=\\$+1+0.000005+3.9121283998153213+59+5+43%0At+224+320+272+320+0+1+0.5705218733467872+0.6402159636357576+100%0Ar+160+320+224+320+0+1000%0Aw+224+208+240+208+0%0Ar+160+208+224+208+0+10000%0Ar+384+272+384+336+0+1000%0Aw+272+224+272+240+0%0A368+64+256+64+224+0+0%0At+240+208+272+208+0+1+4.930305908661726+-1.0493037549963447e-9+10000%0Aw+272+240+272+272+0%0AR+272+192+272+144+0+0+40+5+0+0+0.5%0Aw+272+272+272+304+0%0Aw+272+272+384+272+0%0Ar+384+192+384+272+0+1000%0AR+384+192+384+144+0+0+40+5+0+0+0.5%0Ag+384+336+384+368+0%0Aw+160+208+128+208+0%0Aw+128+208+128+272+0%0Aw+128+272+128+320+0%0Aw+160+320+128+320+0%0AR+64+272+0+272+0+2+100+2.5+2.5+0+0.5%0Aw+64+272+128+272+0%0Aw+64+256+64+272+0%0Ag+272+336+272+368+0%0A368+384+272+464+272+0+0%0Ax+279+236+296+239+4+24+C%0Ax+237+203+253+206+4+24+B%0Ax+280+309+297+312+4+24+C%0Ax+238+315+254+318+4+24+B%0Ax+281+343+297+346+4+24+E%0Ax+278+199+294+202+4+24+E%0A](http://falstad.com/circuit/circuitjs.html?cct=$+1+0.000005+3.9121283998153213+59+5+43%0At+224+320+272+320+0+1+0.5705218733467872+0.6402159636357576+100%0Ar+160+320+224+320+0+1000%0Aw+224+208+240+208+0%0Ar+160+208+224+208+0+10000%0Ar+384+272+384+336+0+1000%0Aw+272+224+272+240+0%0A368+64+256+64+224+0+0%0At+240+208+272+208+0+1+4.930305908661726+-1.0493037549963447e-9+10000%0Aw+272+240+272+272+0%0AR+272+192+272+144+0+0+40+5+0+0+0.5%0Aw+272+272+272+304+0%0Aw+272+272+384+272+0%0Ar+384+192+384+272+0+1000%0AR+384+192+384+144+0+0+40+5+0+0+0.5%0Ag+384+336+384+368+0%0Aw+160+208+128+208+0%0Aw+128+208+128+272+0%0Aw+128+272+128+320+0%0Aw+160+320+128+320+0%0AR+64+272+0+272+0+2+100+2.5+2.5+0+0.5%0Aw+64+272+128+272+0%0Aw+64+256+64+272+0%0Ag+272+336+272+368+0%0A368+384+272+464+272+0+0%0Ax+279+236+296+239+4+24+C%0Ax+237+203+253+206+4+24+B%0Ax+280+309+297+312+4+24+C%0Ax+238+315+254+318+4+24+B%0Ax+281+343+297+346+4+24+E%0Ax+278+199+294+202+4+24+E%0A)

# BJT Motor or LED Driver Example

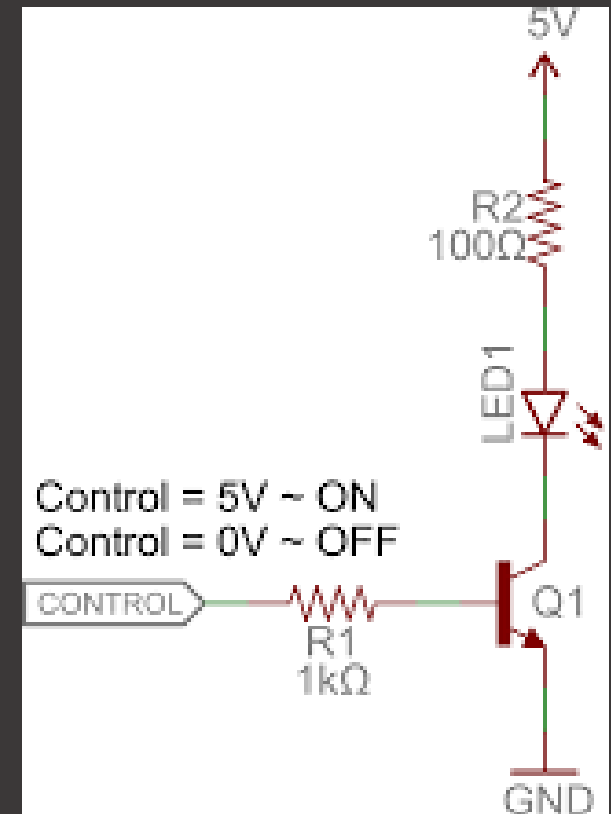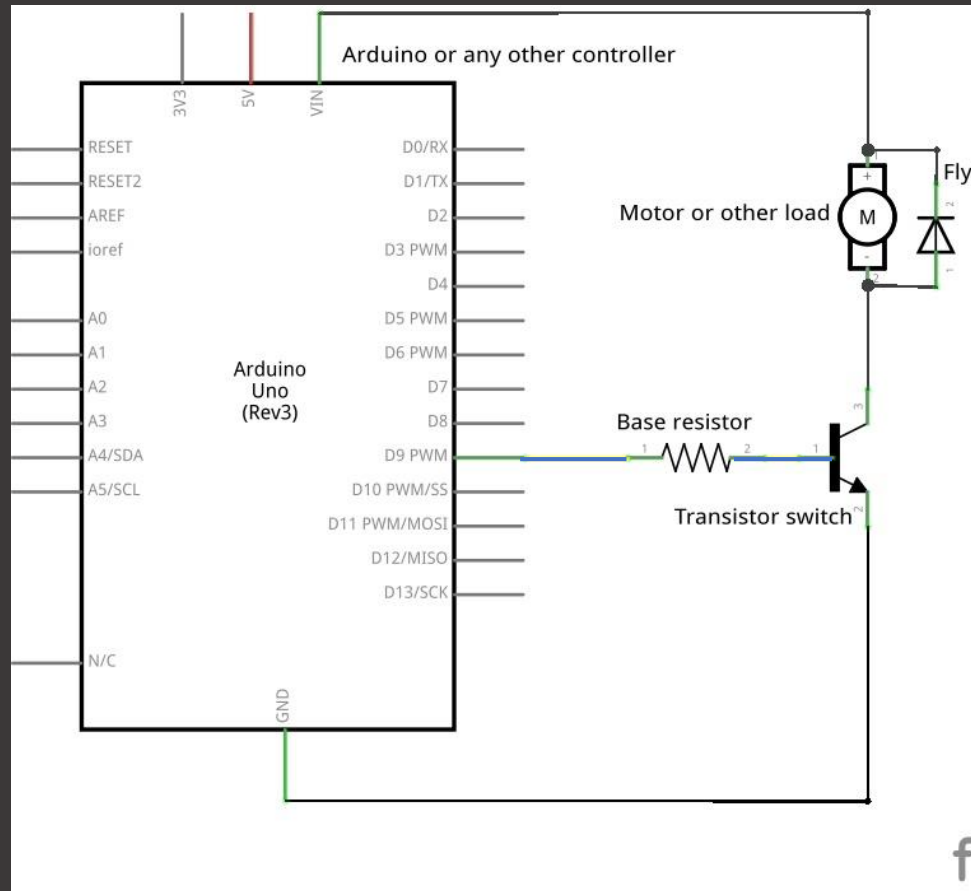





# BJT Photodiode Example

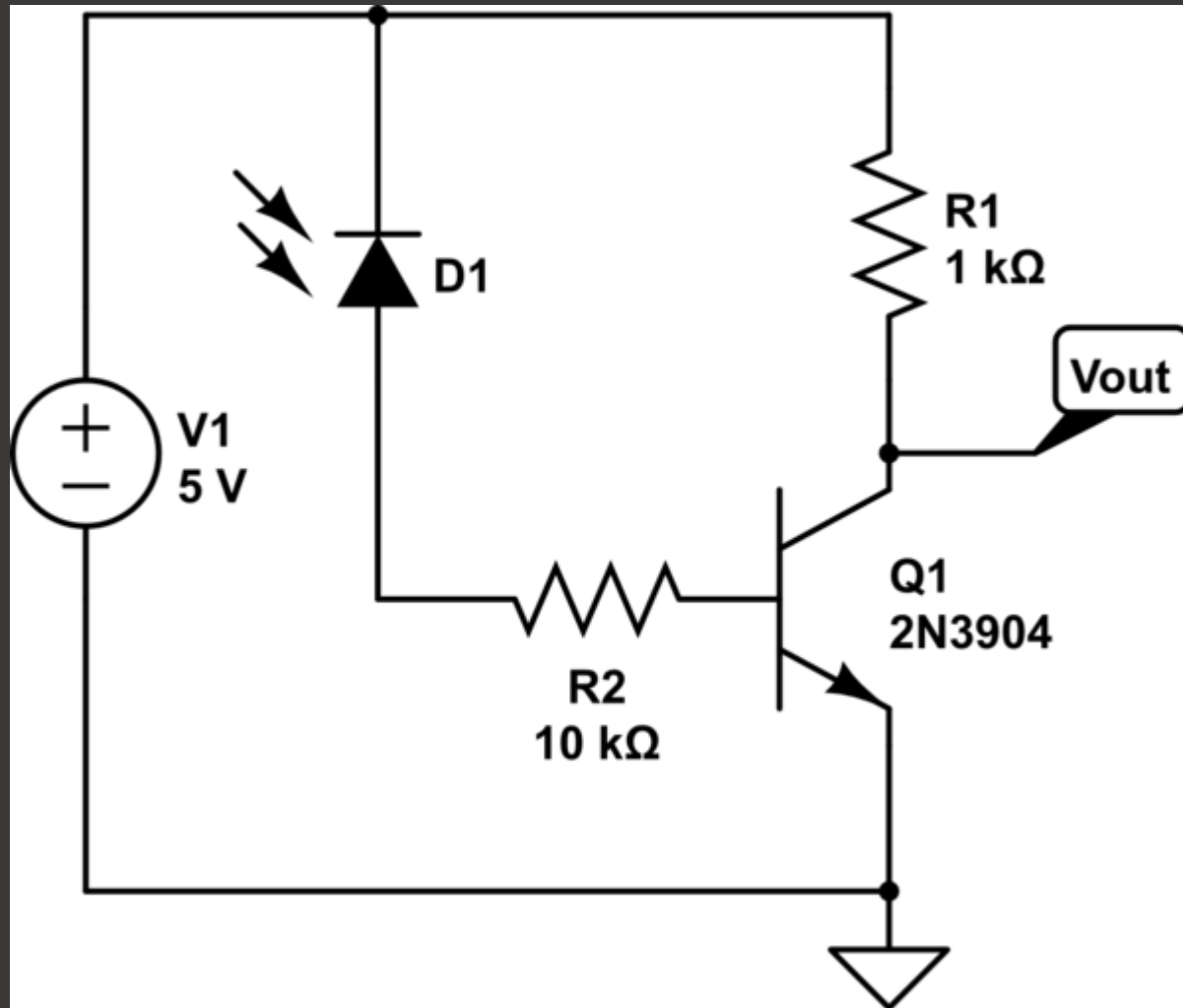

# BJT Speaker Driver Example

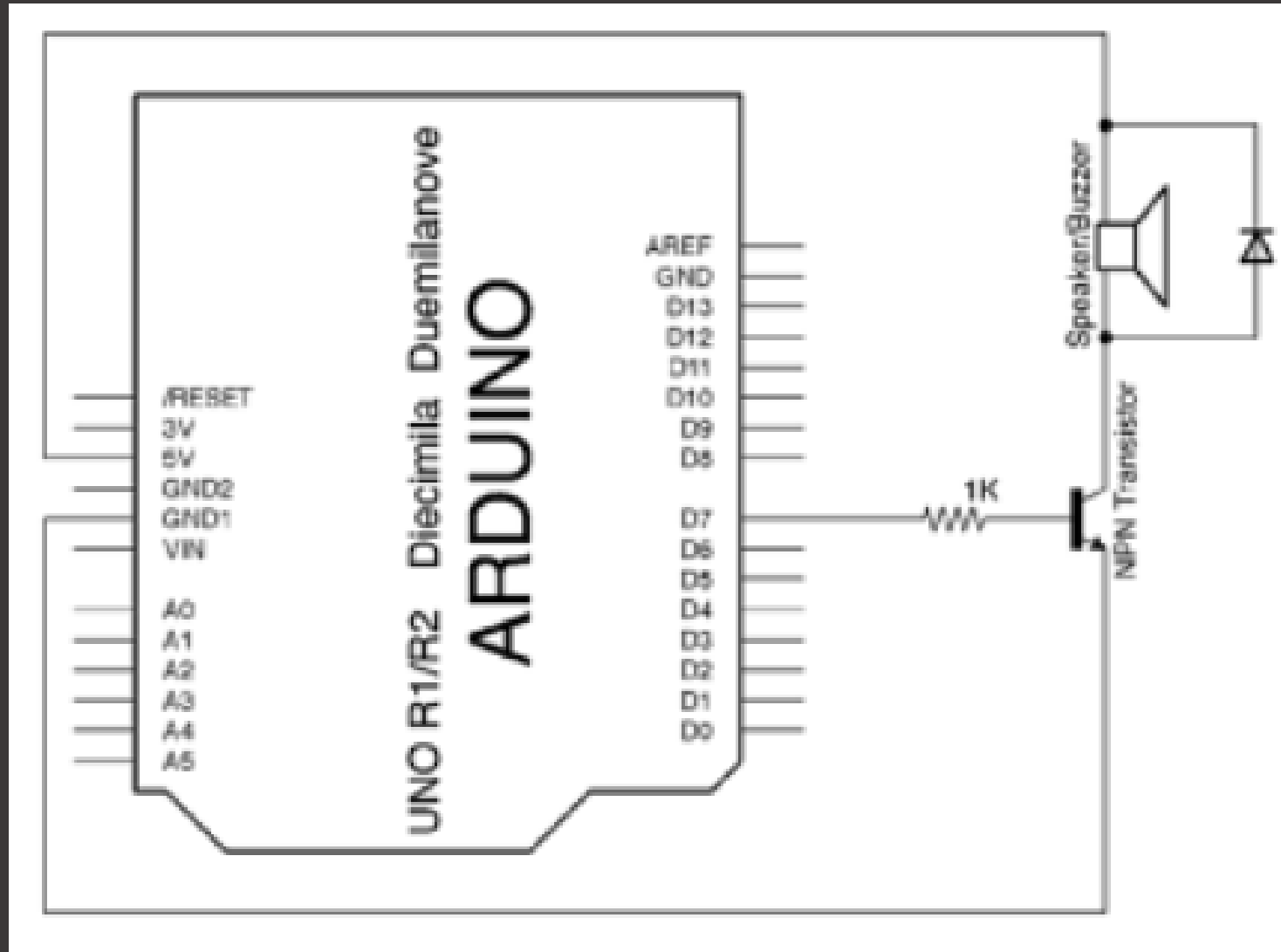


# BJT Relay Example

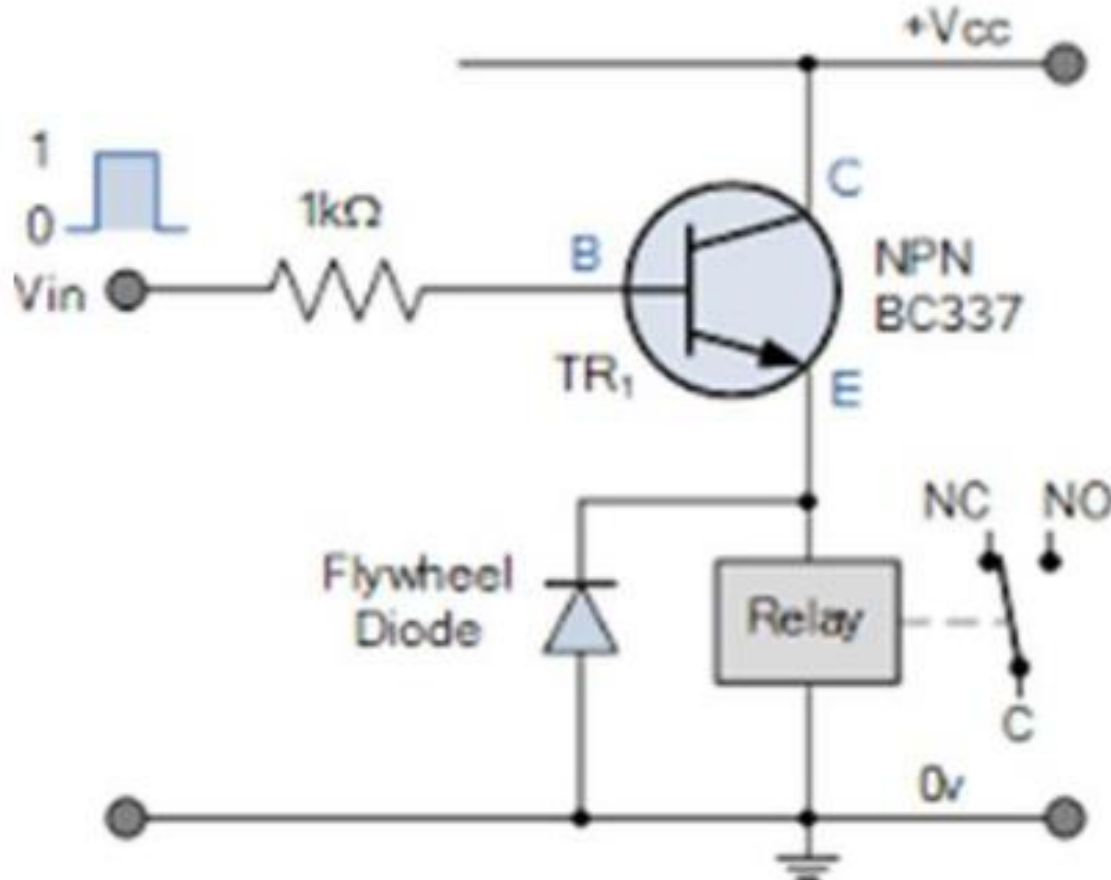

# Common Bipolar Pinouts

TO-92 (Plastic)

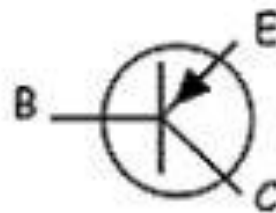


PNP Like 2N3906



NPN Like 2N3904

# Typical Breadboard Application

---

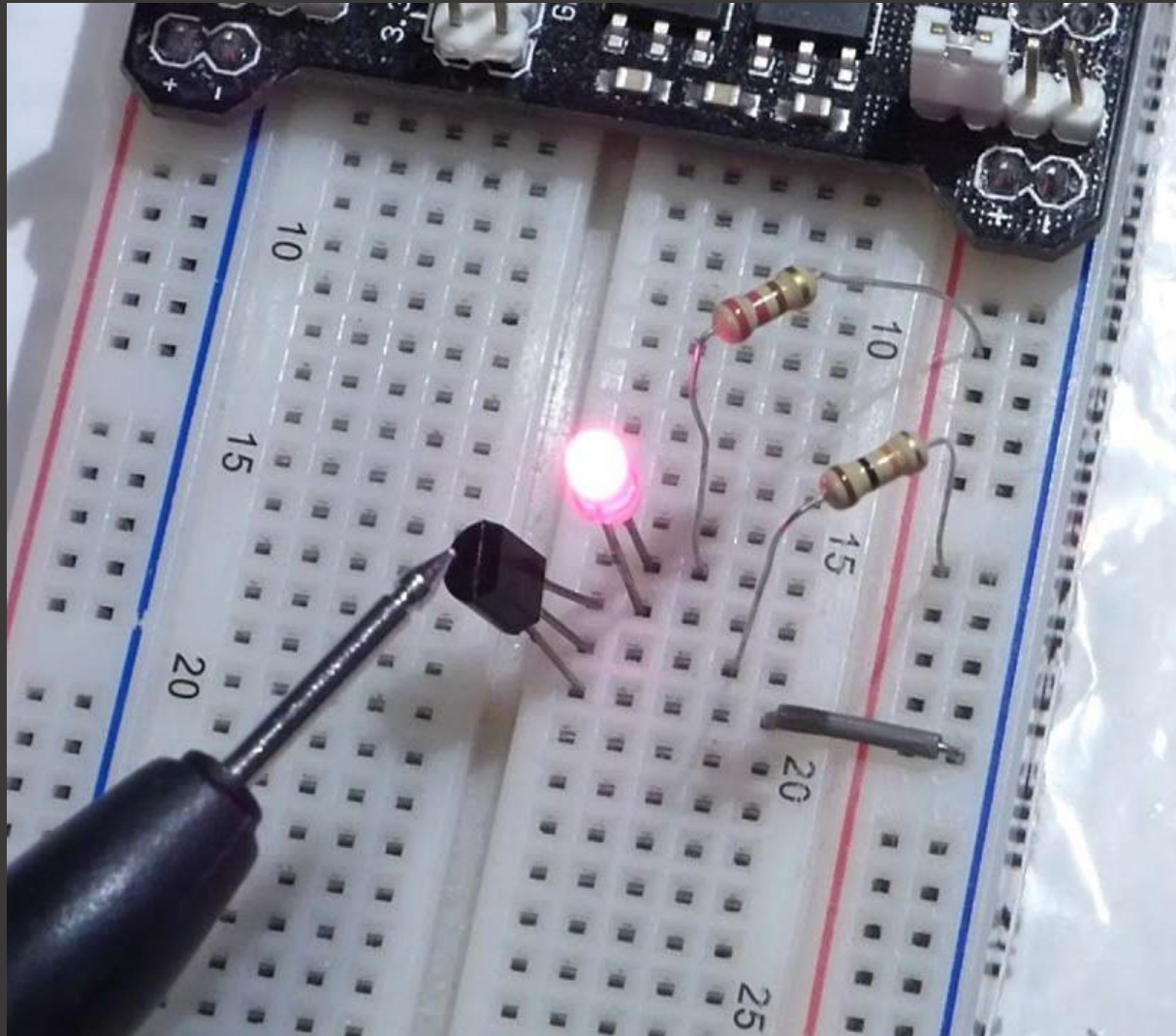

# Key Bipolar Transistor Specs

## OFF CHARACTERISTICS

Collector – Emitter Breakdown Voltage (Note 2) ( $I_C = 1.0 \text{ mAdc}$ , $I_B = 0$ )	$V_{(BR)CEO}$	40	–	Vdc
---	---------------	----	---	-----

## Collector-emitter Breakdown Voltage

- Maximum operating C-E should be 20-50% lower

Collector Current – Continuous	$I_C$	200	mAdc
--------------------------------	-------	-----	------

## Maximum continuous collector current

- You should be below this with some margin ~20%

## SMALL-SIGNAL CHARACTERISTICS

Current – Gain – Bandwidth Product ( $I_C = 10 \text{ mAdc}$ , $V_{CE} = 20 \text{ Vdc}$ , $f = 100 \text{ MHz}$ )	2N3903 2N3904	$f_T$	250 300	– –	MHz
---	------------------	-------	------------	--------	-----




$f_T$  – frequency at which gain falls to 1

- Should be  $> 100\times$  your operating frequency
- Avoid super high frequency transistors (1GHz!)




W. Shockley  
1947  
Nobel Prize 1956


# BJT vs FET as a Switch

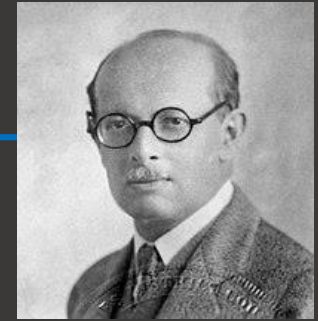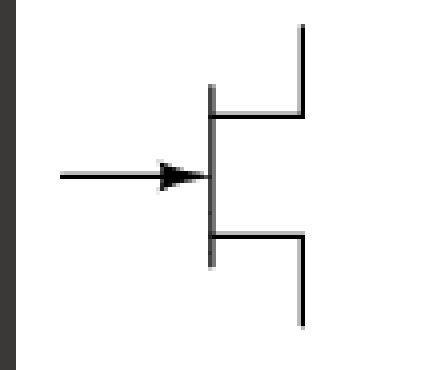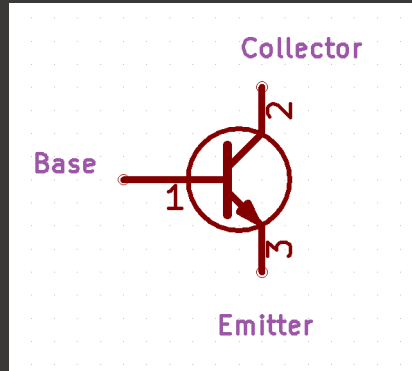

J. E. Lilienfeld  
1925

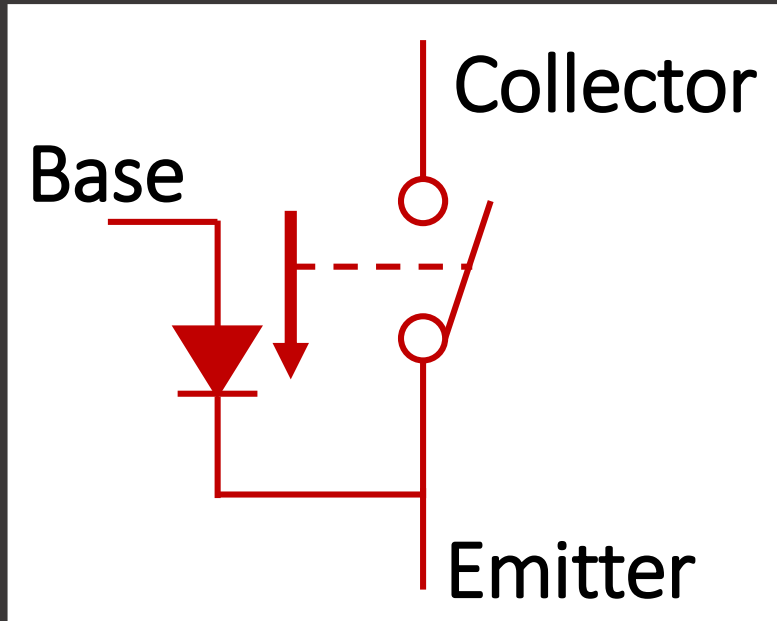


Current Controlled

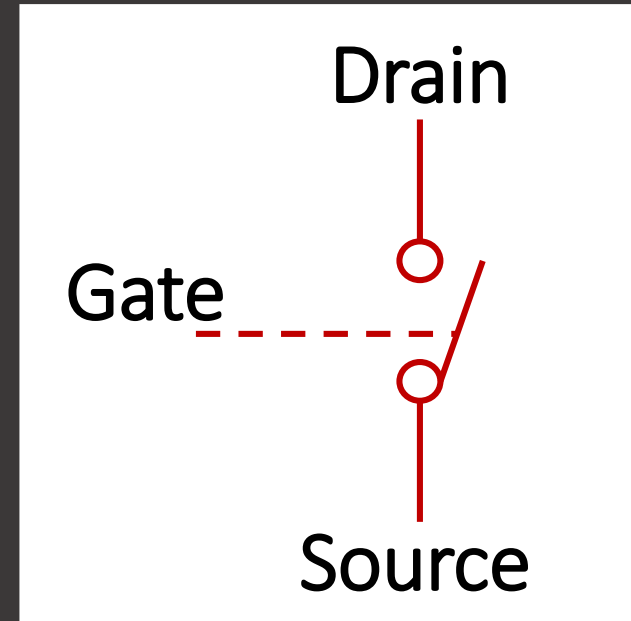

Voltage Controlled

# FET vs BJT in Operation

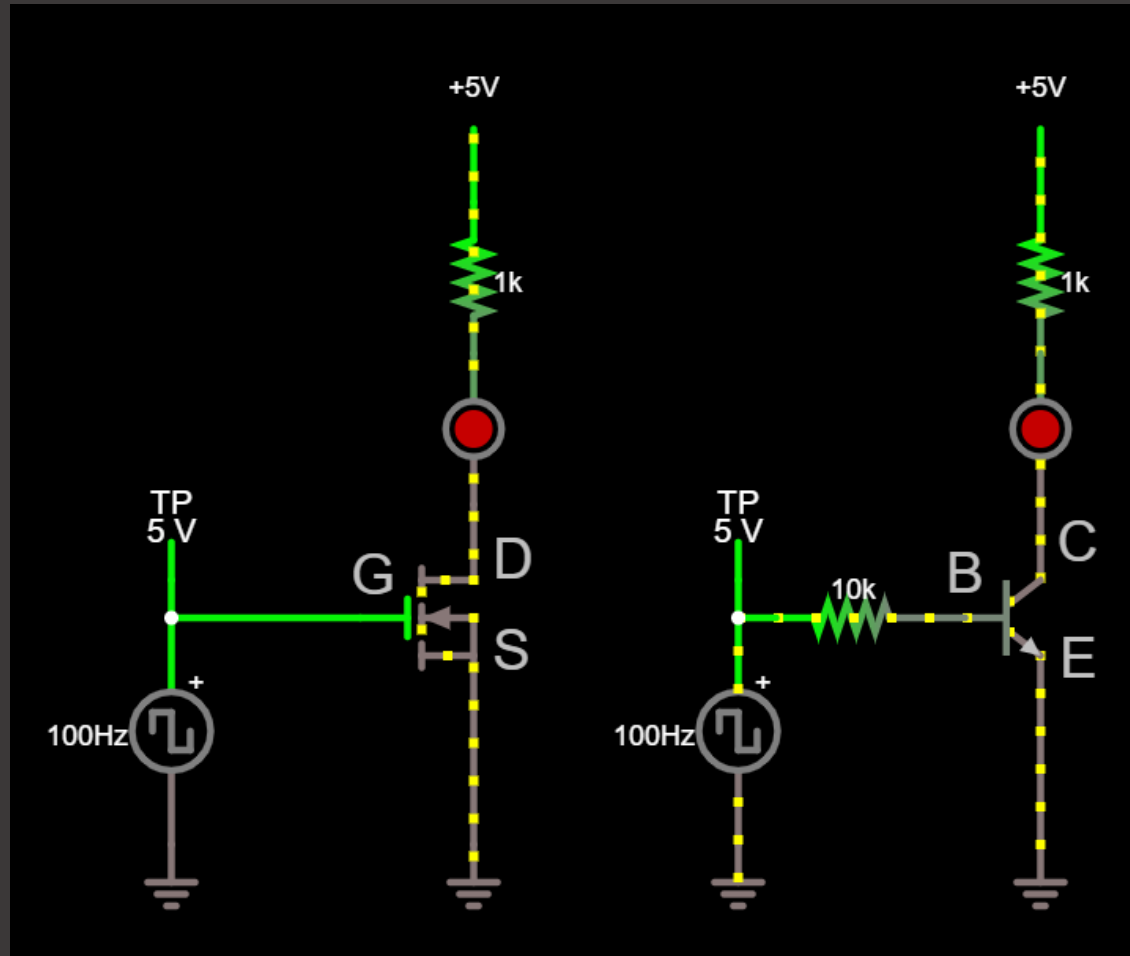

[http://falstad.com/circuit/circuitjs.html?cct=\\$+1+0.000005+3.9121283998153213+59+5+43%0Av+80+384+80+288+0+2+100+2.5+2.5+0+0.5%0Aw+80+288+160+288+0%0A162+208+176+208+240+2+default-](http://falstad.com/circuit/circuitjs.html?cct=$+1+0.000005+3.9121283998153213+59+5+43%0Av+80+384+80+288+0+2+100+2.5+2.5+0+0.5%0Aw+80+288+160+288+0%0A162+208+176+208+240+2+default-)  
led+1+0+0+0.01%0Ar+208+112+208+176+0+1000%0Aw+208+240+208+272+0%0Ag+80+384+80+400+0%0A368+80+272+80+240+0+0%0Aw+80+272+80+288+0%0Aw+320+272+320+288+0%0A368+320+272+320+240+0+0%0Ag+320+384+320+400+0%0Aw+448+240+448+272+0%0Ar+448+112+448+176+0+1000%0A162+448+176+448+240+2+default-  
led+1+0+0+0.01%0Aw+448+304+448+384+0%0Av+320+384+320+288+0+2+100+2.5+0+0.5%0At+416+288+448+288+0+1+-4.999808758737633+1.049998087170923e-9+100%0Ar+336+288+400+288+0+10000%0Aw+400+288+416+288+0%0Aw+336+288+320+288+0%0AR+448+112+448+64+0+0+40+5+0+0+0.5%0Ag+448+384+448+400+0%0Aw+208+304+208+384+0%0Ag+208+384+208+400+0%0AR+208+112+208+64+0+0+40+5+0+0+0.5%0Af+160+288+208+288+32+1.5+1%0A



The figure contains two circuit diagrams for a MOSFET switching experiment. Both circuits use a 5V supply, a 1kΩ resistor, and a 100Hz AC source.

**Left Diagram (Common-Source Configuration):**


- The MOSFET's source (S) is connected to ground.
- The drain (D) is connected to a 1kΩ resistor, which is then connected to the 5V supply.
- The gate (G) is connected to a 100Hz AC source.
- A test point (TP) is located at the 5V supply.
- Another test point (TP) is located at the gate (G), labeled 0V.
- A red LED is connected between the drain (D) and ground.

**Right Diagram (Common-Drain Configuration):**

- The MOSFET's gate (G) is connected to a 100Hz AC source.
- The drain (D) is connected directly to the 5V supply.
- The source (S) is connected to a 1kΩ resistor, which is then connected to ground.
- A test point (TP) is located at the 5V supply.
- Another test point (TP) is located at the gate (G), labeled 0V.


17

# CMOS Output

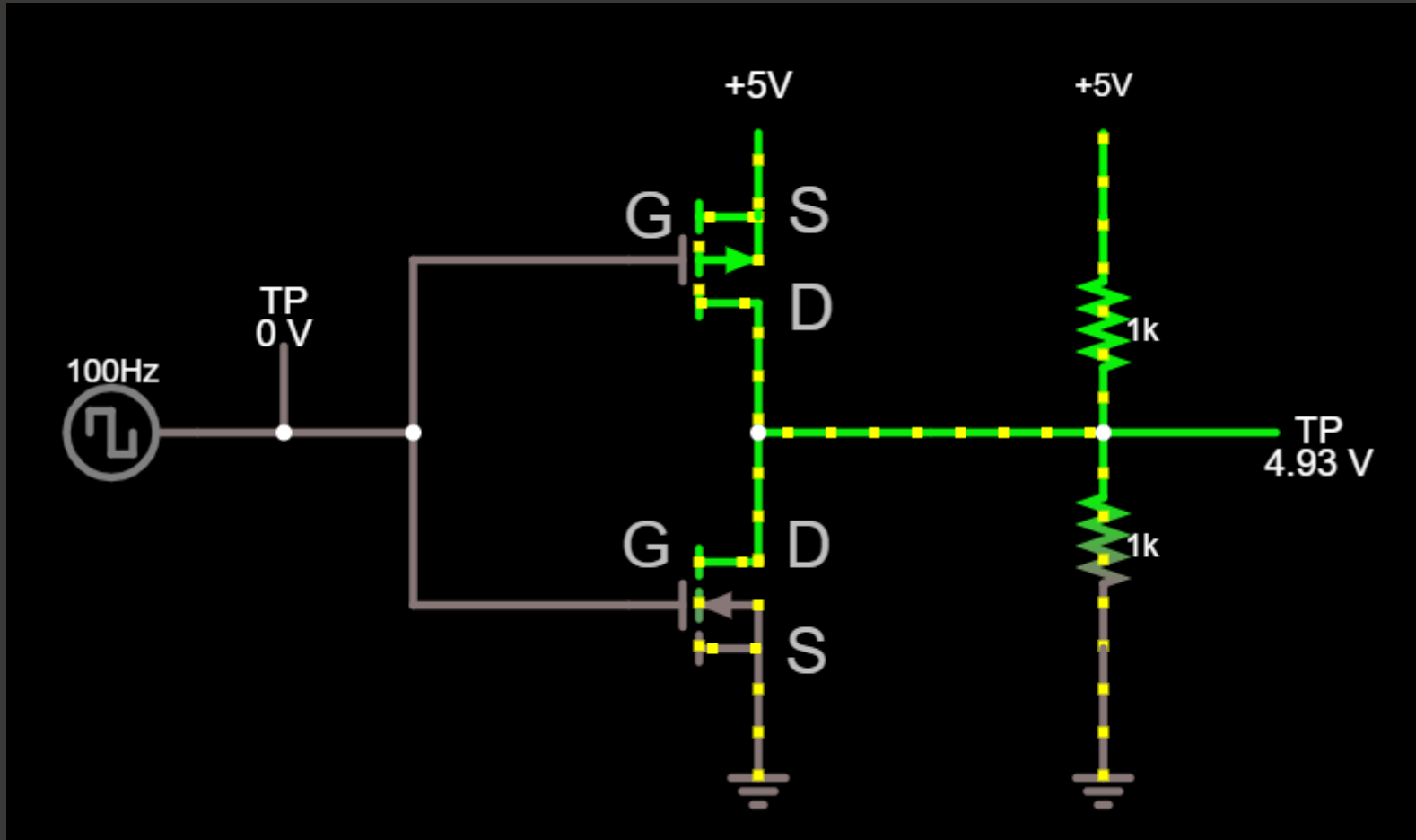


[http://falstad.com/circuit/circuitjs.html?cct=\\$+1+0.000005+3.9121283998153213+59+5+43%0Ar+432+272+432+352+0+1000%0Ag+304+352+304+400+0%0A368+432+272+512+272+0+0%0Aw+304+272+304+320+0%0Af+256+336+304+336+32+1.5+0.02%0Af+256+208+304+208+33+1.5+0.02%0A368+128+272+128+224+0+0%0Ax+244+189+262+192+4+24+G%0Ax+319+195+335+198+4+24+S%0Ax+321+237+338+240+4+24+D%0AR+304+192+304+144+0+0+40+5+0+0+0.5%0Aw+304+224+304+272+0%0Aw+304+272+368+272+0%0Aw+256+208+176+208+0%0Aw+176+336+256+336+0%0Aw+176+272+128+272+0%0Aw+128+272+96+272+0%0AR+96+272+64+272+0+2+100+2.5+2.5+0+0.5%0AR+432+192+432+272+0+1000%0Ag+432+352+432+400+0%0AR+432+192+432+144+0+0+40+5+0+0+0.5%0Aw+368+272+432+272+0%0Aw+176+208+176+272+0%0Aw+176+272+176+336+0%0A](http://falstad.com/circuit/circuitjs.html?cct=$+1+0.000005+3.9121283998153213+59+5+43%0Ar+432+272+432+352+0+1000%0Ag+304+352+304+400+0%0A368+432+272+512+272+0+0%0Aw+304+272+304+320+0%0Af+256+336+304+336+32+1.5+0.02%0Af+256+208+304+208+33+1.5+0.02%0A368+128+272+128+224+0+0%0Ax+244+189+262+192+4+24+G%0Ax+319+195+335+198+4+24+S%0Ax+321+237+338+240+4+24+D%0AR+304+192+304+144+0+0+40+5+0+0+0.5%0Aw+304+224+304+272+0%0Aw+304+272+368+272+0%0Aw+256+208+176+208+0%0Aw+176+336+256+336+0%0Aw+176+272+128+272+0%0Aw+128+272+96+272+0%0AR+96+272+64+272+0+2+100+2.5+2.5+0+0.5%0AR+432+192+432+272+0+1000%0Ag+432+352+432+400+0%0AR+432+192+432+144+0+0+40+5+0+0+0.5%0Aw+368+272+432+272+0%0Aw+176+208+176+272+0%0Aw+176+272+176+336+0%0A)

# MOSFET Examples

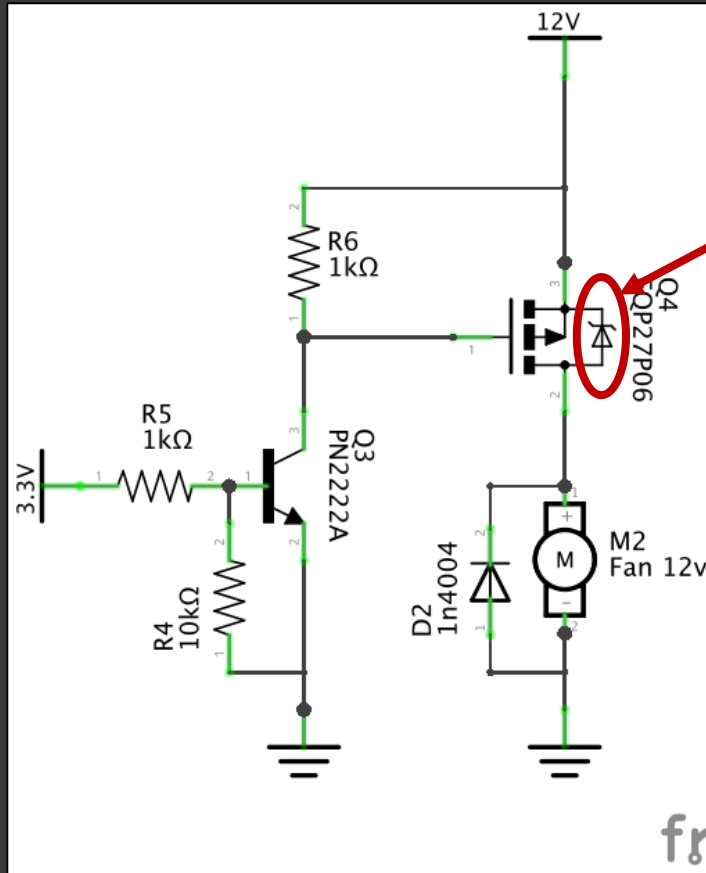

Note the “body diode” which is intrinsic to all MOSFETs

## Fault Protected High Side Switch

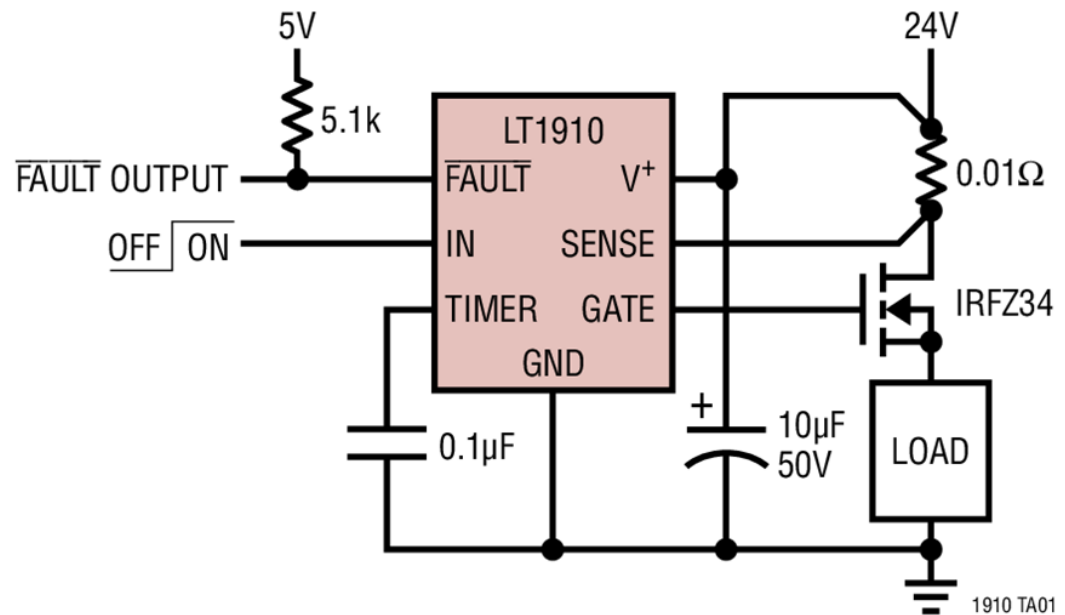

### FET AUDIO SWITCH

**Q1**  
2N5462

**C1** 10U

**R1** 10K

**C3**

**U01**

**R3** 1M0

**R2** 10K

**C2** 10U

**AUDIO IN**

**AUDIO OUT**

**+V**

**R4** 33K

**CTL**

**Q2** 2N2222

**R5** 10K

**C4** 10U

**U10**

**0=AUDIO**  
**1=MUTE**

**OPTIONAL**

**RC031230**

# Key MOSFET Specs

Characteristic	Symbol	Min	Max	Unit
<b>OFF CHARACTERISTICS</b>				
Drain-Source Breakdown Voltage ( $V_{GS} = 0, I_D = 10 \mu A_{dc}$ )	$V_{(BR)DSS}$	60	–	Vdc

## Drain-Source Breakdown Voltage

- Maximum operating D-S should be 20-50% lower

<b>ON CHARACTERISTICS (Note 1)</b>				
Gate Threshold Voltage ( $V_{DS} = V_{GS}, I_D = 1.0 mA_{dc}$ )	$V_{GS(th)}$	0.8	3.0	Vdc

## Gate threshold voltage




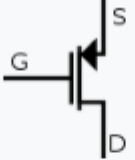

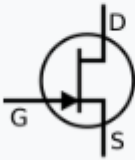
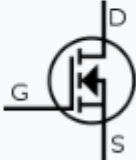

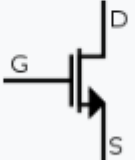

- You should be well above/below this

Static Drain-Source On-Resistance ( $V_{GS} = 10 V_{dc}, I_D = 0.5 A_{dc}$ ) ( $V_{GS} = 4.5 V_{dc}, I_D = 75 mA_{dc}$ )	$r_{DS(on)}$	– –	5.0 6.0	$\Omega$
Drain-Source On-Voltage ( $V_{GS} = 10 V_{dc}, I_D = 0.5 A_{dc}$ ) ( $V_{GS} = 4.5 V_{dc}, I_D = 75 mA_{dc}$ )	$V_{DS(on)}$	– –	2.5 0.45	Vdc

## On-Voltage


- Should be low enough

# MOSFET Schematic Symbols

<b>P-channel</b>					
<b>N-channel</b>					
	<b>JFET</b>	<b>MOSFET enh.</b>	<b>MOSFET enh. (no bulk)</b>	<b>MOSFET dep.</b>	


- There are many, many variations on these
- FETs of the same type (P vs N) behave similar to each other
- Be aware but don't fret over it too much

# “Common Emitter/Source” Inverts

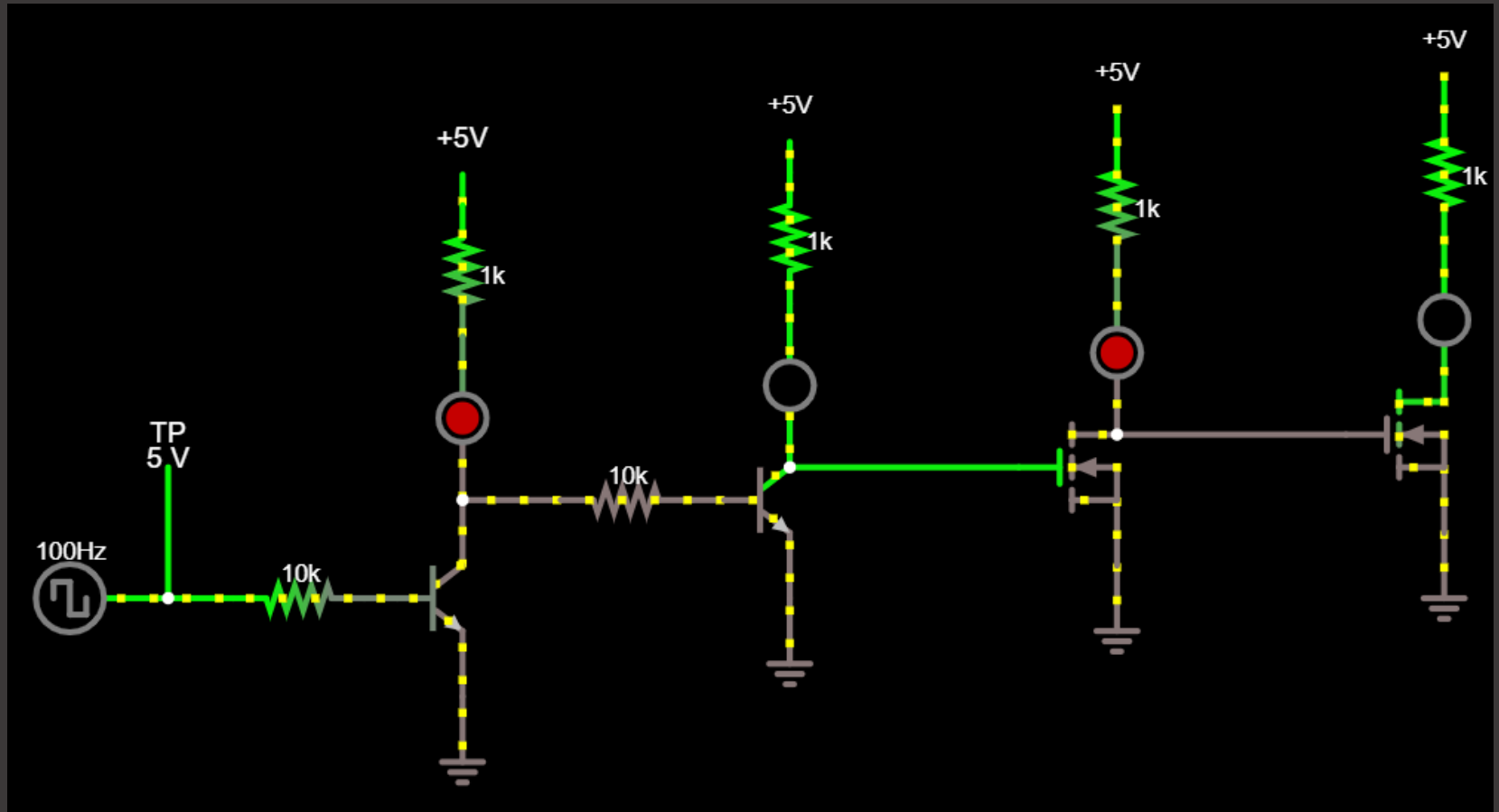

[http://falstad.com/circuit/circuitjs.html?cct=\\$+1+0.000005+3.9121283998153213+59+5+43%0Ar+464+240+464+304+0+1000%0Ag+272+336+272+368+0%0Aw+272+240+272+272+0%0At+240+288+272+288+0+1+0.5705218733467888+0.640215963635758+100%0Ar+160+288+224+288+0+10000%0Aw+224+288+240+288+0%0A368+96+240+96+160+0+0%0At+240+192+272+192+0+-1+4.930305908661727+-1.0493037549963447e-9+10000%0Aw+272+208+272+240+0%0AR+272+144+272+112+0+0+40+5+0+0+0.5%0Aw+272+144+272+176+0%0Aw+272+304+272+336+0%0Ar+160+192+224+192+0+10000%0Aw+160+288+128+288+0%0Aw+160+192+128+192+0%0Aw+128+192+128+240+0%0Aw+128+240+128+288+0%0Aw+128+240+96+240+0%0AR+96+240+48+240+0+2+100+2.5+2.5+0+0.5%0Ar+464+176+464+240+0+1000%0Ag+464+304+464+336+0%0AR+464+176+464+144+0+0+40+5+0+0+0.5%0A368+400+240+400+160+0+0%0Aw+464+240+400+240+0%0Aw+400+240+272+240+0%0Ax+308+201+357+204+4+24+PNP%0Ax+305+300+355+303+4+24+NPN%0Ax+235+181+251+184+4+24+B%0Ax+236+278+252+281+4+24+B%0Aw+240+192+224+192+0%0Ax+280+274+297+277+4+24+C%0Ax+280+220+297+223+4+24+C%0Ax+281+320+297+323+4+24+E%0Ax+280+177+296+180+4+24+E%0A](http://falstad.com/circuit/circuitjs.html?cct=$+1+0.000005+3.9121283998153213+59+5+43%0Ar+464+240+464+304+0+1000%0Ag+272+336+272+368+0%0Aw+272+240+272+272+0%0At+240+288+272+288+0+1+0.5705218733467888+0.640215963635758+100%0Ar+160+288+224+288+0+10000%0Aw+224+288+240+288+0%0A368+96+240+96+160+0+0%0At+240+192+272+192+0+-1+4.930305908661727+-1.0493037549963447e-9+10000%0Aw+272+208+272+240+0%0AR+272+144+272+112+0+0+40+5+0+0+0.5%0Aw+272+144+272+176+0%0Aw+272+304+272+336+0%0Ar+160+192+224+192+0+10000%0Aw+160+288+128+288+0%0Aw+160+192+128+192+0%0Aw+128+192+128+240+0%0Aw+128+240+128+288+0%0Aw+128+240+96+240+0%0AR+96+240+48+240+0+2+100+2.5+2.5+0+0.5%0Ar+464+176+464+240+0+1000%0Ag+464+304+464+336+0%0AR+464+176+464+144+0+0+40+5+0+0+0.5%0A368+400+240+400+160+0+0%0Aw+464+240+400+240+0%0Aw+400+240+272+240+0%0Ax+308+201+357+204+4+24+PNP%0Ax+305+300+355+303+4+24+NPN%0Ax+235+181+251+184+4+24+B%0Ax+236+278+252+281+4+24+B%0Aw+240+192+224+192+0%0Ax+280+274+297+277+4+24+C%0Ax+280+220+297+223+4+24+C%0Ax+281+320+297+323+4+24+E%0Ax+280+177+296+180+4+24+E%0A)

# Same on the High Side

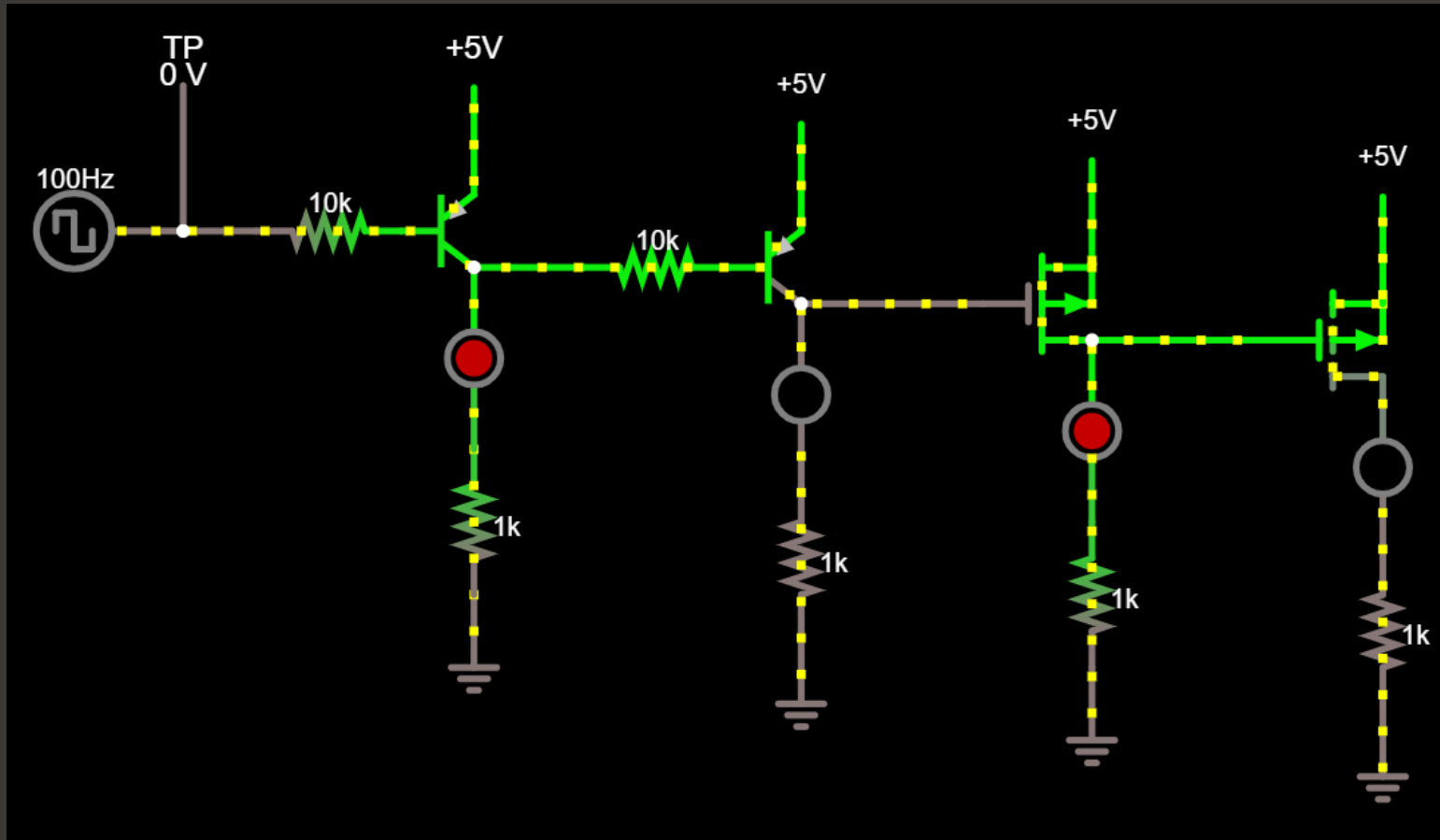

[http://falstad.com/circuit/circuitjs.html?cct=\\$+1+0.000005+3.9121283998153213+59+5+43%0Ar+0+320+64+320+0+10000%0Aw+64+320+80+320+0%0A368+-32+320+-32+240+0+0%0AR+112+304+112+224+0+0+40+5+0+0+0.5%0Aw+0+320+-32+320+0%0AR+-32+320+-80+320+0+2+100+2.5+0+0.5%0Aw+160+336+112+336+0%0A162+272+352+272+432+2+default-led+1+0+0+0.01%0Ar+272+432+272+496+0+1000%0AR+272+320+272+224+0+0+40+5+0+0+0.5%0Aw+224+336+240+336+0%0Ar+160+336+224+336+0+10000%0Ag+272+496+272+528+0%0Aw+384+352+272+352+0%0At+80+320+112+320+0+-1+-0.5716207307972958+-0.6317815784740484+100%0At+240+336+272+336+0+-1+4.9386779068845374+-0.06016084863317328+100%0Ag+112+480+112+512+0%0Ar+112+416+112+480+0+1000%0A162+112+336+112+416+2+default-led+1+0+0+0.01%0Af+384+352+432+352+33+1.5+0.02%0Ag+432+512+432+544+0%0Ar+432+448+432+512+0+1000%0A162+432+368+432+448+2+default-led+1+0+0+0.01%0AR+432+336+432+240+0+0+40+5+0+0+0.5%0AR+592+352+592+256+0+0+40+5+0+0+0.5%0A162+592+384+592+464+2+default-led+1+0+0+0.01%0Ar+592+464+592+528+0+1000%0Ag+592+528+592+560+0%0Af+544+368+592+368+33+1.5+0.02%0Aw+544+368+432+368+0%0A](http://falstad.com/circuit/circuitjs.html?cct=$+1+0.000005+3.9121283998153213+59+5+43%0Ar+0+320+64+320+0+10000%0Aw+64+320+80+320+0%0A368+-32+320+-32+240+0+0%0AR+112+304+112+224+0+0+40+5+0+0+0.5%0Aw+0+320+-32+320+0%0AR+-32+320+-80+320+0+2+100+2.5+0+0.5%0Aw+160+336+112+336+0%0A162+272+352+272+432+2+default-led+1+0+0+0.01%0Ar+272+432+272+496+0+1000%0AR+272+320+272+224+0+0+40+5+0+0+0.5%0Aw+224+336+240+336+0%0Ar+160+336+224+336+0+10000%0Ag+272+496+272+528+0%0Aw+384+352+272+352+0%0At+80+320+112+320+0+-1+-0.5716207307972958+-0.6317815784740484+100%0At+240+336+272+336+0+-1+4.9386779068845374+-0.06016084863317328+100%0Ag+112+480+112+512+0%0Ar+112+416+112+480+0+1000%0A162+112+336+112+416+2+default-led+1+0+0+0.01%0Af+384+352+432+352+33+1.5+0.02%0Ag+432+512+432+544+0%0Ar+432+448+432+512+0+1000%0A162+432+368+432+448+2+default-led+1+0+0+0.01%0AR+432+336+432+240+0+0+40+5+0+0+0.5%0AR+592+352+592+256+0+0+40+5+0+0+0.5%0A162+592+384+592+464+2+default-led+1+0+0+0.01%0Ar+592+464+592+528+0+1000%0Ag+592+528+592+560+0%0Af+544+368+592+368+33+1.5+0.02%0Aw+544+368+432+368+0%0A)





And now  
for something  
completely different...




# Transistors as Amplifiers

# A More Accurate NPN Model

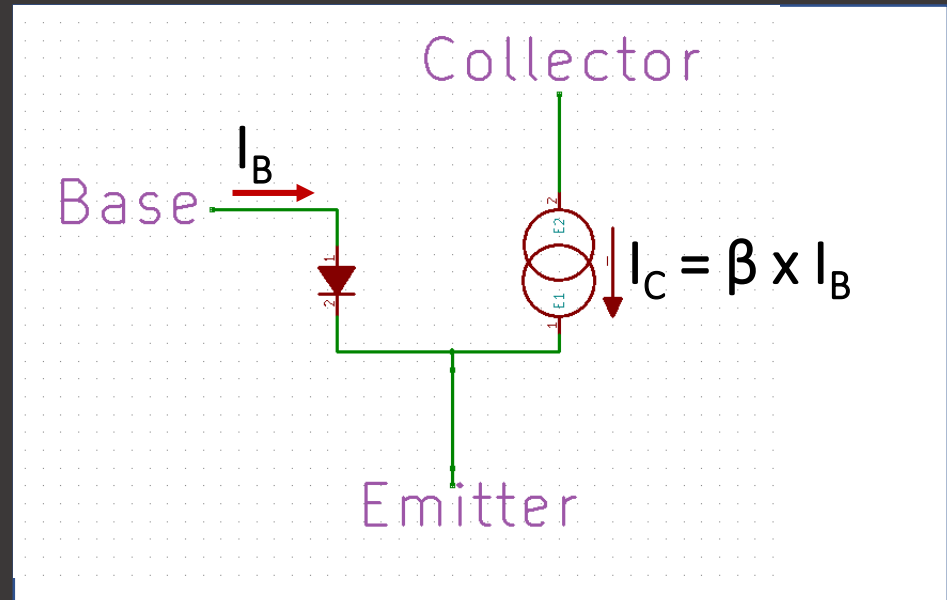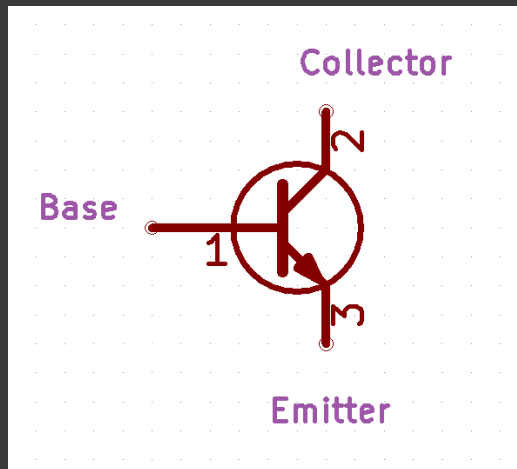


$\beta$  (aka  $h_{fe}$ ) is the “current gain” of the device


# A Bad Common Emitter Amplifier

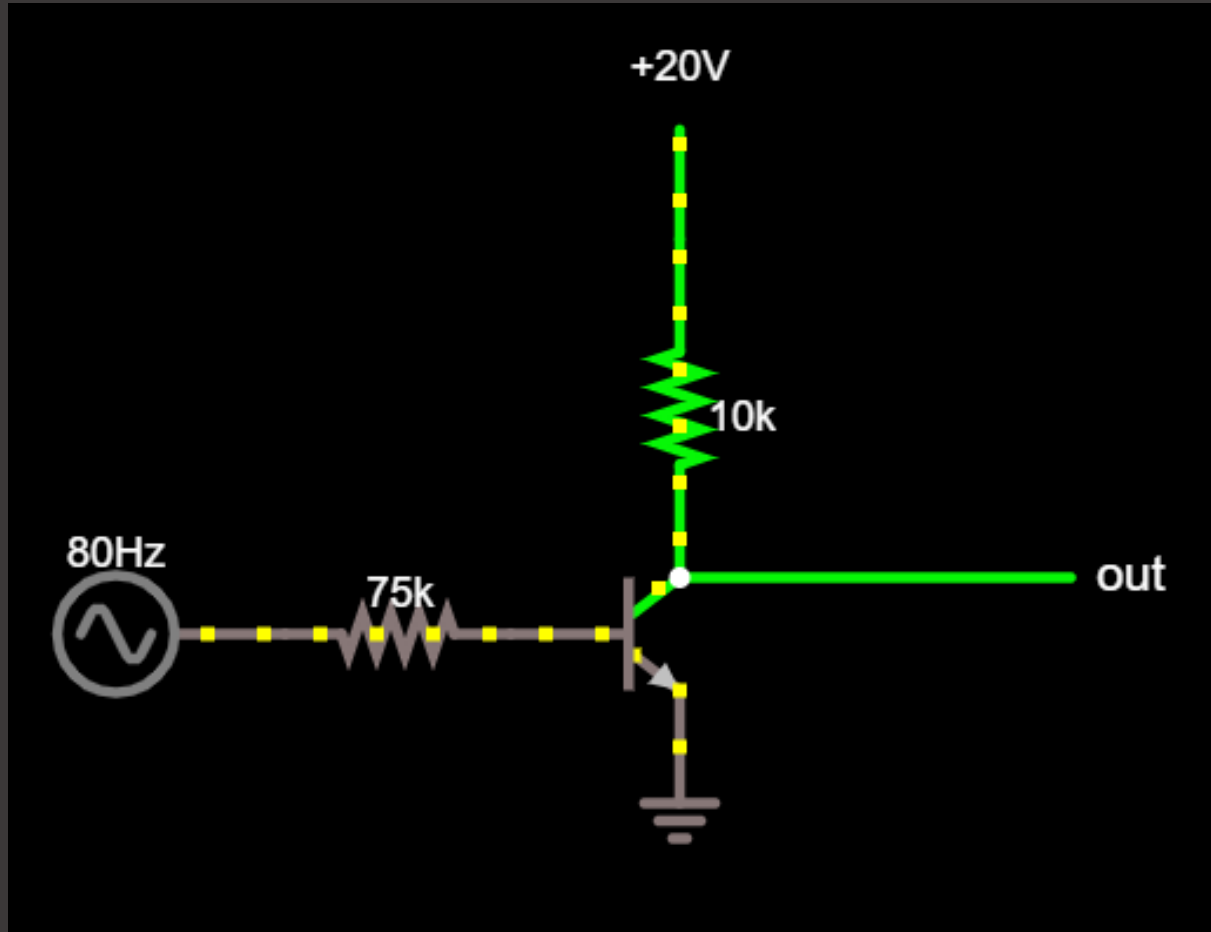

[http://falstad.com/circuit/circuitjs.html?cct=\\$+1+0.000005+16.13108636308289+60+15+53%0Ar+208+272+272+272+0+75000%0At+272+272+320+272+0+1+-18.713788175122275+0.528820044743417+100%0Ag+320+288+320+320+0%0AR+320+160+320+112+0+0+40+20+0+0+0.5%0Ar+320+160+320+256+0+10000%0AR+208+272+160+272+0+1+80+1+1+0+0.5%0AO+320+256+448+256+0%0Ao+5+32+0+4614+3.9999999999999996+0.0001+0+2+5+3%0Ao+6+32+0+4614+19.999999997799996+0.0001+0+1%0A](http://falstad.com/circuit/circuitjs.html?cct=$+1+0.000005+16.13108636308289+60+15+53%0Ar+208+272+272+272+0+75000%0At+272+272+320+272+0+1+-18.713788175122275+0.528820044743417+100%0Ag+320+288+320+320+0%0AR+320+160+320+112+0+0+40+20+0+0+0.5%0Ar+320+160+320+256+0+10000%0AR+208+272+160+272+0+1+80+1+1+0+0.5%0AO+320+256+448+256+0%0Ao+5+32+0+4614+3.9999999999999996+0.0001+0+2+5+3%0Ao+6+32+0+4614+19.999999997799996+0.0001+0+1%0A)

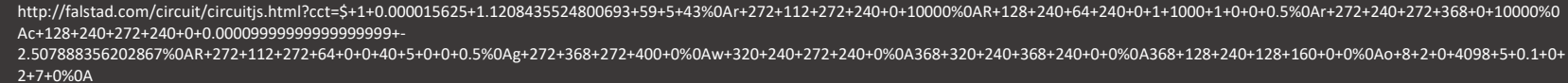


# A Mediocre CE Amplifier

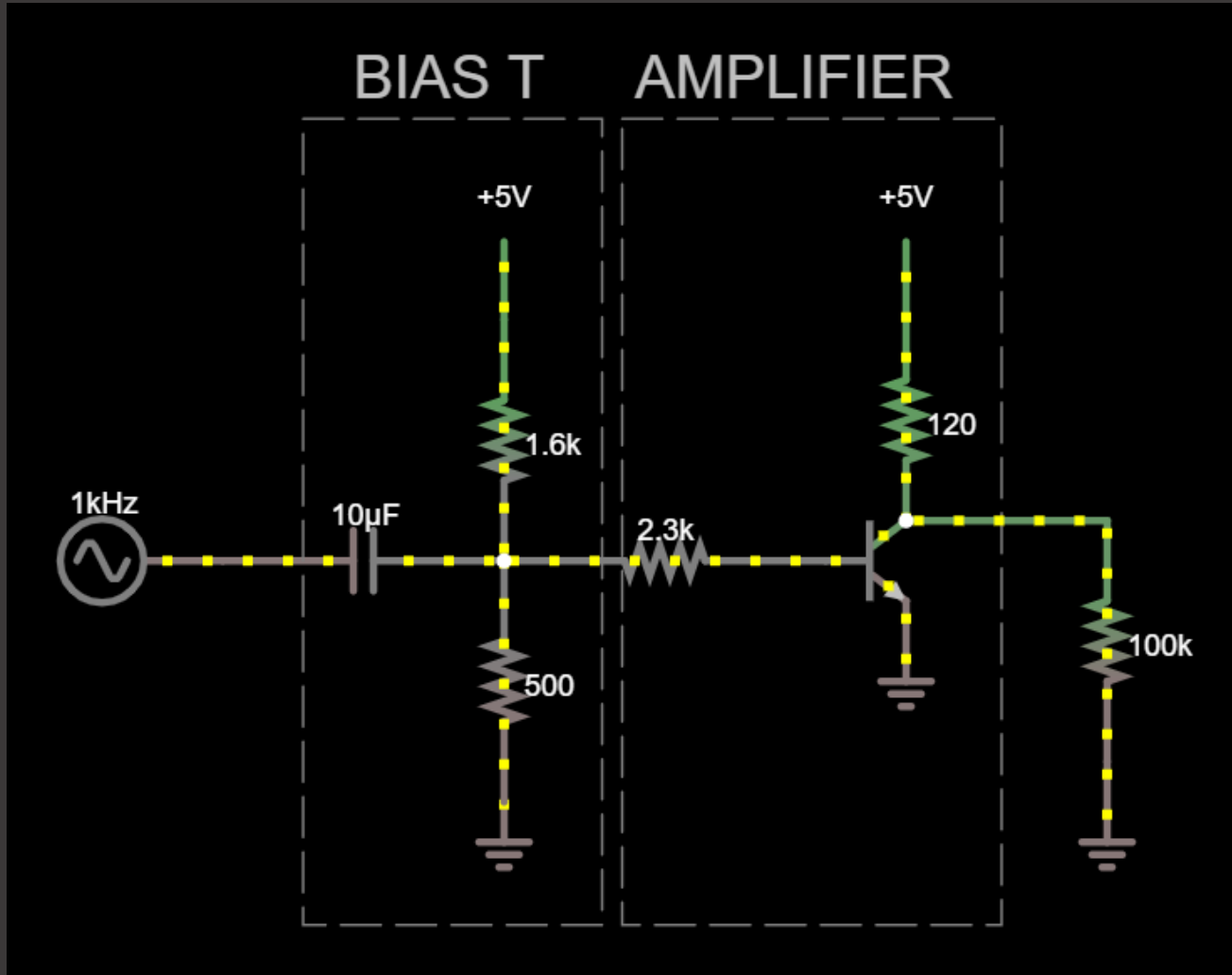

[http://falstad.com/circuit/circuitjs.html?cct=\\$+1+0.000005+1.5642631884188172+60+15+53%0Ag+176+320+176+336+0%0AR+176+128+176+80+0+0+40+5+0+0+0.5%0AR+176+128+176+224+0+1600%0AR+64+224+16+224+0+1+1000+0.5+0.5+0+0.5%0AR+176+224+176+320+0+500%0Ac+64+224+176+224+0+0.00001+-0.6202998006592448%0At+304+224+336+224+0+1+0.4226432803100168+0.6906075355751219+100%0AR+176+224+304+224+0+2300%0Ag+336+240+336+272+0%0AR+336+128+336+208+0+120%0AR+336+128+336+80+0+0+40+5+0+0+0.5%0Ax+116+40+192+43+4+24+BIAS%5CsT%0Ab+96+48+215+369+0%0Ab+223+48+374+369+0%0Ax+228+40+354+43+4+24+AMPLIFIER%0Aw+336+208+416+208+0%0AR+416+208+416+304+0+100000%0Ag+416+304+416+336+0%0Ao+3+2+0+20998+1.9999999999999999+0.0001+0+2+3+3%0Ao+15+2+0+20738+5+0.1+1+2+15+3%0A](http://falstad.com/circuit/circuitjs.html?cct=$+1+0.000005+1.5642631884188172+60+15+53%0Ag+176+320+176+336+0%0AR+176+128+176+80+0+0+40+5+0+0+0.5%0AR+176+128+176+224+0+1600%0AR+64+224+16+224+0+1+1000+0.5+0.5+0+0.5%0AR+176+224+176+320+0+500%0Ac+64+224+176+224+0+0.00001+-0.6202998006592448%0At+304+224+336+224+0+1+0.4226432803100168+0.6906075355751219+100%0AR+176+224+304+224+0+2300%0Ag+336+240+336+272+0%0AR+336+128+336+208+0+120%0AR+336+128+336+80+0+0+40+5+0+0+0.5%0Ax+116+40+192+43+4+24+BIAS%5CsT%0Ab+96+48+215+369+0%0Ab+223+48+374+369+0%0Ax+228+40+354+43+4+24+AMPLIFIER%0Aw+336+208+416+208+0%0AR+416+208+416+304+0+100000%0Ag+416+304+416+336+0%0Ao+3+2+0+20998+1.9999999999999999+0.0001+0+2+3+3%0Ao+15+2+0+20738+5+0.1+1+2+15+3%0A)


# Problems with this amplifier

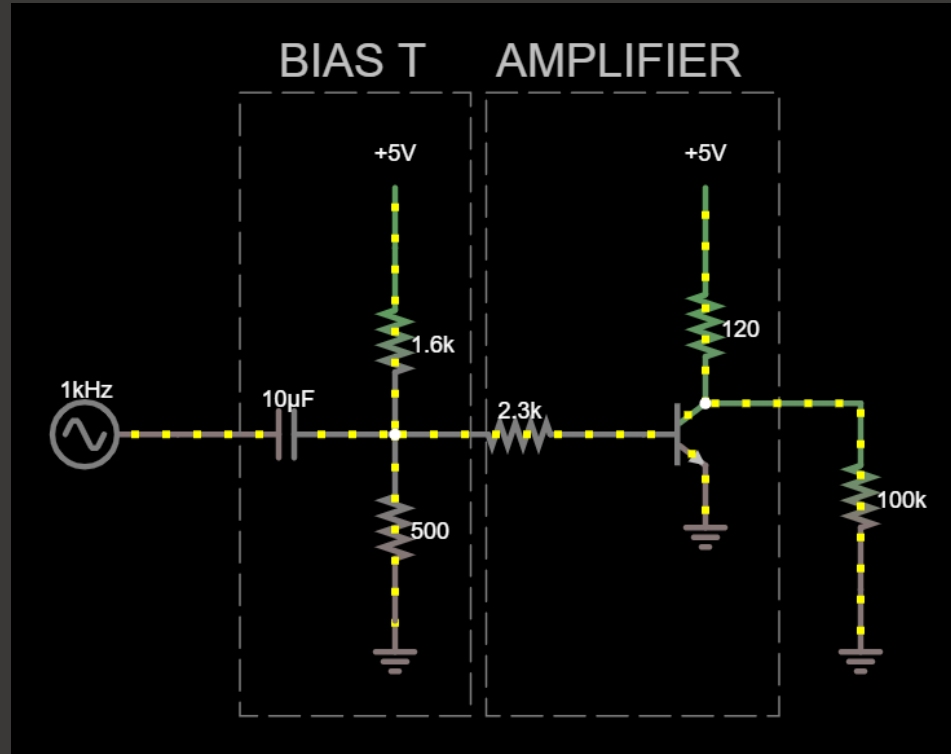

## Problems


- Gain will vary too much with  $\beta$  ( $h_{fe}$ ) variation
- Linearity isn't very good
- Input dynamic range is poor
- Circuit needs fine-tuning per transistor used

# Emitter Resistor

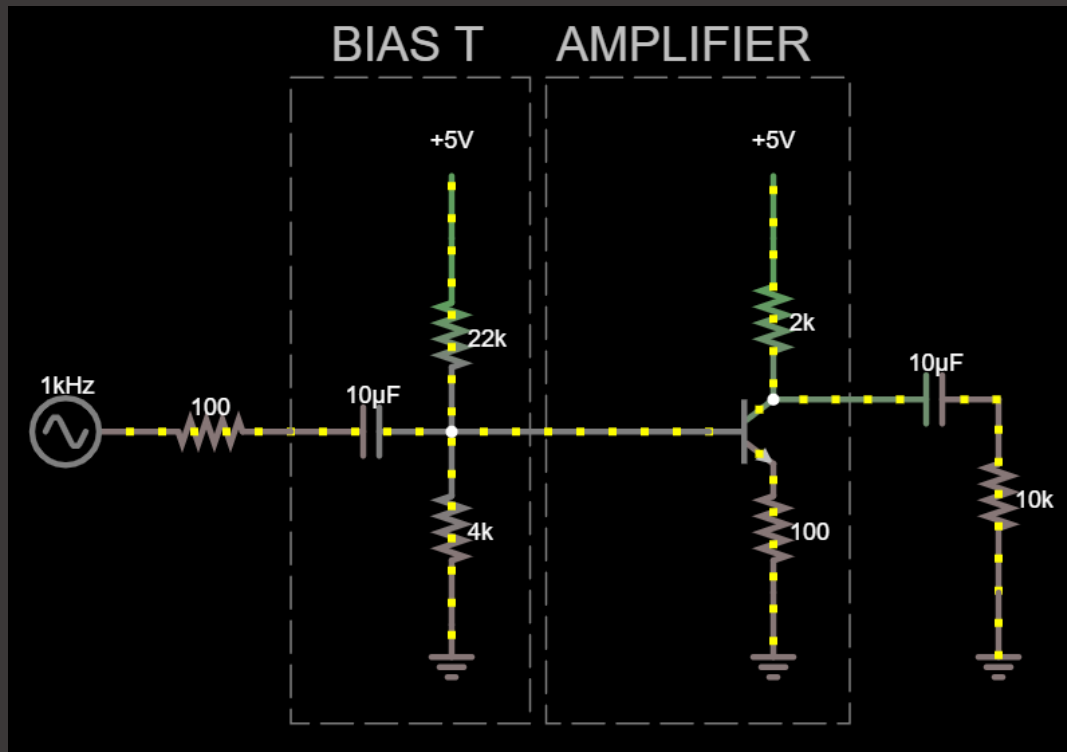


- Gain  $\sim -R_c/R_e$
- Improved distortion
- Improved dynamic range
- Less sensitive to individual transistor characteristics

# Example circuits


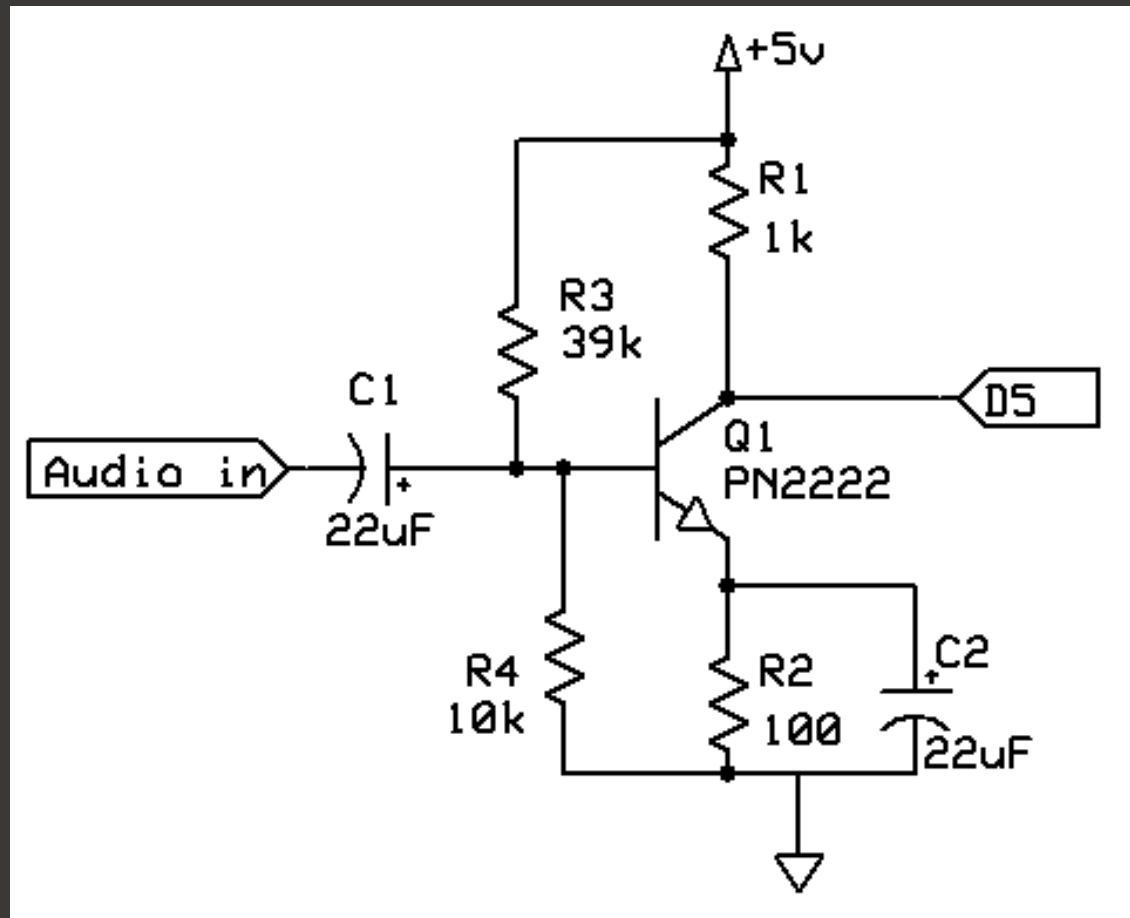






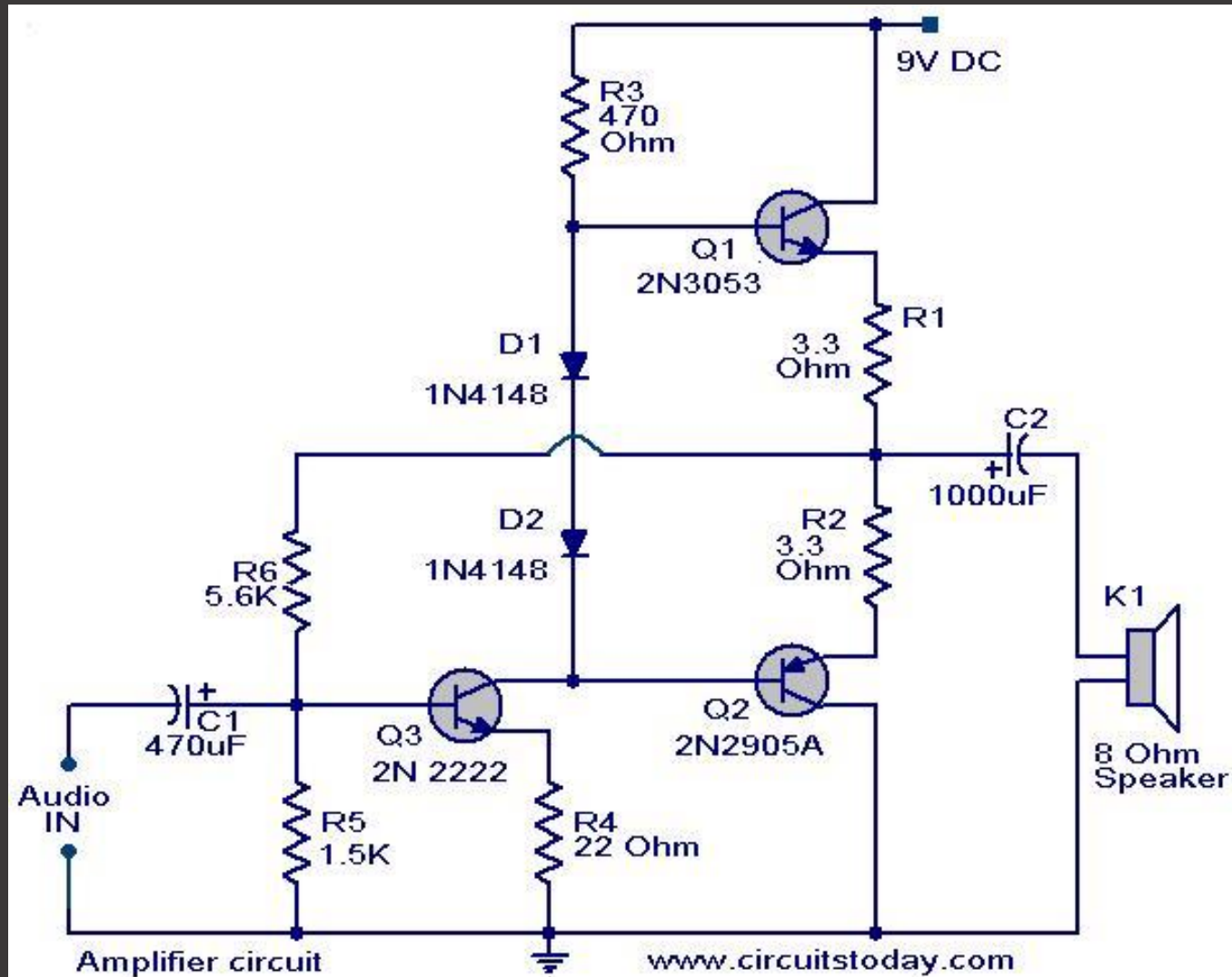



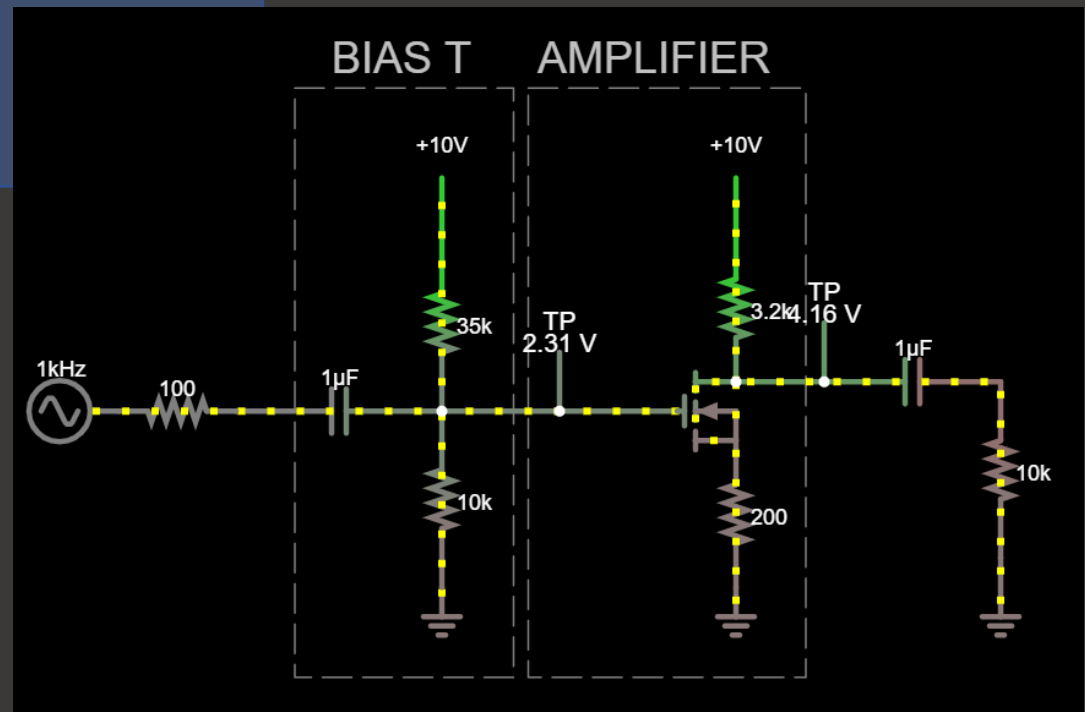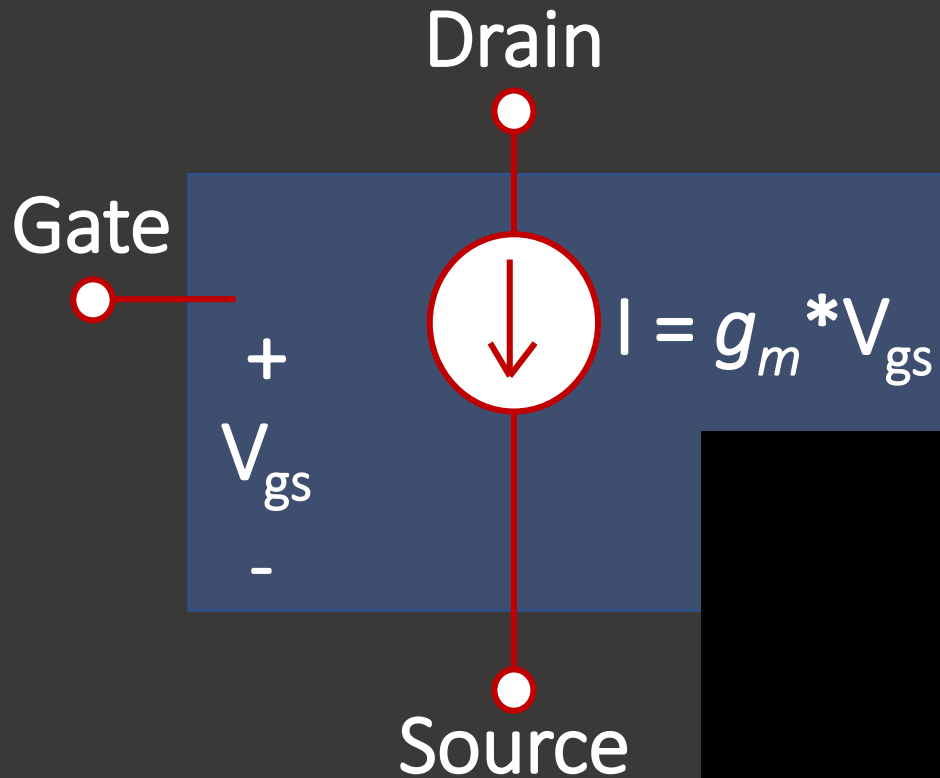



# Example circuits



# A more accurate FET model



# FETs vs BJT – Which is best?

Questionable generalizations!	Bipolar (BJT)	FET (MOSFET)
Speed		
Gate/base current		
On-state voltage drop		
Low voltage circuits, esp when controlling high current		
Ease of selection/application	(?) 	(?) 

Practical guidance/tendencies:

- Low power, low voltage -> bipolar
- High current -> FET
- High efficiency switching supplies -> FET

# Go-to Transistors

---

Bipolar – the workhorse for enthusiasts

- 2N3904 – NPN, 40V, 200mA, 300MHz  $f_T$
- 2N3906 – PNP, -40V, 200mA, 250MHz  $f_T$
- TIP120 – NPN, 60V, 5A



## MOSFETs

- Probably don't want to stock FETs
- Wanna play? 2N7000, 2N7002 - NMOS