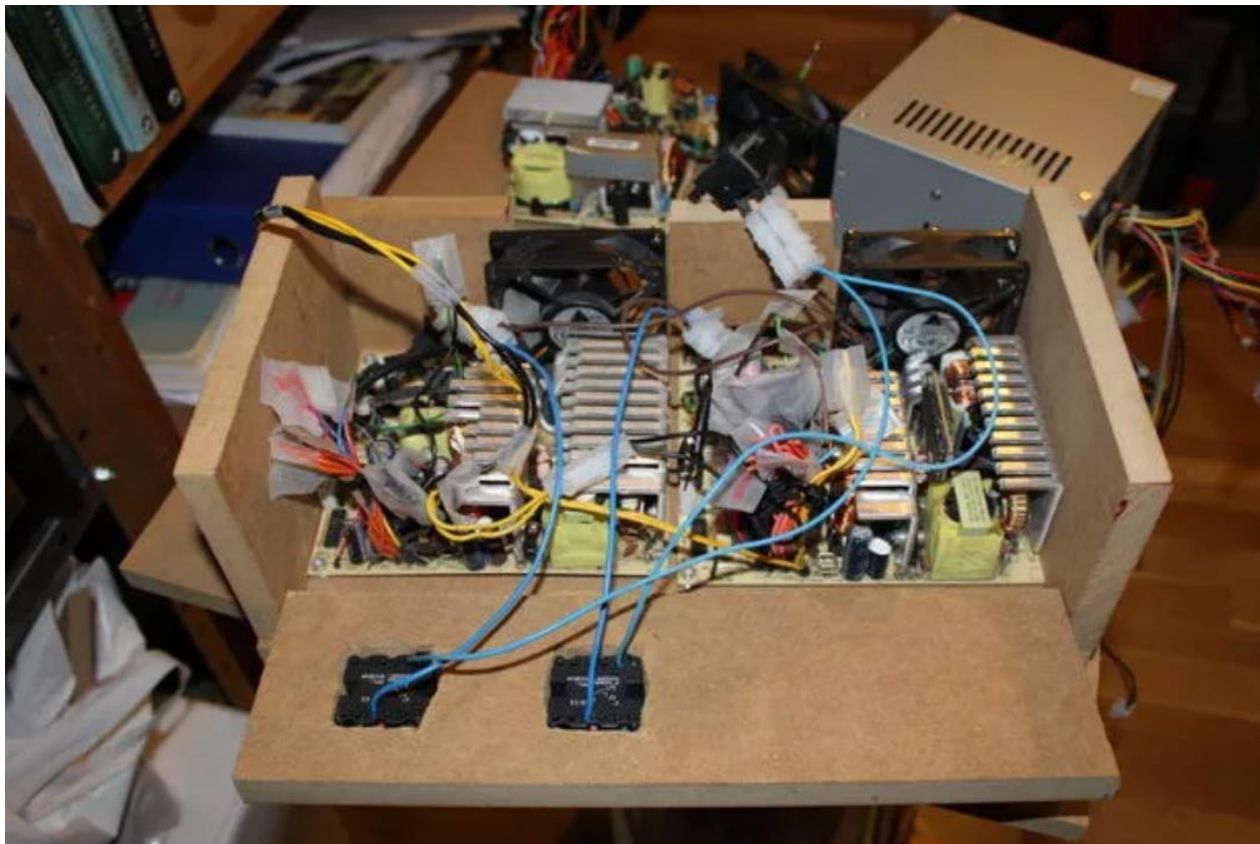


Power Supplies 101

AC-DC Converters

3-Feb-2018



WARNING

WARNING

WARNING

WARNING

WARNING

Rules of thumb, assumptions and mixed-quality analogies to come!



BAD ANALOGIES

**JUST BECAUSE ONE ARGUMENT RESEMBLES ANOTHER,
DOESN'T MEAN THAT CATS CAN FLY IN SPACE.**

Tonight's Agenda AC-DC Supplies

Tonight's theory will help you understand:

- Classical AC-DC linear supplies
 - How they work
 - Component selection, supply design
- Switch mode AC-DC linear supplies
 - How they work at a very high level
- Switching vs linear trade-offs

Tonight's lab:

- Power up a switch mode AC-DC supply
- Build a linear AC-DC power supply
- Use an oscilloscope to measure AC and DC waveforms
- Measure load regulation

Next week:

- How regulation loops work
- More detail on how switch mode supplies work
- How 3-terminal linear regulators work and wire some up
- Use some DC-DC switching supplies


Voltage, Current and Power Supplies

A power supply provides a constant voltage to its load at all times


- Voltage rating of supply must be equal to what the load requires
- If the load needs 5V then the supply must be rated at 5V

The load draws however much current it needs, this varies with time

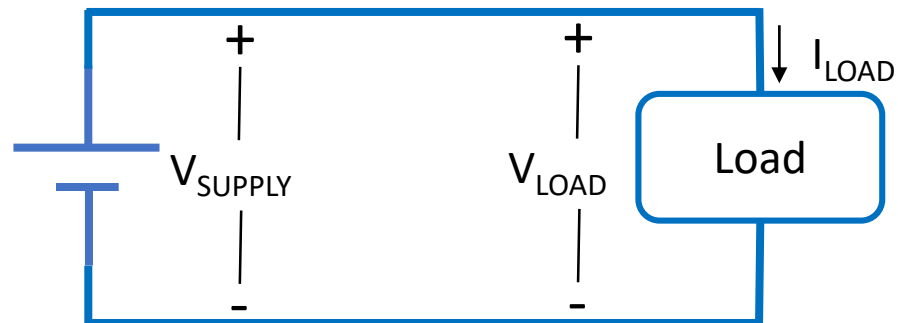- An audio amp draws more current when a loud signal is being played than when a quiet signal is being played
- A blinking LED circuit draws more current when the LED is illuminated
- Supply current rating must be larger than or equal to what the load needs. A 1 million amp power supply will work with a load that only needs 1 amp




Classic AC to DC Linear Supply

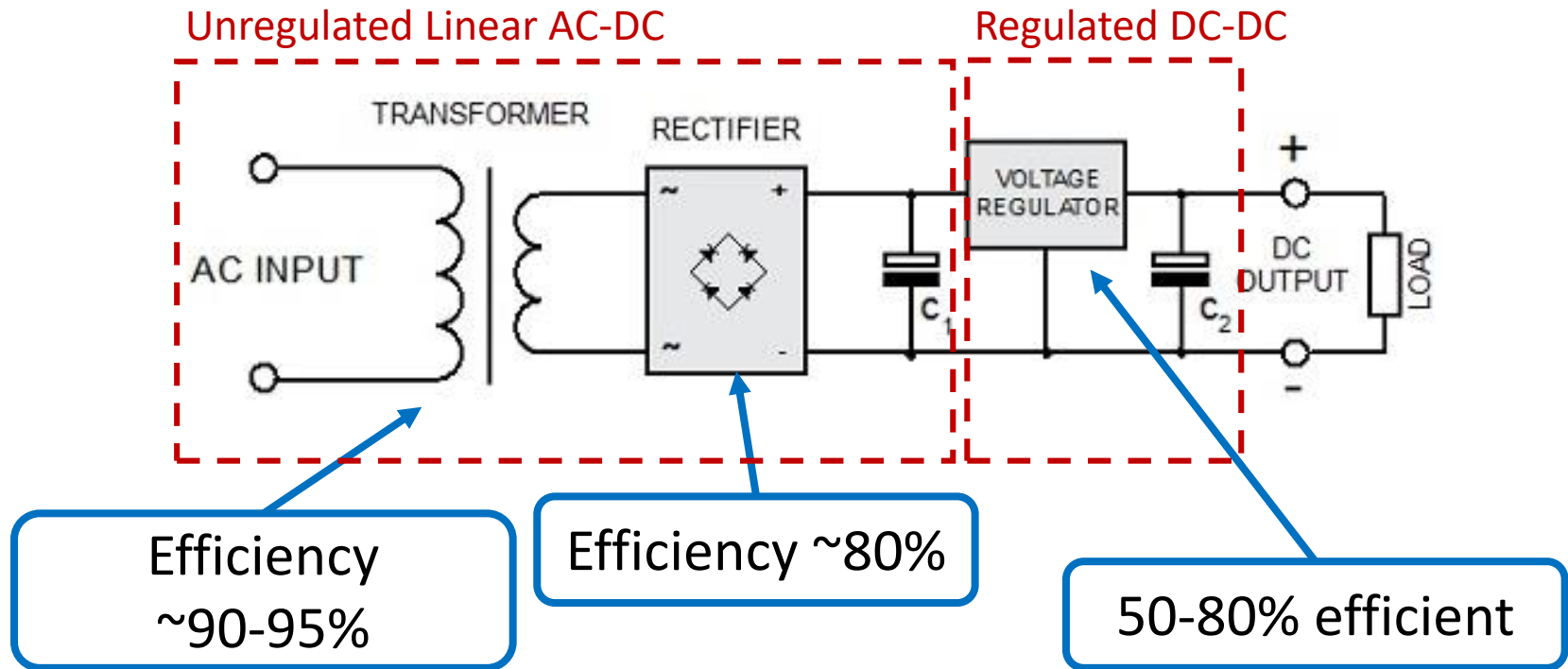

- An unregulated linear AC-DC supply is fairly efficient, 75%
- An unregulated linear AC-DC supply might be a fast off-the-shelf option
- A regulated linear AC-DC supply is typically 40-60% efficient

How does an unregulated linear work?

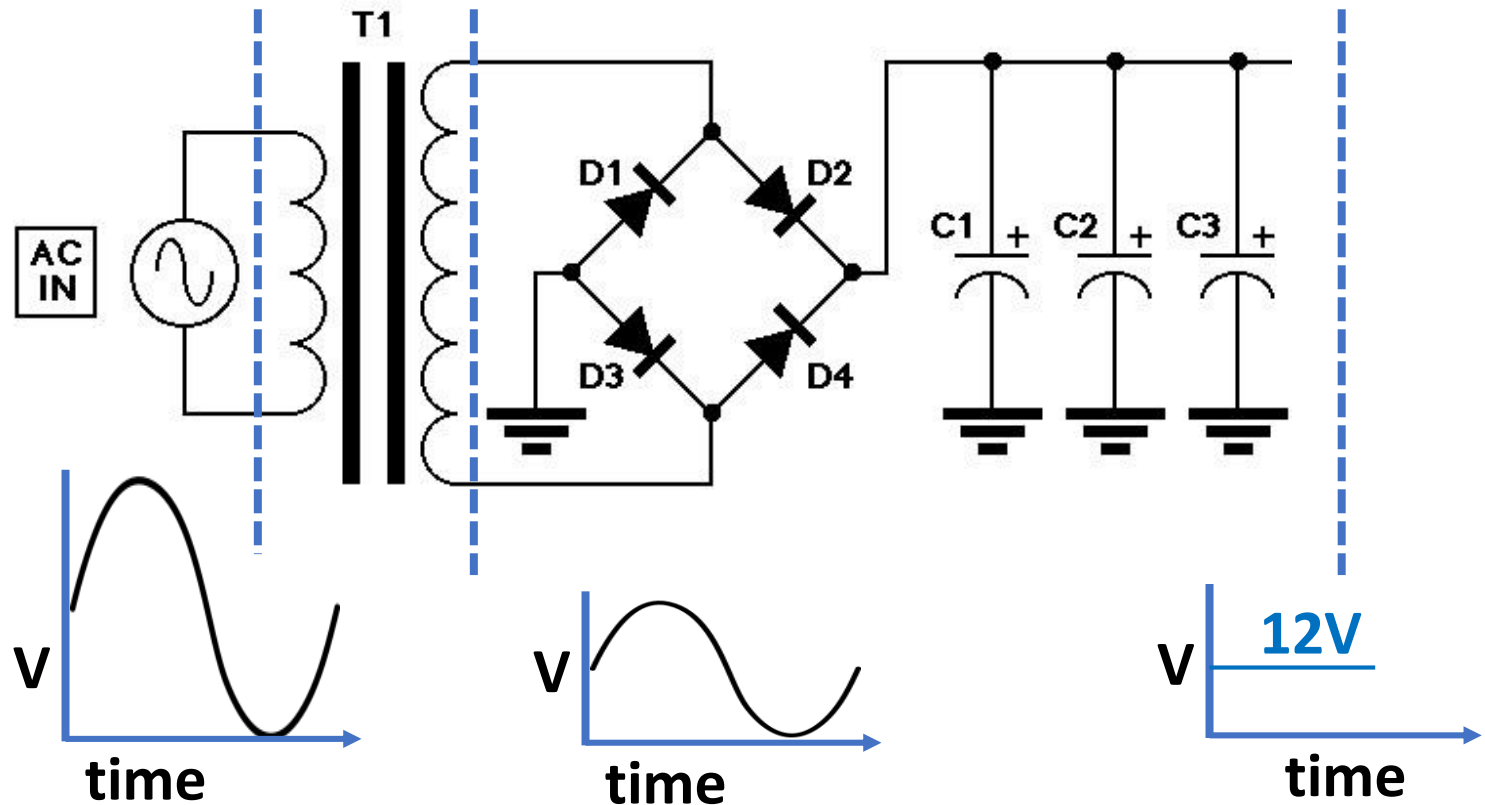


120VAC RMS
170V peak
340V peak-peak


12VAC RMS
17V peak
34V peak-peak

~16VDC no load
~11V full load
~30% drop is typical

Unregulated vs regulated behavior

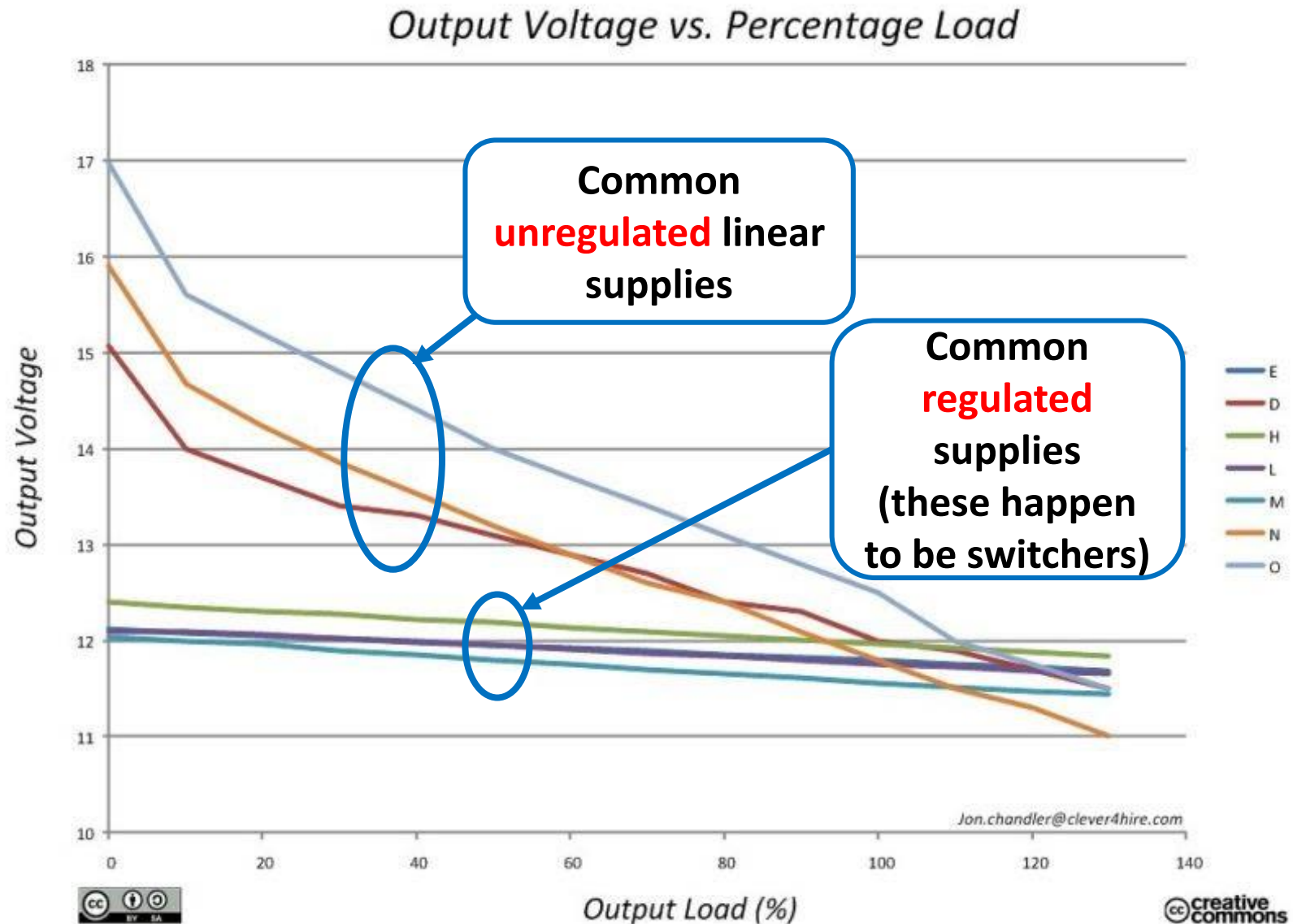

Bypass/Decoupling Capacitors

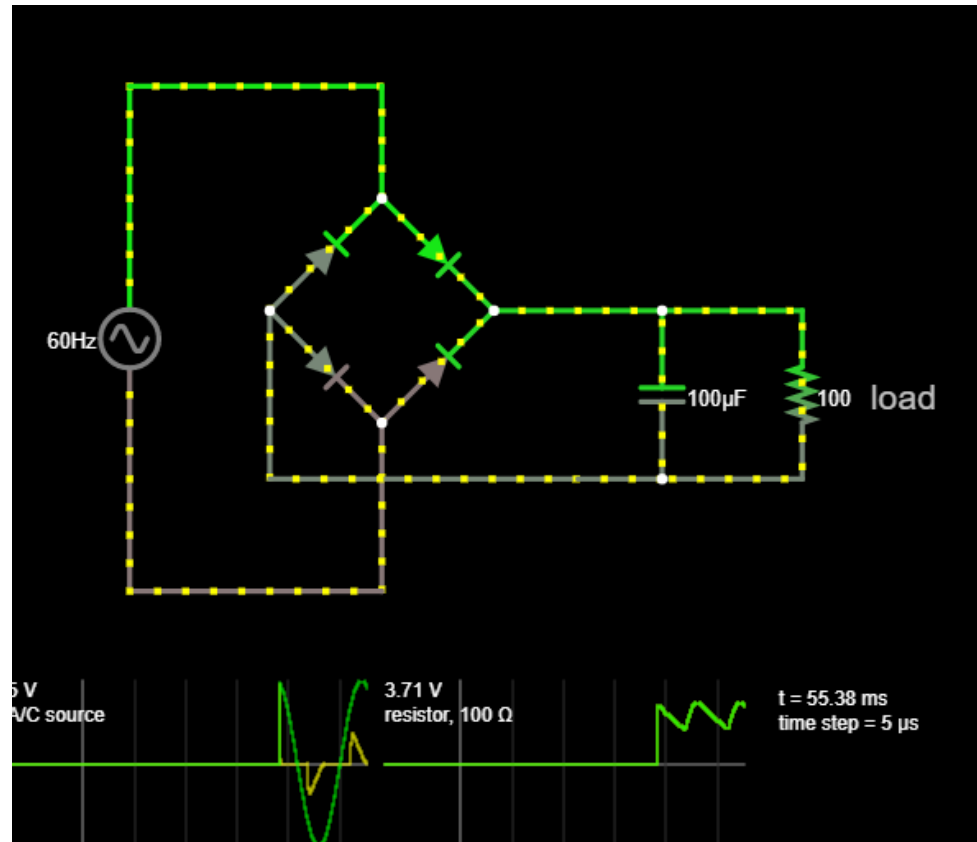

See simulations

Component Selection

Transformer:

- Primary voltage = Wall voltage
- Secondary voltage = $V_{DC} \times 1.1 + 5.2$
- Secondary current = $I_{DC} \times 1.8$
- Volt Amp rating = $V_{DC} \times I_{DC}$

Rectifier diodes:

- Peak Inverse Voltage > 2.5x transformer's rated secondary
- Maximum average current rating > 2x the DC current required

Filter capacitors

- $C \sim I_{DC} / (60 \times V_{RIPPLE})$
- or $C \sim I_{DC} / 100$ for 1.6V ripple

120VAC to 5V 1A DC supply:

Transformer:

- • 120V
- • $5V \times 1.1 + 5.2 = 10.9V \rightarrow 12V$
- • $1A \times 1.8 = 1.8A$
- • $10.9V \times 1.8A = 19.6VA$

Rectifier diodes:

- • $12V \times 2.5 = 30V$
- • $1A \times 2 = 2A$

Filter capacitors:

- • $1A / 100 = 0.01F$ or $10,000\mu F$

Workhorse Components

Transformers:

- Scavenge from old electronics, wall warts, ebay
- Tend to be expensive to buy new.

Diodes:


- 1N400x family

MAXIMUM RATINGS (T _A = 25 °C unless otherwise noted)										
PARAMETER	SYMBOL	1N4001	1N4002	1N4003	1N4004	1N4005	1N4006	1N4007	UNIT	
Maximum repetitive peak reverse voltage	V _{RRM}	50	100	200	400	600	800	1000	V	
Maximum RMS voltage	V _{RMS}	35	70	140	280	420	560	700	V	
Maximum DC blocking voltage	V _{DC}	50	100	200	400	600	800	1000	V	
Maximum average forward rectified current 0.375" (9.5 mm) lead length at T _A = 75 °C	I _{F(AV)}	1.0							A	
Peak forward surge current 8.3 ms single half sine-wave superimposed on rated load	I _{FSM}	30							A	
Non-repetitive peak forward surge current square waveform T _A = 25 °C (fig. 3)	t _p = 1 ms	I _{FSM}	45							A
	t _p = 2 ms		35							
	t _p = 5 ms		30							


Capacitors

- Will be electrolytic type to achieve required large value of capacitance
- Can scavenge but be wary of older parts, electrolytics degrade over time
- A small cap, 0.1uF or so is sometimes used to filter high frequency noise

AC-DC Switch Mode Supply

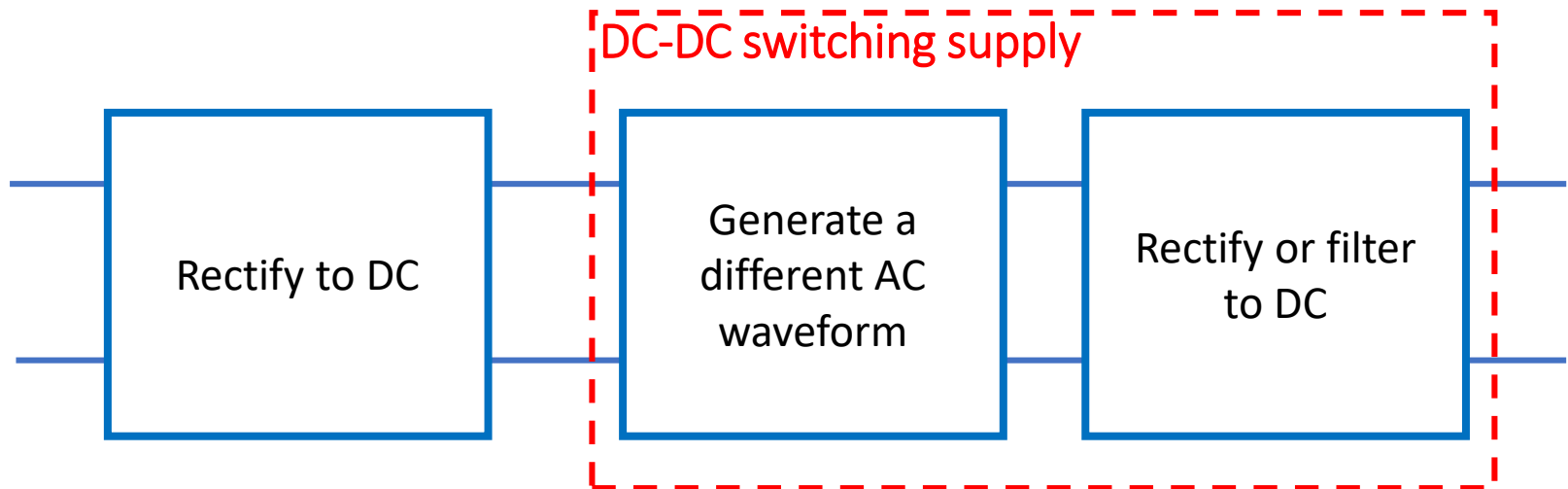

A little more detailed view

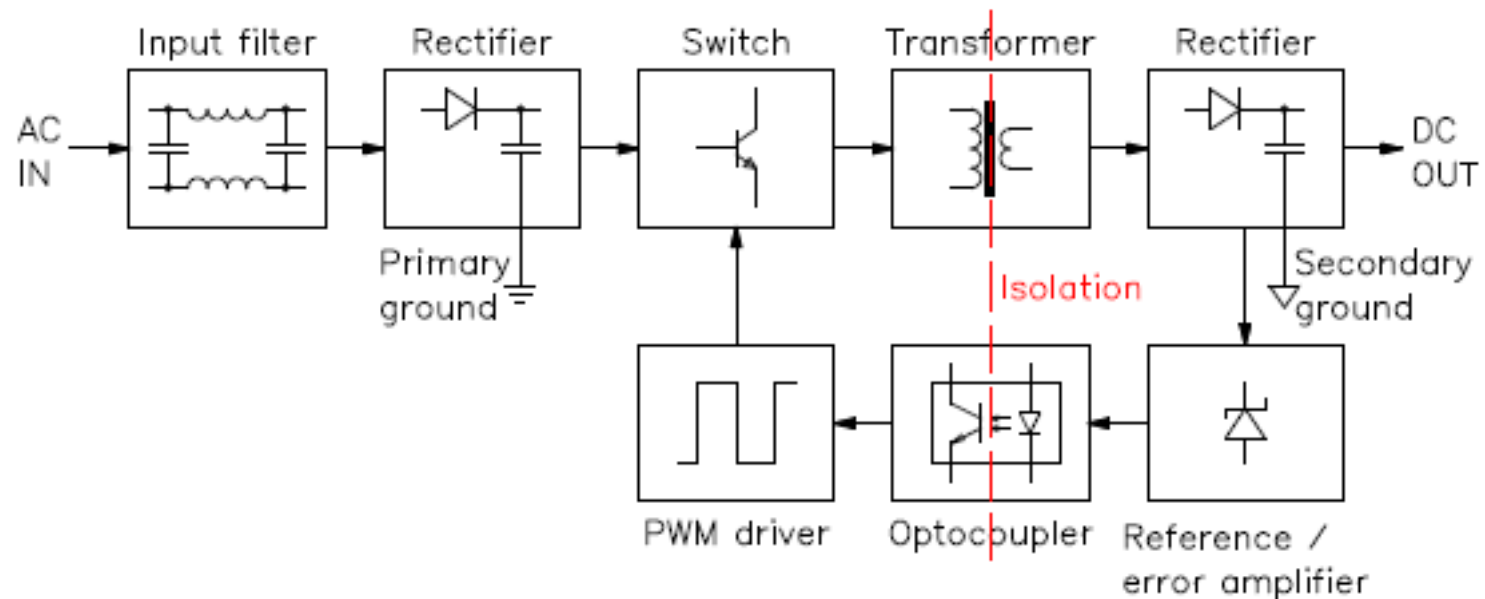

AC-DC type, 2.5A class linear vs switching supplies

	Why Build	Why Use Off the Shelf
Switching (Regulated)	<ul style="list-style-type: none">• “I want to learn about AC-DC switching supplies”• A big project in its own right• >\$20	<ul style="list-style-type: none">• “I just want power”• Small• Easy• Efficient• \$10
Linear Regulated	<ul style="list-style-type: none">• “I want to learn about AC-DC linear supplies”• “I have the parts laying around”• Free to \$20	<ul style="list-style-type: none">• “I already have one”• “Switchers are noisy”• Hard to find• Free - \$50?
Linear Unregulated	<ul style="list-style-type: none">• “I want to learn about AC-DC supplies”• “I have the parts laying around”• Don’t care that output voltage varies a lot (e.g. 11-17V)• Free to \$20	<ul style="list-style-type: none">• “I already have one”• “Switchers are noisy”• Some wall warts• Free - \$10