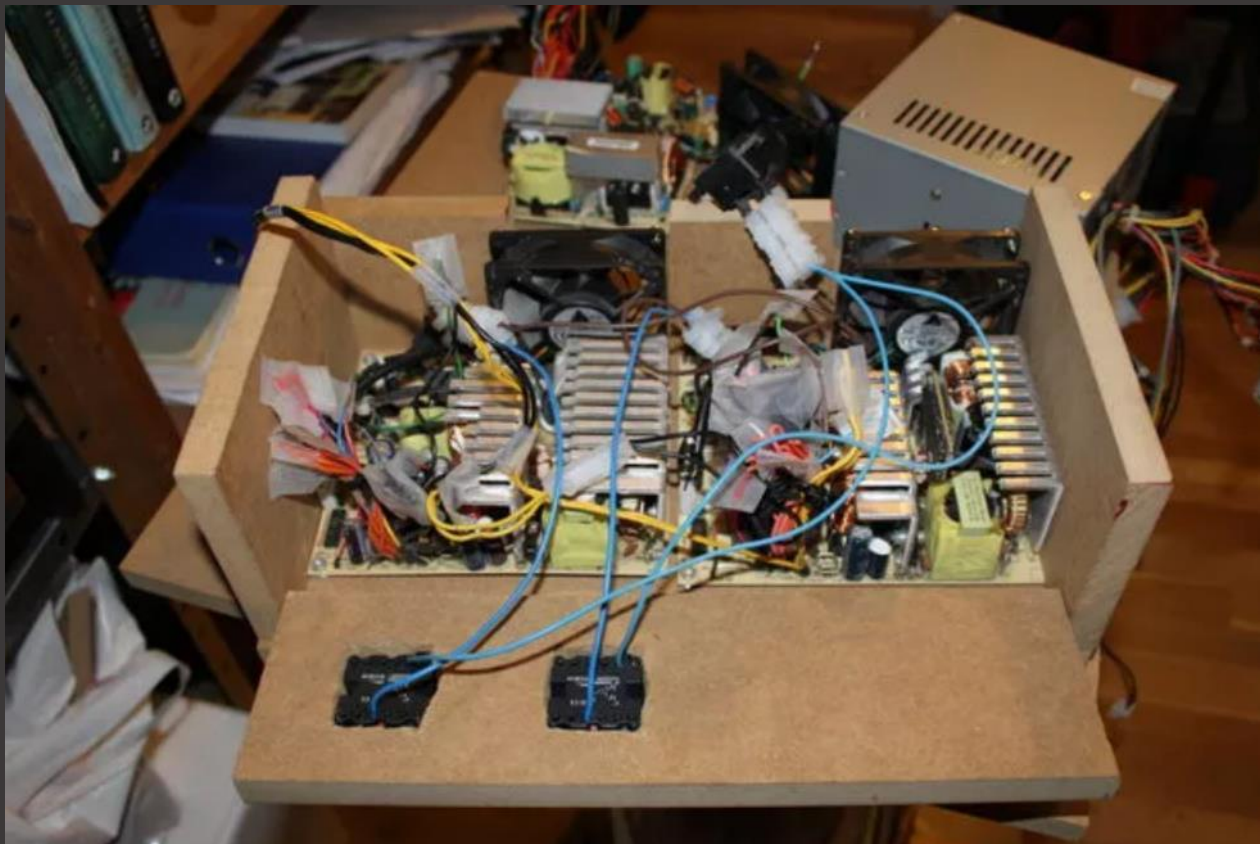


# Basic Electronics Components

Feb-2019



**WARNING**

**WARNING**

**WARNING**

**WARNING**

**WARNING**

**Rules of thumb, assumptions and mixed-quality analogies to come!**



# BAD ANALOGIES

**JUST BECAUSE ONE ARGUMENT RESEMBLES ANOTHER,  
DOESN'T MEAN THAT CATS CAN FLY IN SPACE.**



# Plumbing Analogy

---






# Voltage

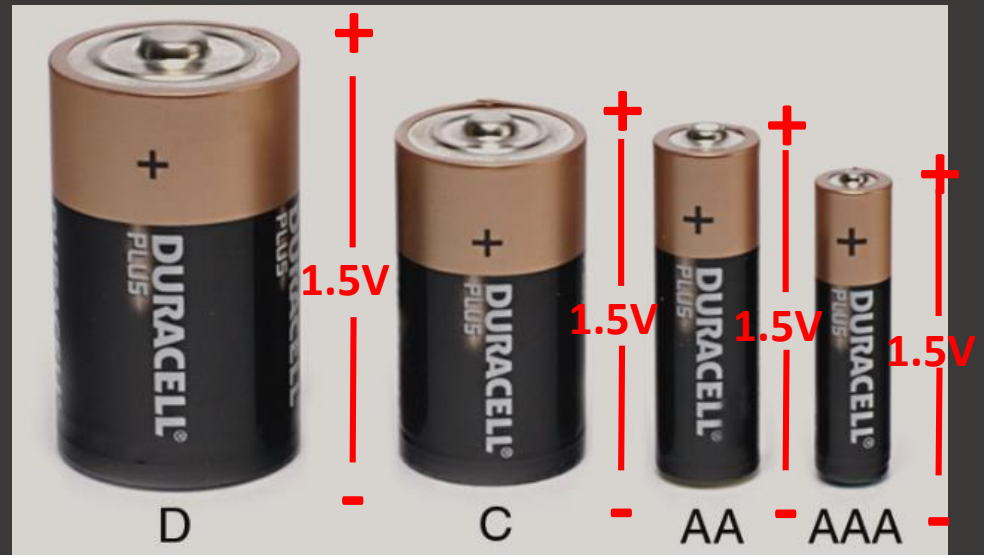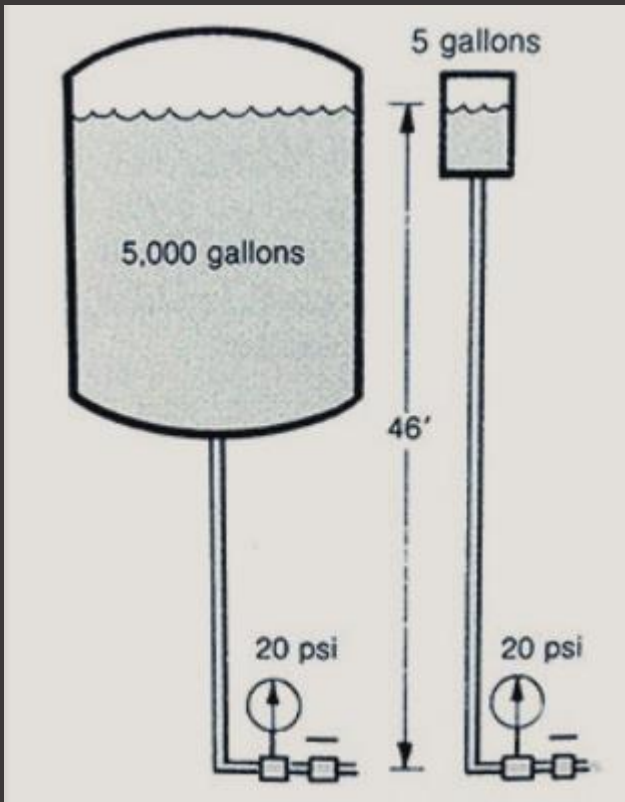


# Powering a Light Bulb

---

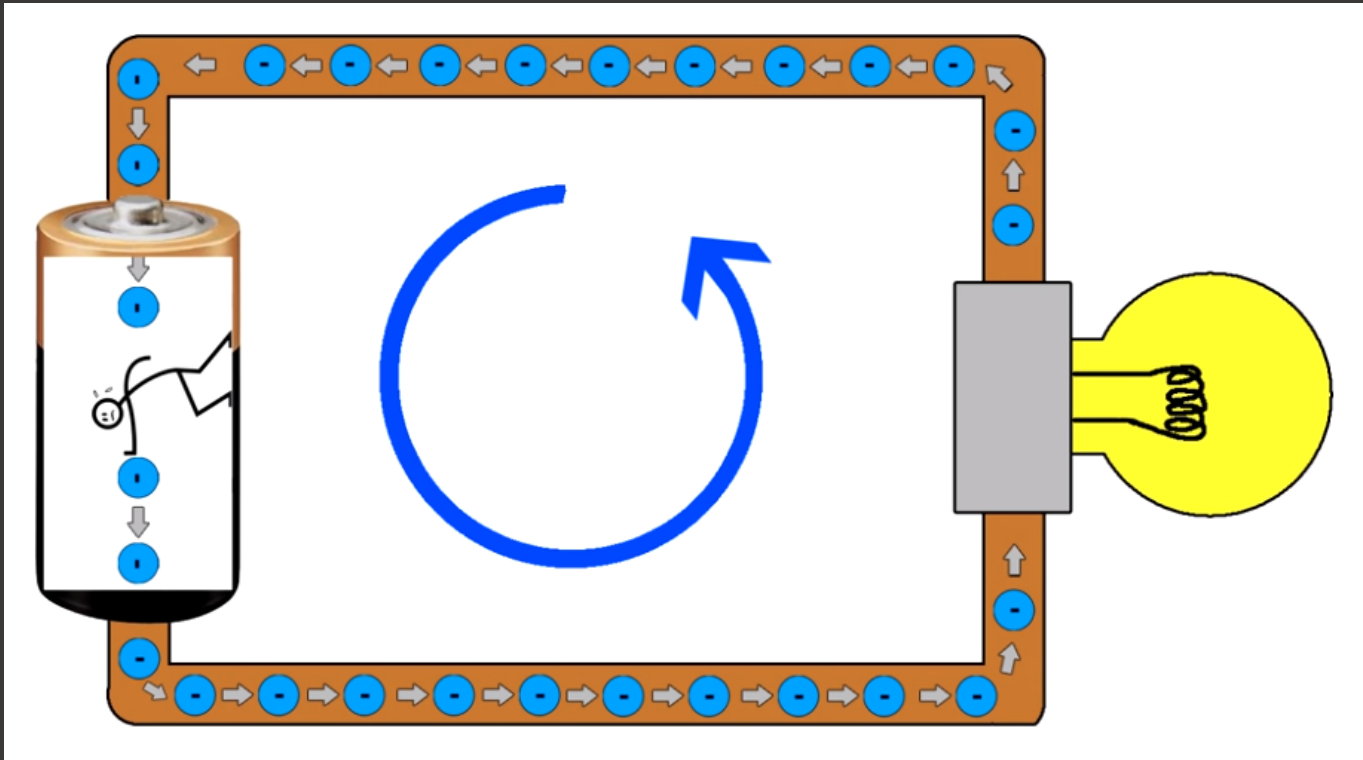

Voltage is the pushing force  
Pushes electrons through a circuit



# Powering a Complex Circuit

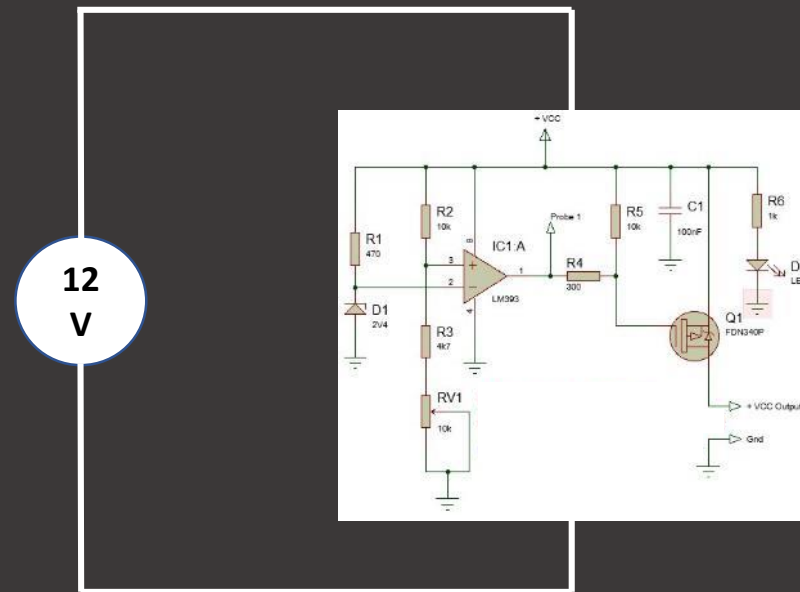

Voltage is applied across any circuit to power it
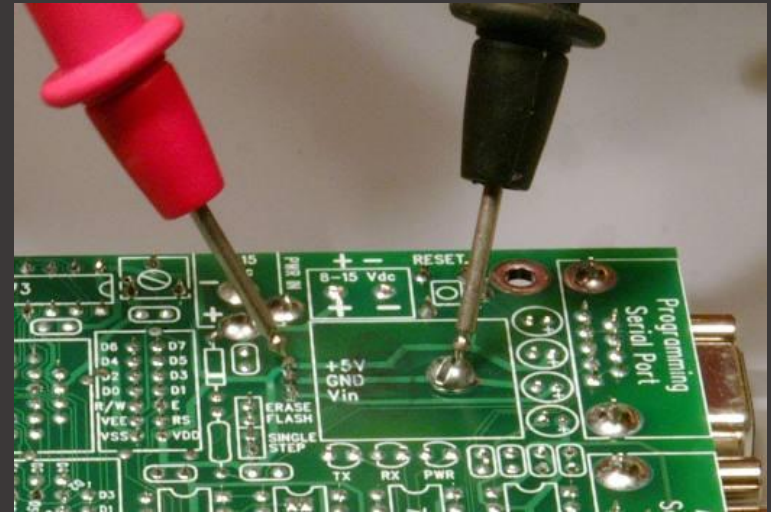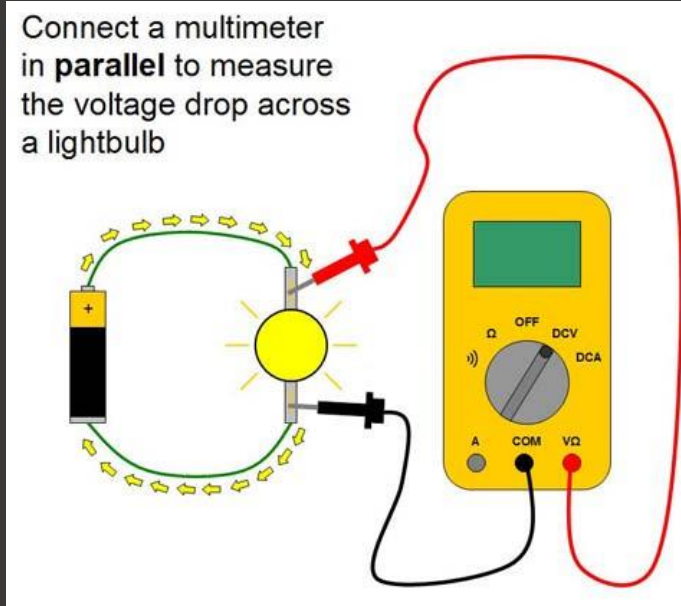
# Measuring Voltage

Connect a multimeter in **parallel** to measure the voltage drop across a lightbulb




Voltage is measured between two points:

- Common (reference, ground)
- Positive

# Current



---

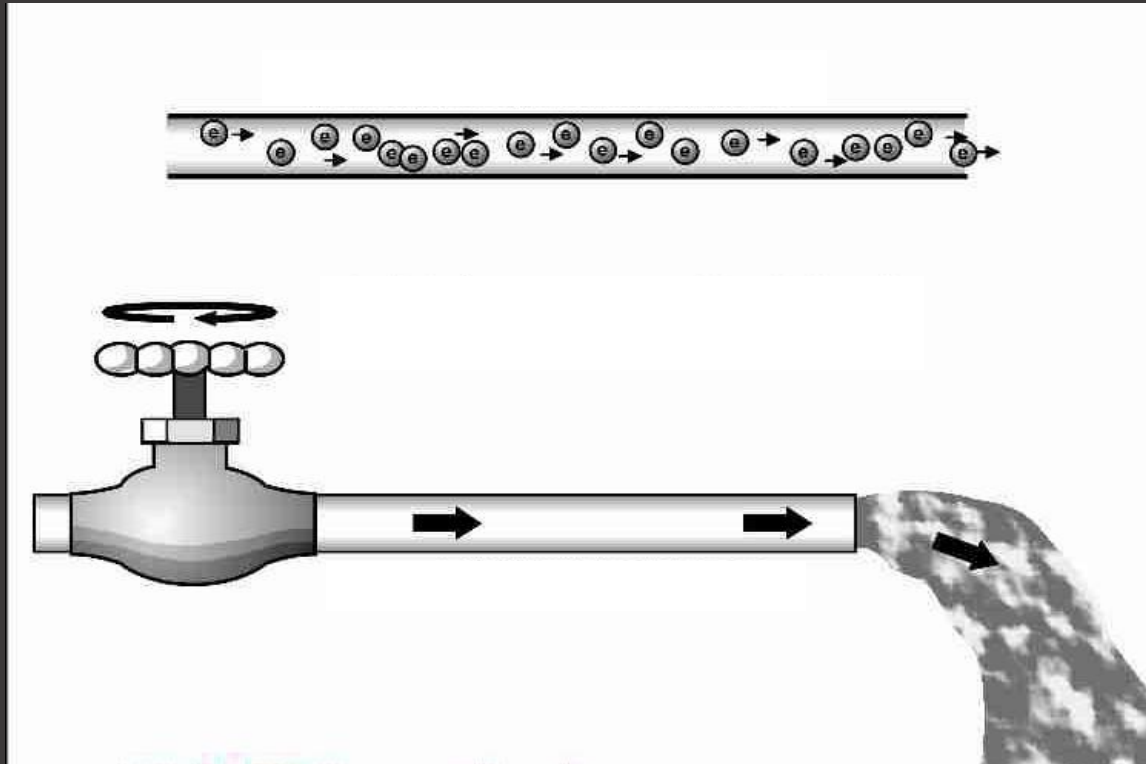

Current is the flow of electrons  
Similar to the flow of water



# Current

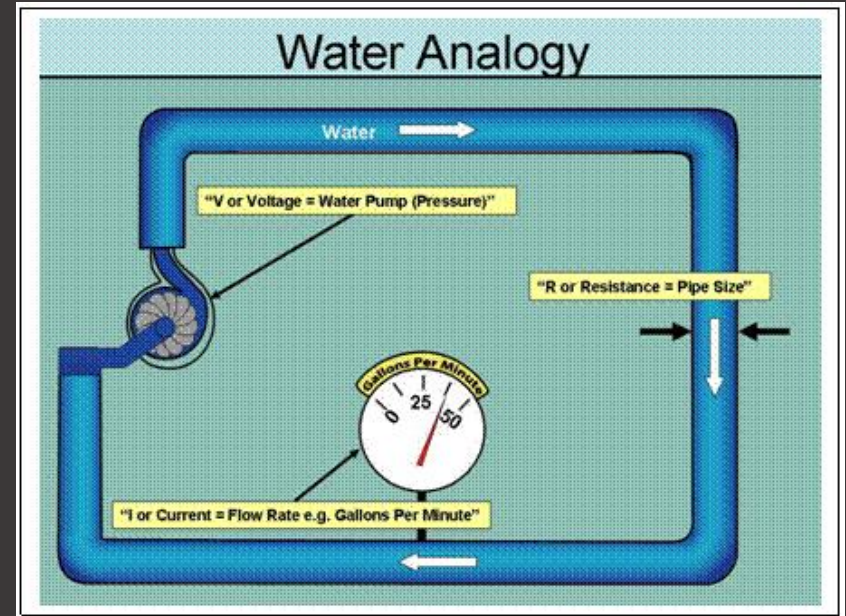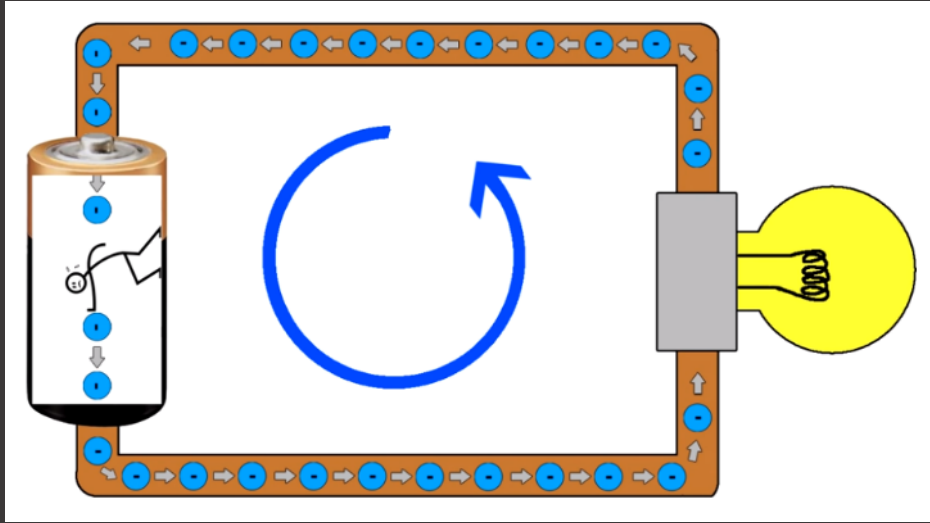


Measured in amps

1A (1 amp) =  $6.25 \times 10^{18}$  electrons per second


# Measuring Current

---

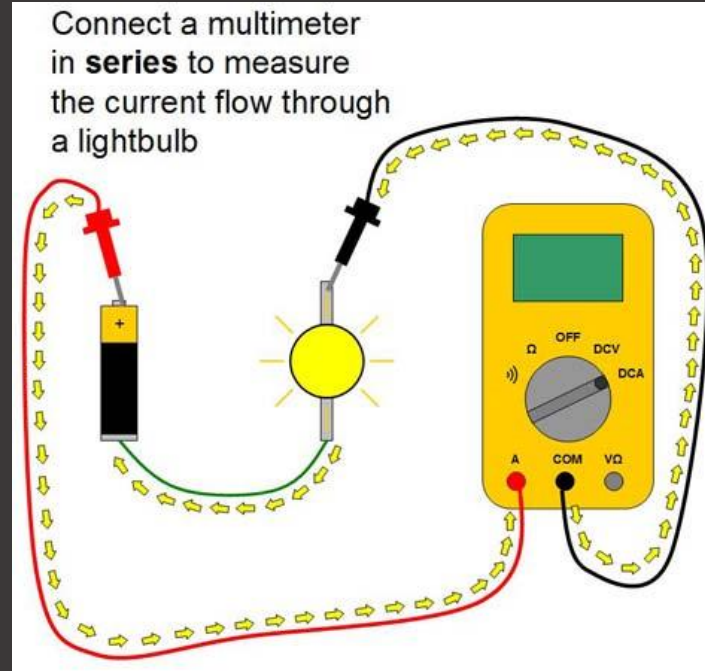


Current can be measured by passing it through a multimeter

# Power

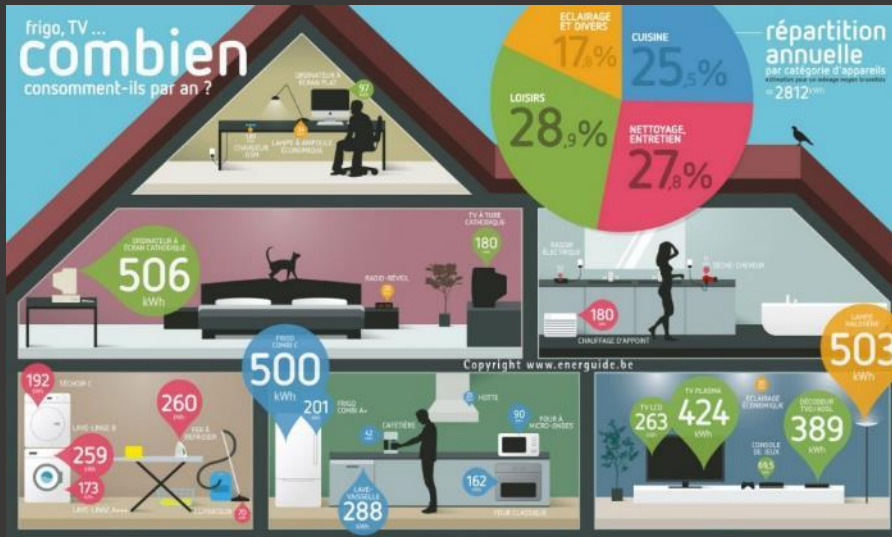

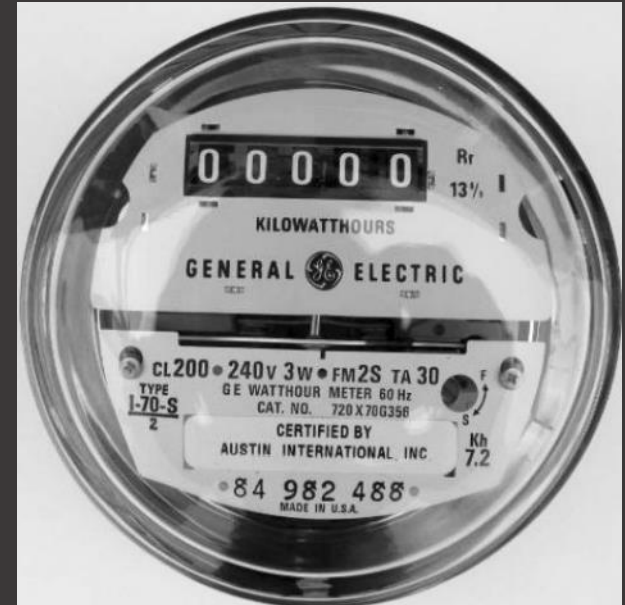Power = Watts =  
Amount of energy  
used at a particular  
point in time




Energy =  
Power x Time = W x hr  
Total energy a house  
uses in a month

# Calculating Power

---

Power = Voltage x Current

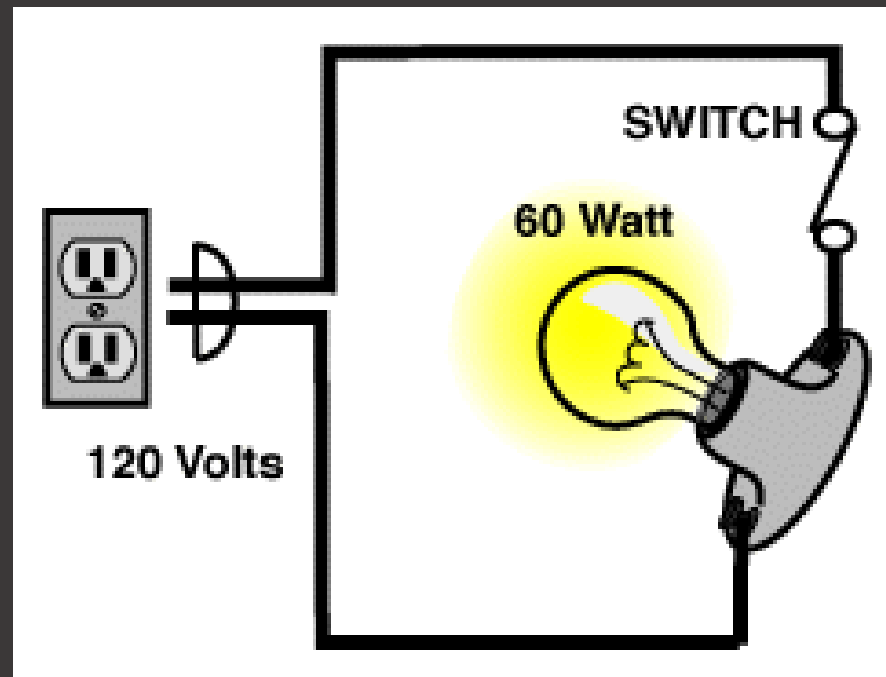

$$120V \times 0.5A = 60W$$

# Resistors – A minute to learn, a lifetime to master


---






# We use them every day

---

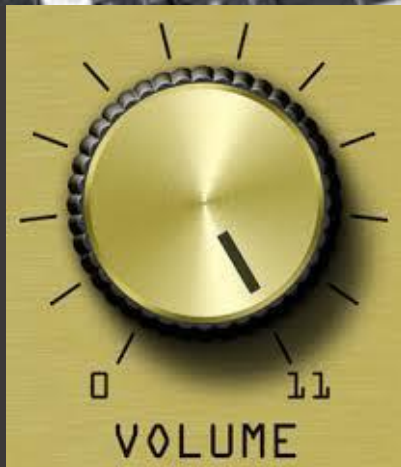

# Resistors – Resist the flow of current

---

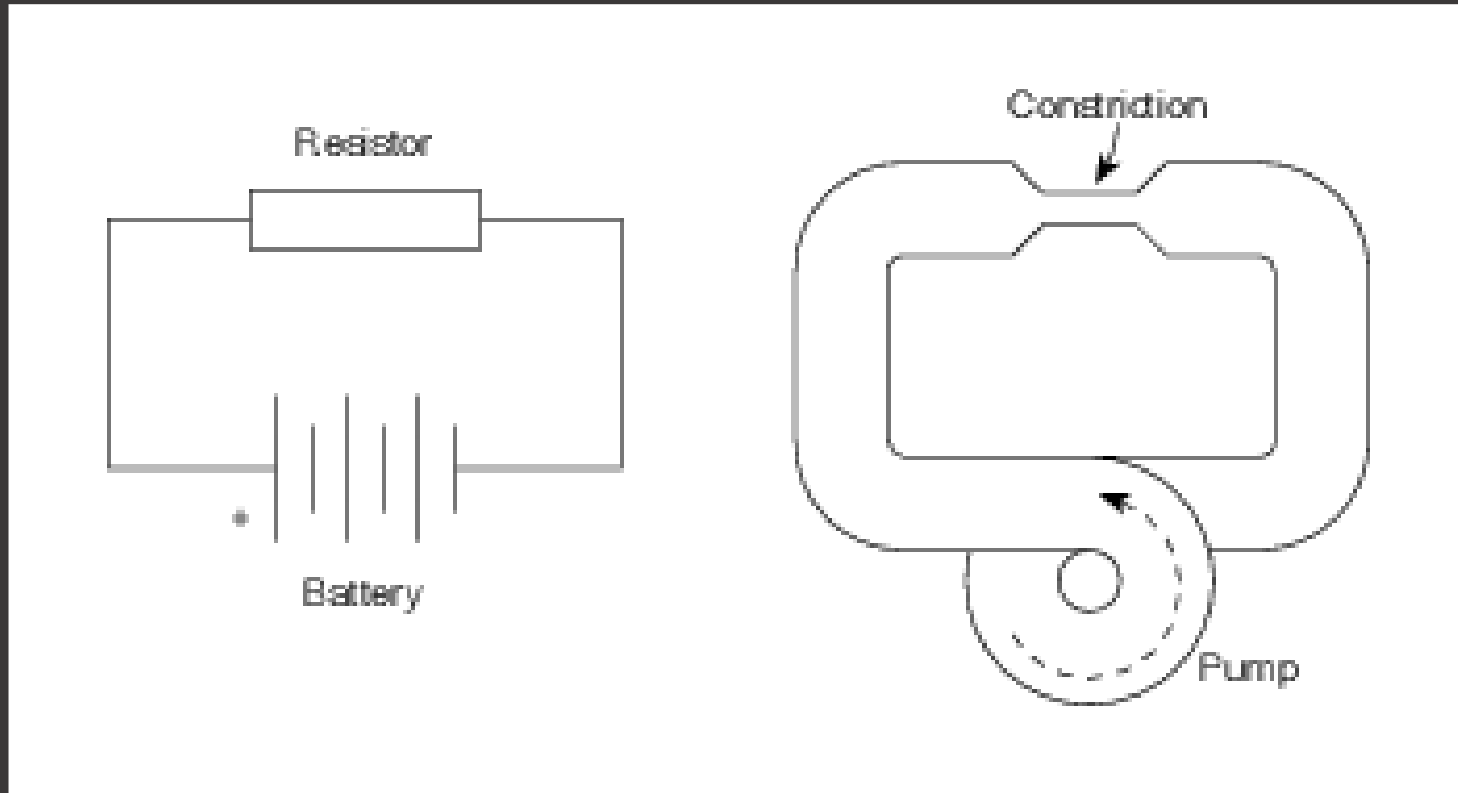


Resistance – measured in Ohms ( $\Omega$ )

# Conductors vs Insulators



Conductors

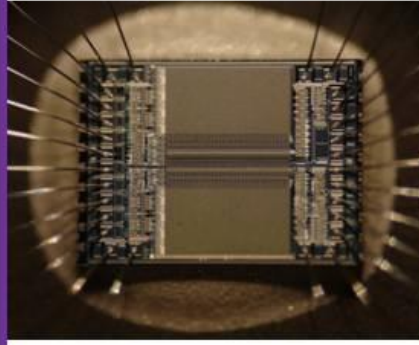

Semi-conductors



Insulators



# All Shapes and Sizes

Surface Mount Resistors



Leaded Resistors



High Power & TO Type Resistors



High Voltage Resistors



Current Sense / Shunt Resistors



Precision Resistors



Custom Resistors






Wirewound Resistors



Pulse Withstanding Resistors






# Fixed Resistors – Construction

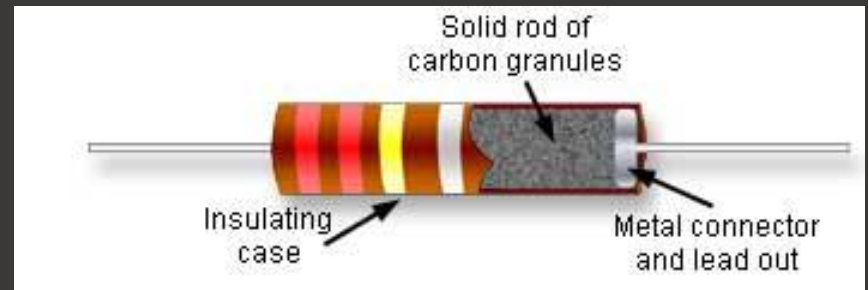
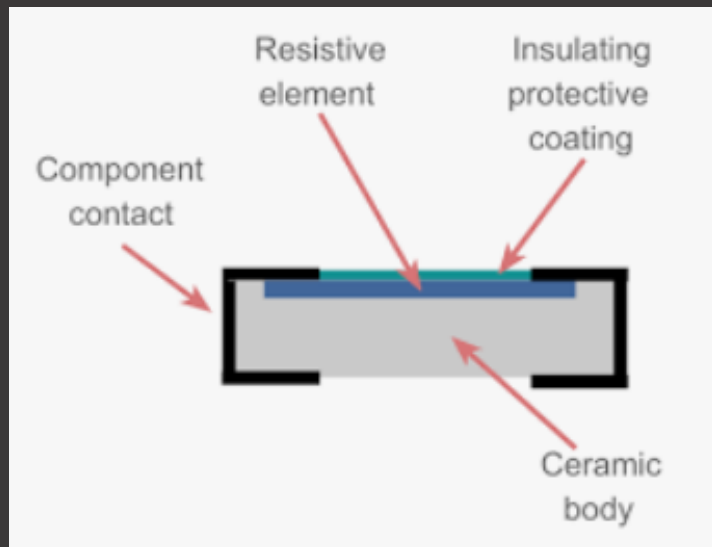
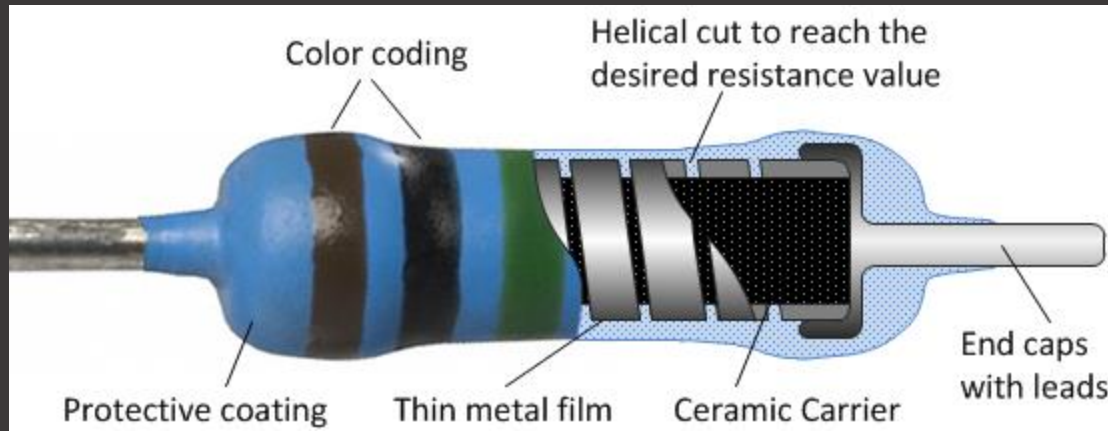




# Variable Resistors – Construction

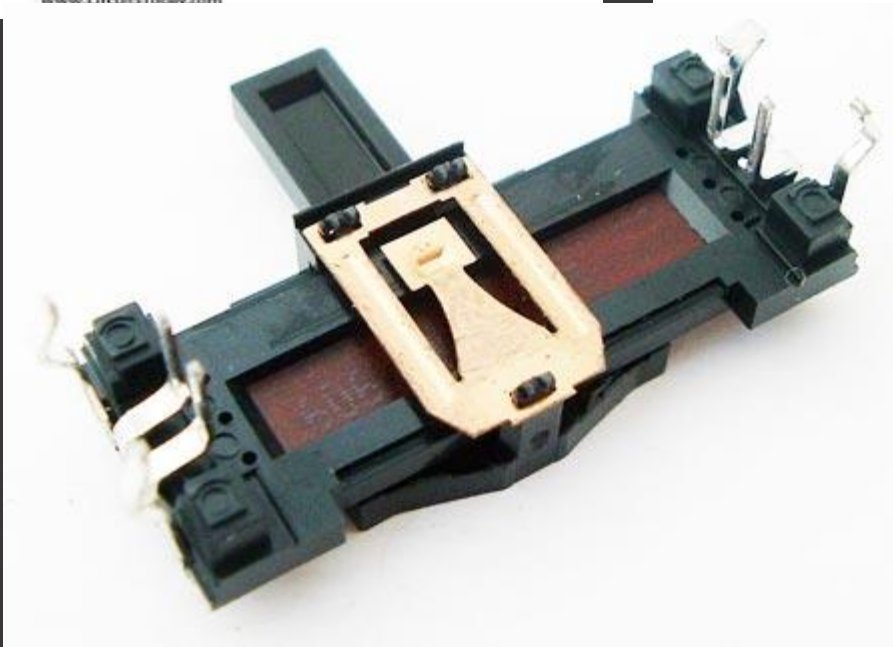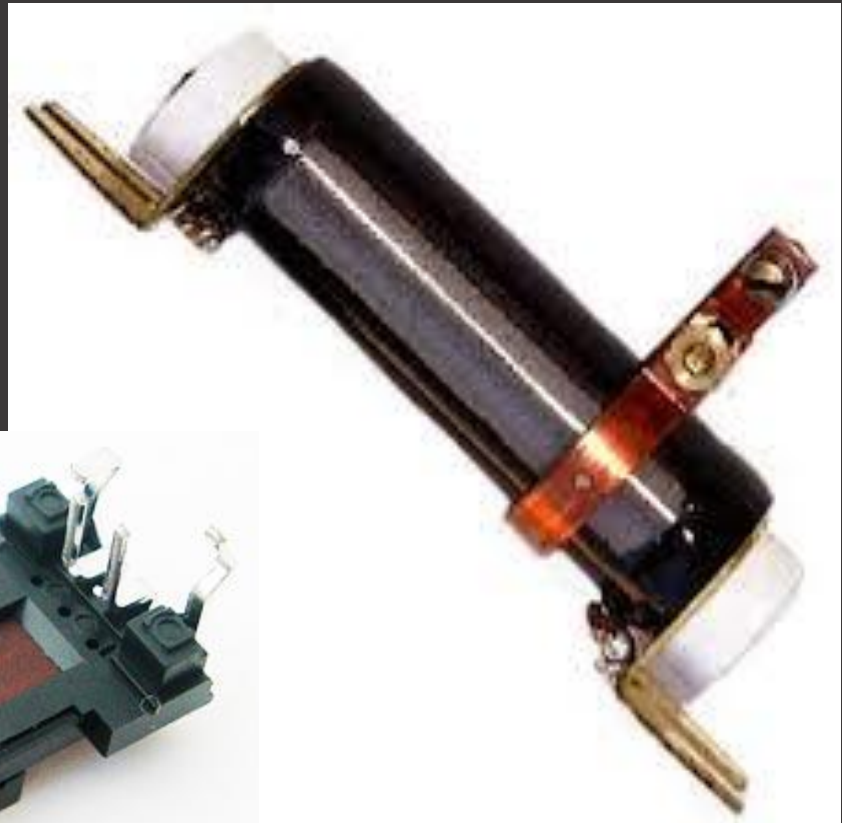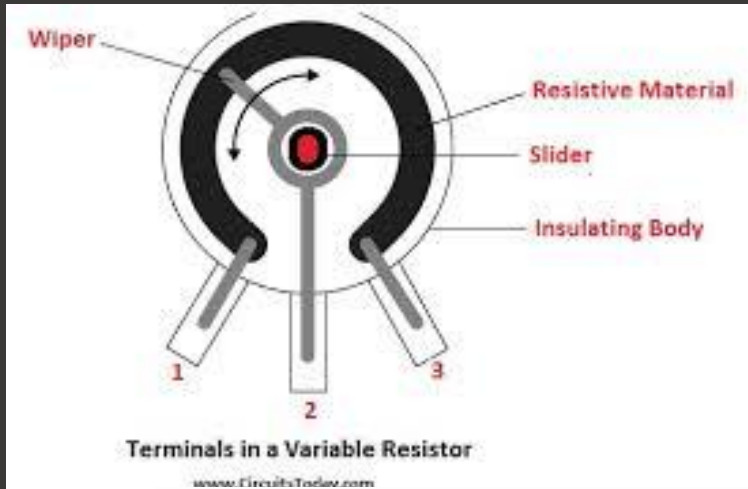


# Resistors – Simple but useful!

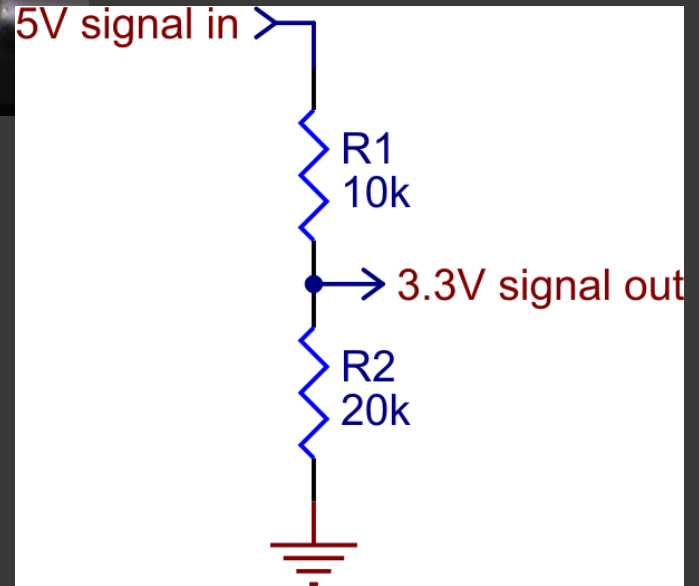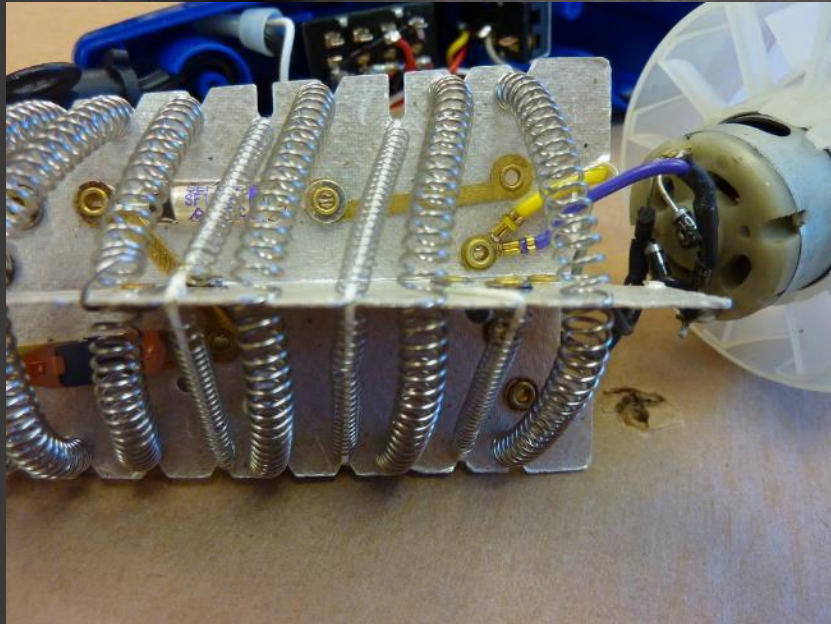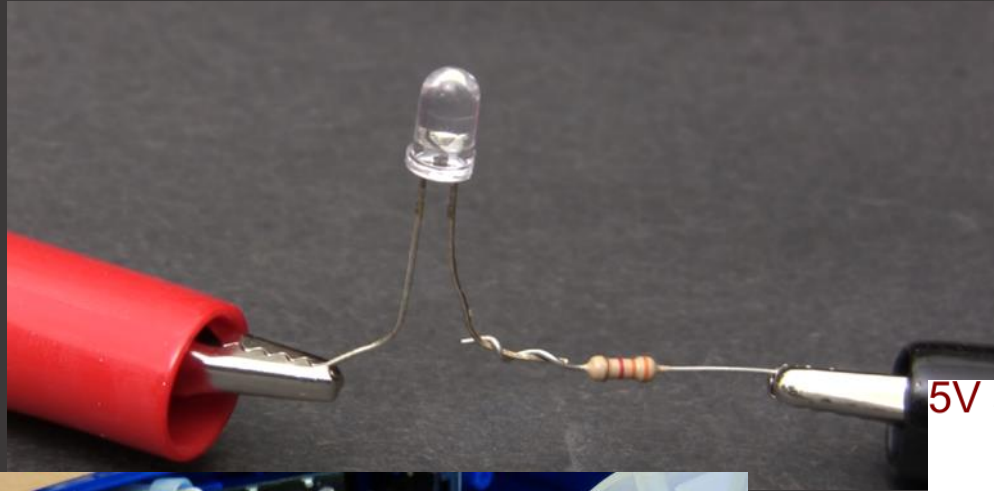

# Ohm's Law





---

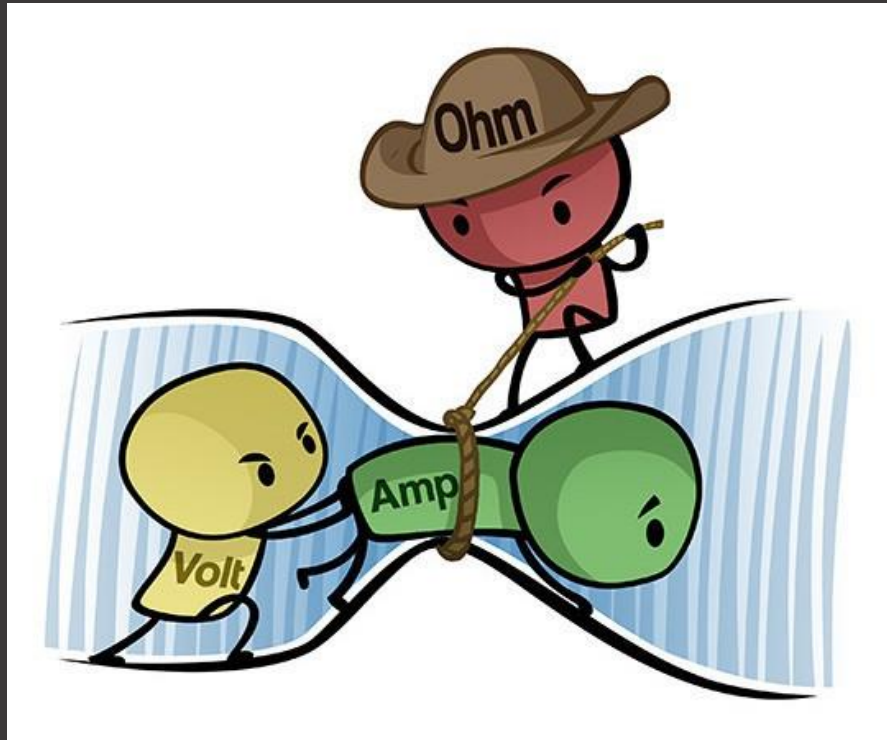

$$V = I * R$$

Special Relationship between voltage,  
current, resistance



# Ohm's Law

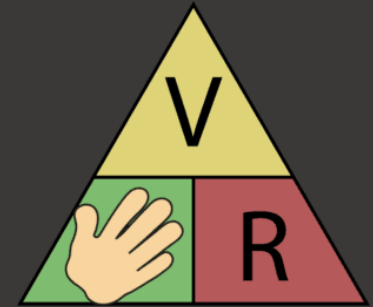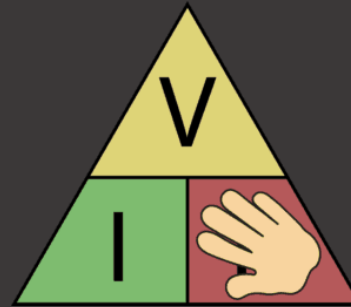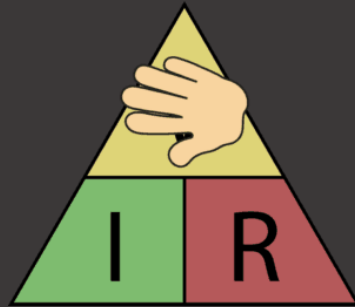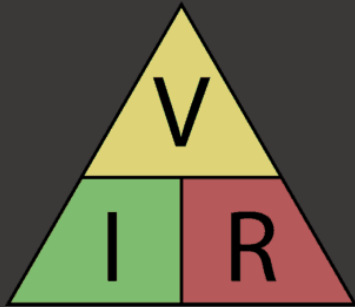

$$V = I * R$$


$$R = V / I$$

$$I = V / R$$

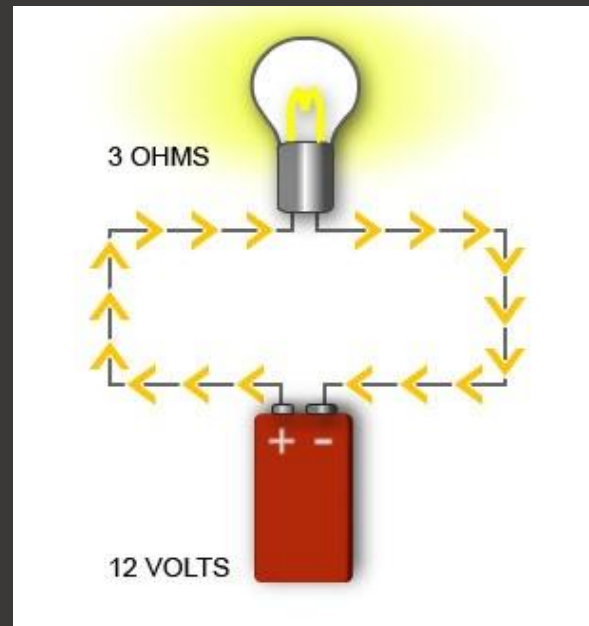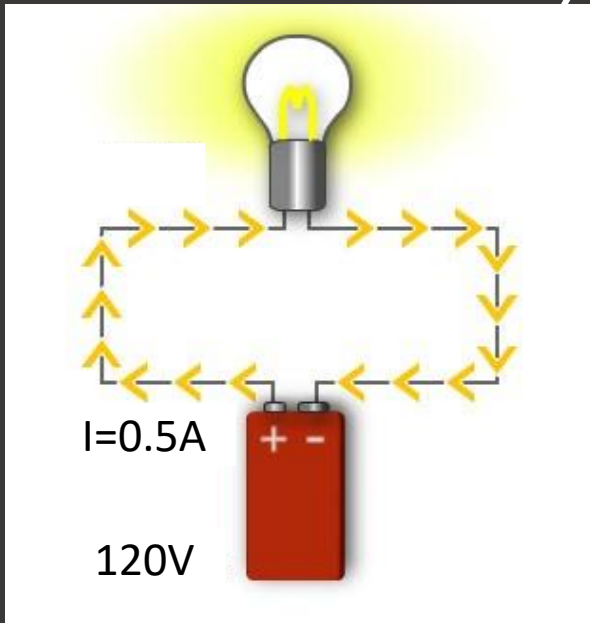


# Resistors in Series

---

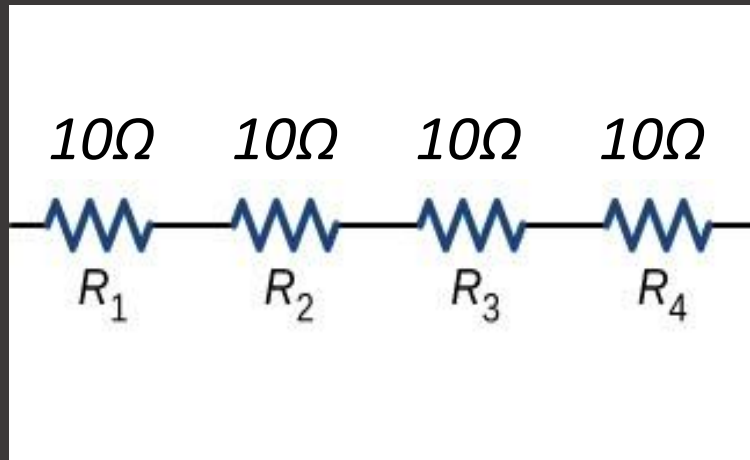


=

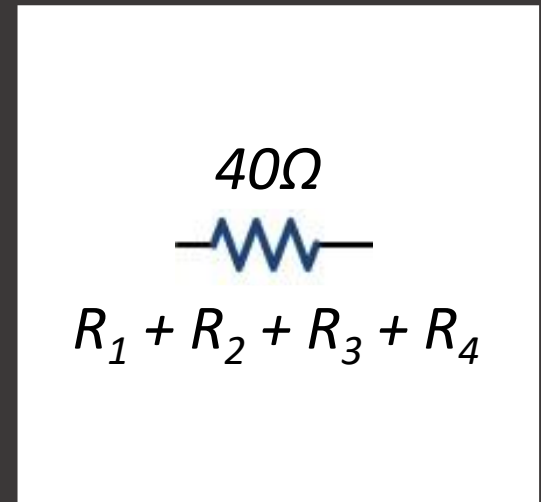




# Resistors in Parallel

---

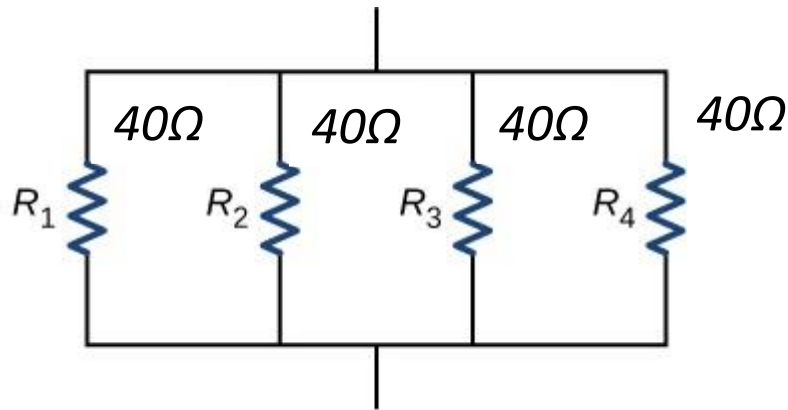


=

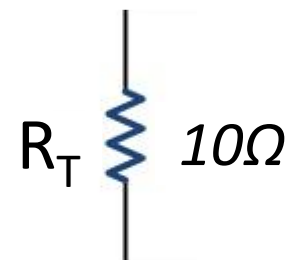

$$R_T = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4}}$$

# Diodes/LEDs

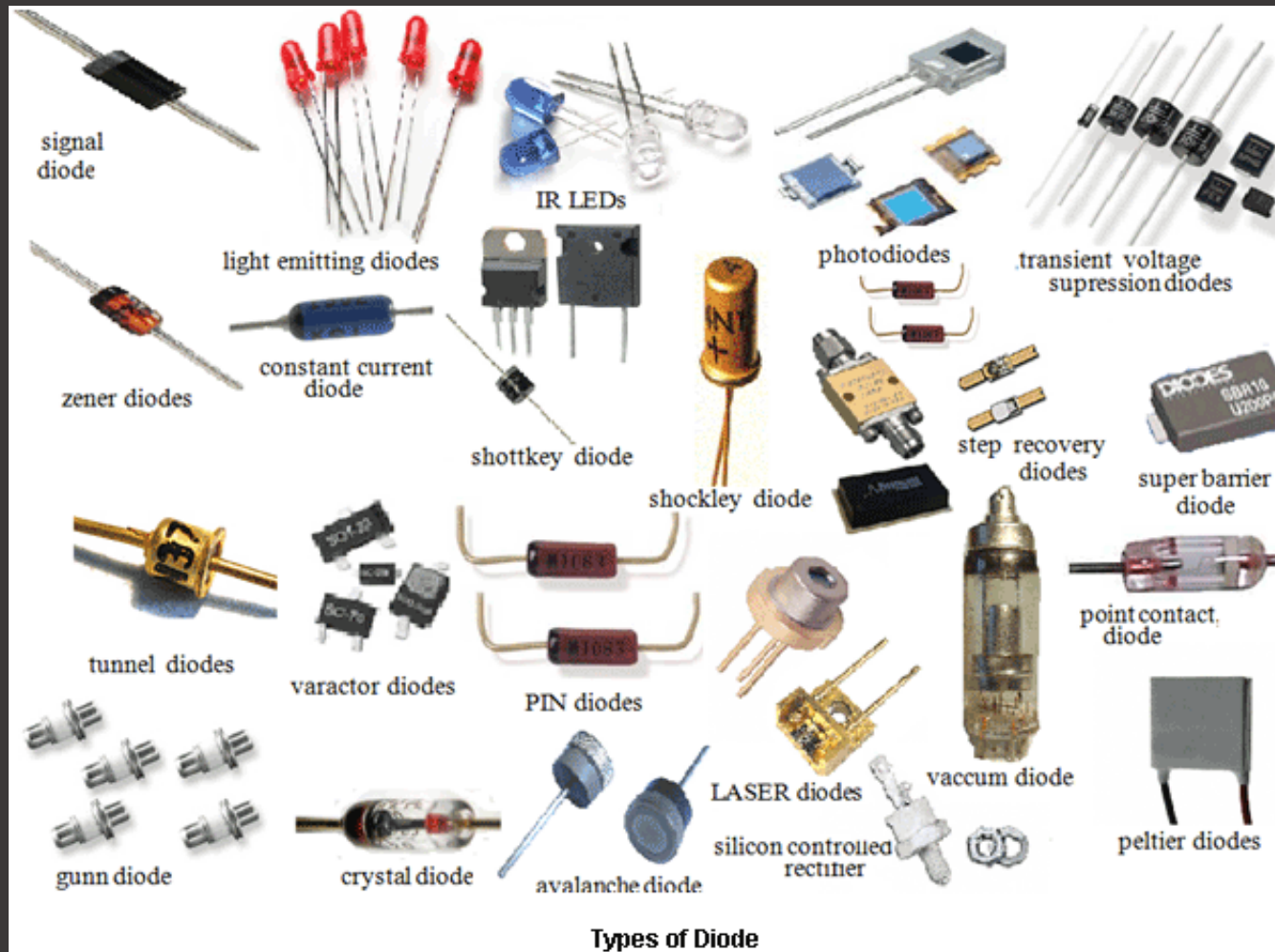


# Diodes – Everyday Uses

---




# Diodes – One-Way Gate

Current Flow

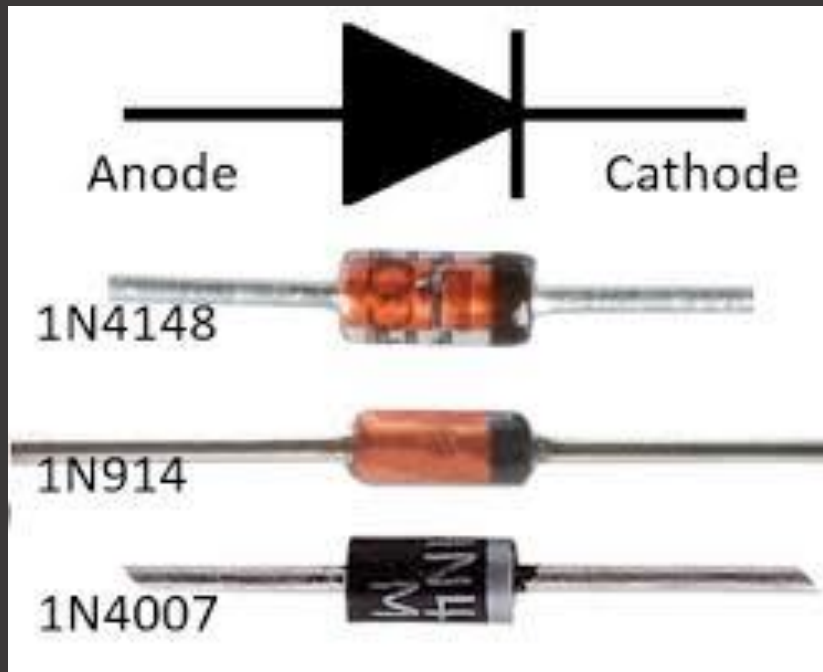


LED

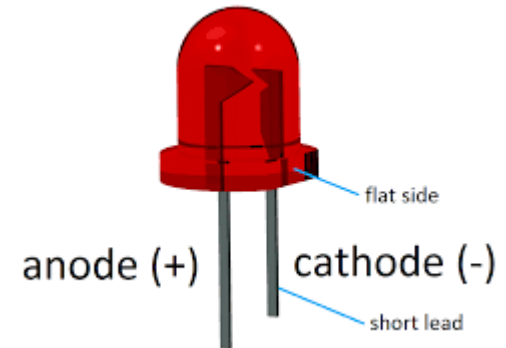

# How to use a diode

---

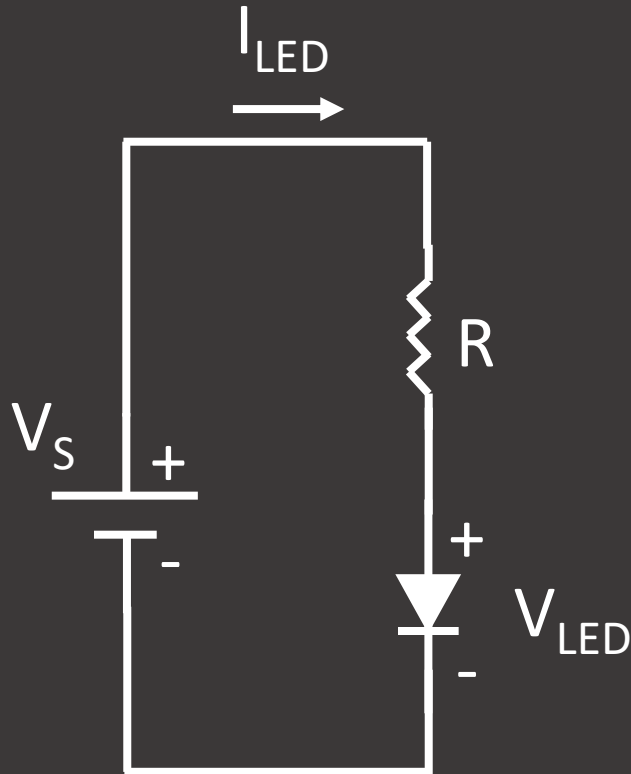



$$V_S \geq V_{LED} + 1V$$

$$I_{LED} \sim 10-20\text{mA}$$

$$V_{LED} \sim 1.8-3.3V$$



# Practical Circuit

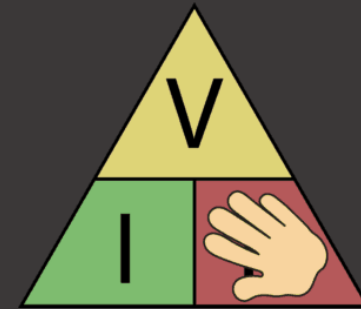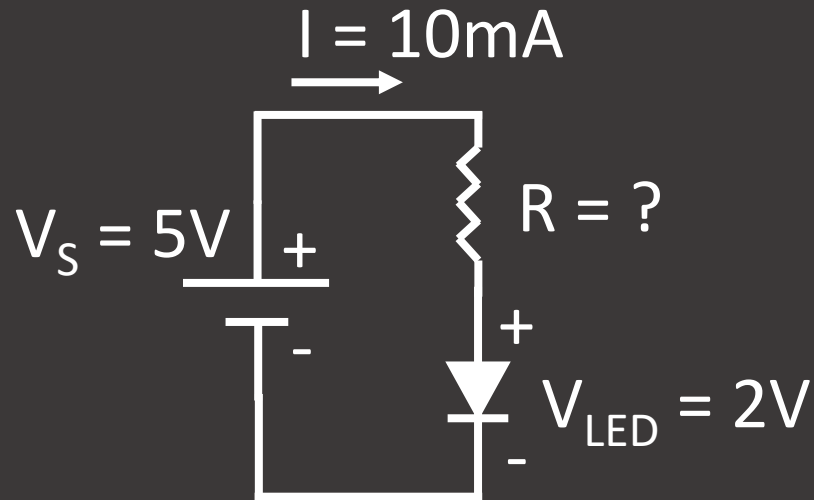

$$R = V / I$$



$$\begin{aligned} R &= (5V - 2V) / 0.01A \\ &= 3V / 0.01A \\ &= 300\Omega \end{aligned}$$

# Switches




# Switch Example

---

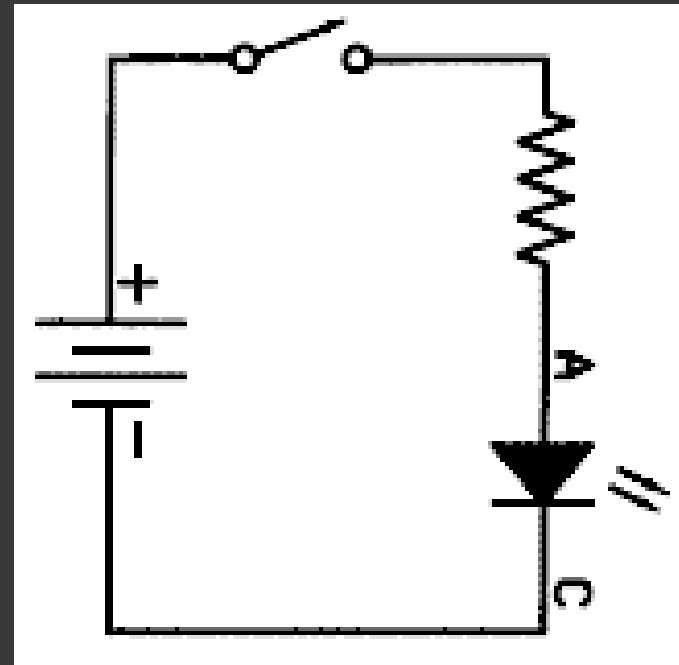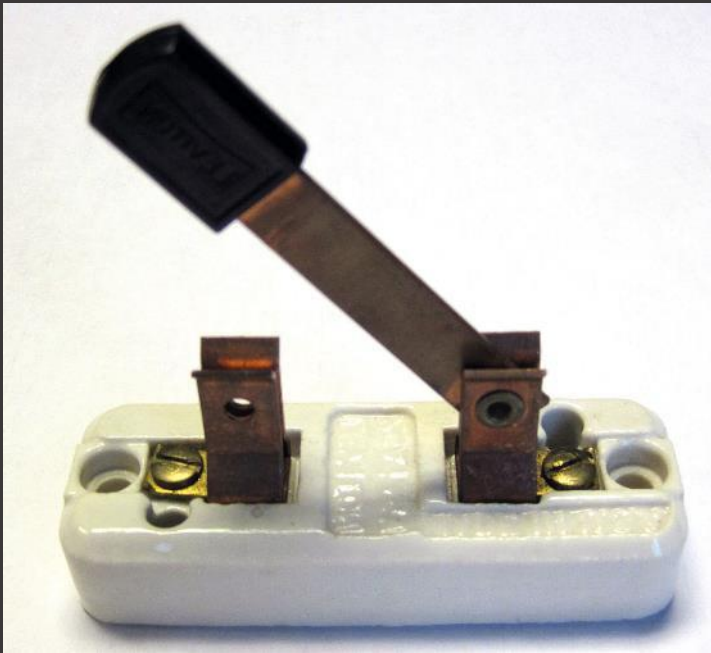



# More Switch Types

---

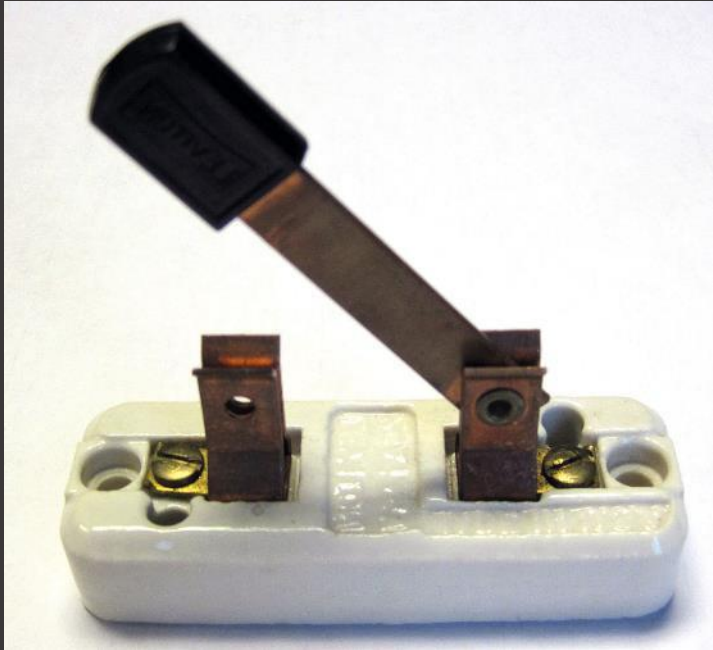

# Poles and Throws

## Switches Configuration by Function

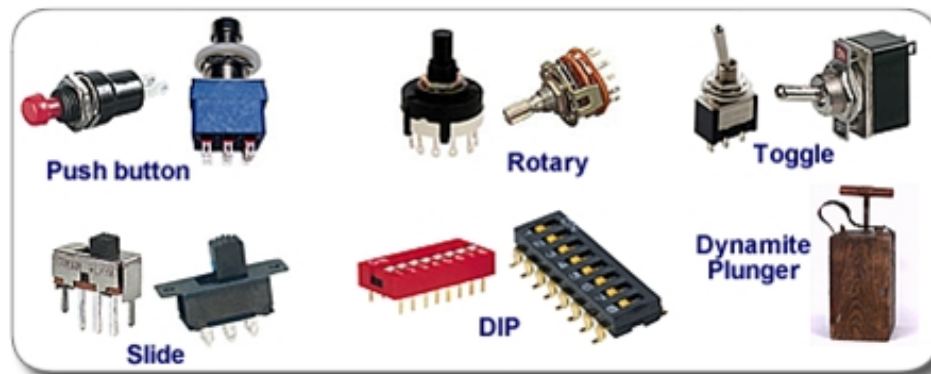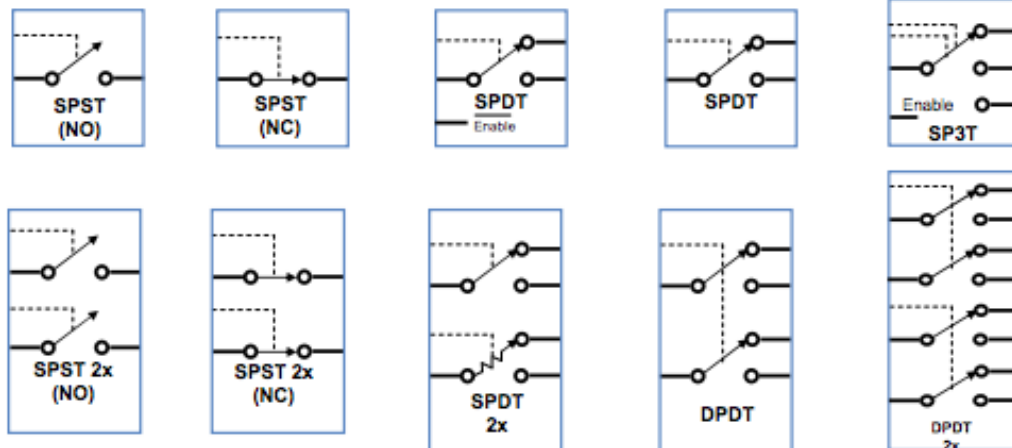



# Capacitors



Radial Ceramic Capacitor



Three Terminal Capacitor




Wierd Ended Electrolytic Capacitor



Surface Mount Electrolytic Capacitor



Motor Run Capacitor

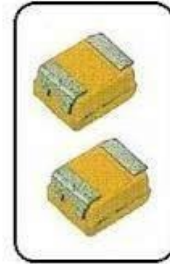


Solid Chip Tanta



Surface Mount Ceramic Capacitor



Suppressor Capacitor

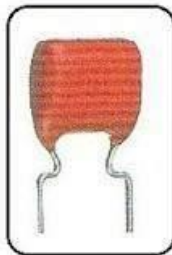

Polyster Capacitor




Polyproplyne Capacitor



Memory Back-up Capacitor



Trimmer Capacitor

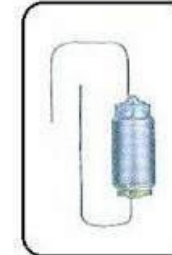

Polysterene Capacitor



Aluminium Electrolytic Capacitor




PCB Mount Electrolytic Capacitor

# Similar to Batteries

---




# “Supply Bypass” Capacitors

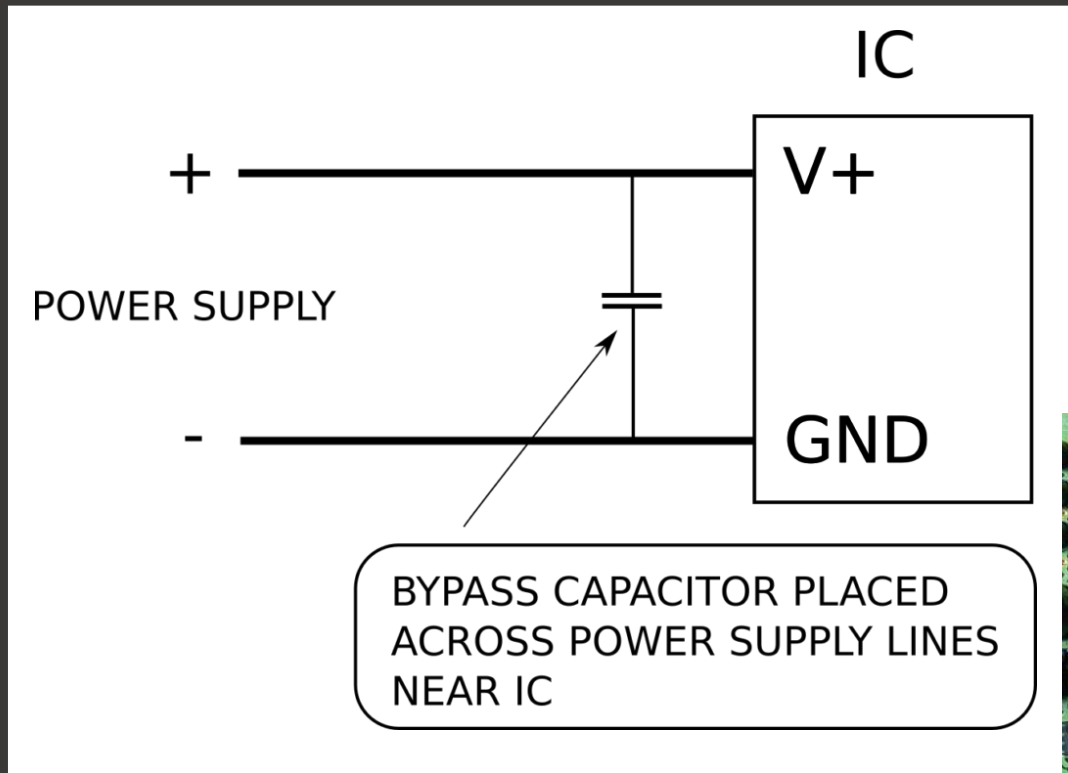



# Capacitors in Parallel

---

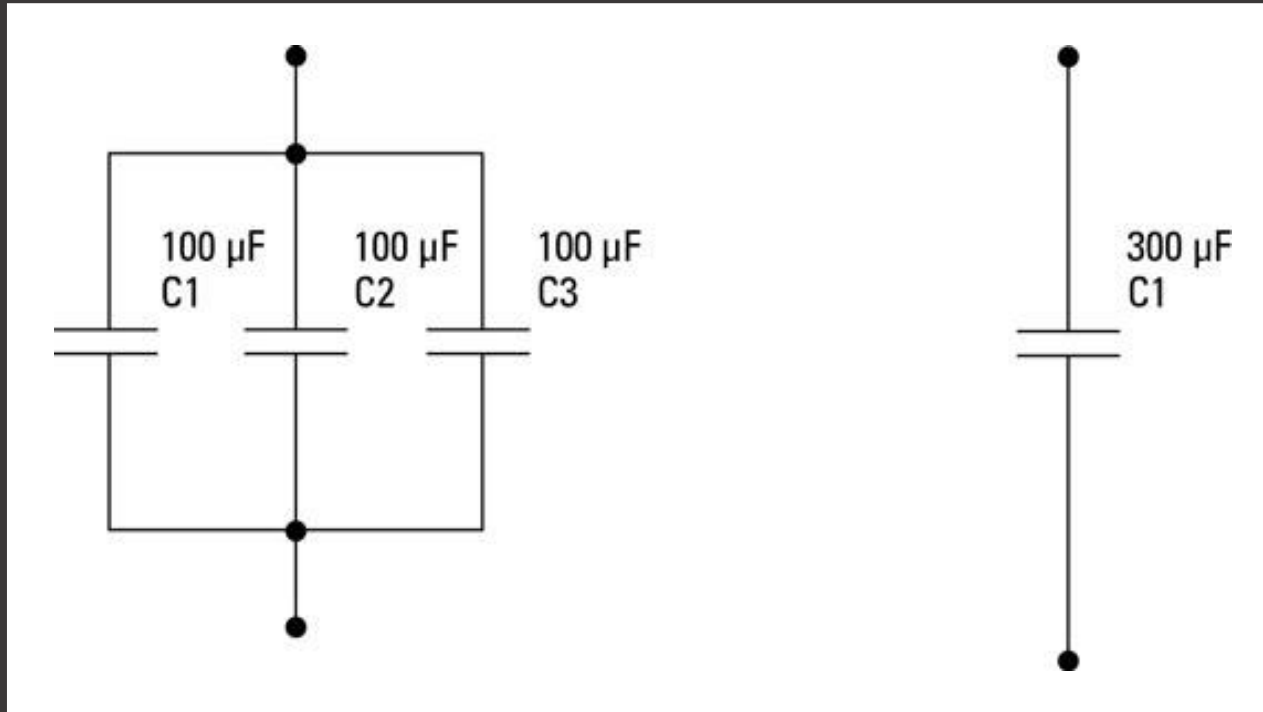

$$C_T = C_1 + C_2 + C_3$$

# Capacitors in Series

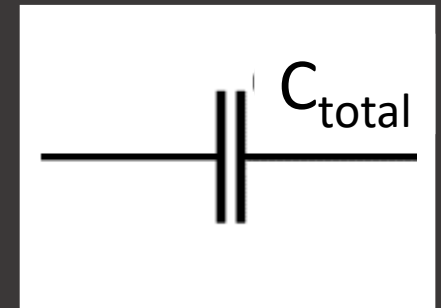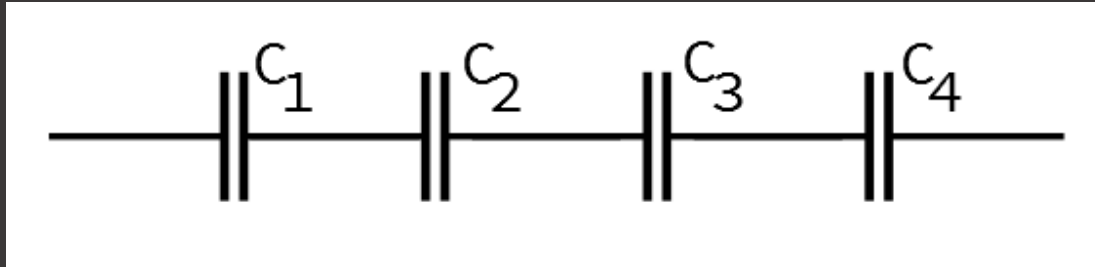

*Series Capacitances*

$$C_{\text{total}} = \frac{1}{\frac{1}{C_1} + \frac{1}{C_2} + \dots + \frac{1}{C_n}}$$

# Further Reading

---

Falstad Circuit Simulator – Runs in Browser  
Mattermost Channel

YouTube Videos

All About Circuits

- <https://www.allaboutcircuits.com/education/>

Sparkfun – [learn.sparkfun.com](https://learn.sparkfun.com)