
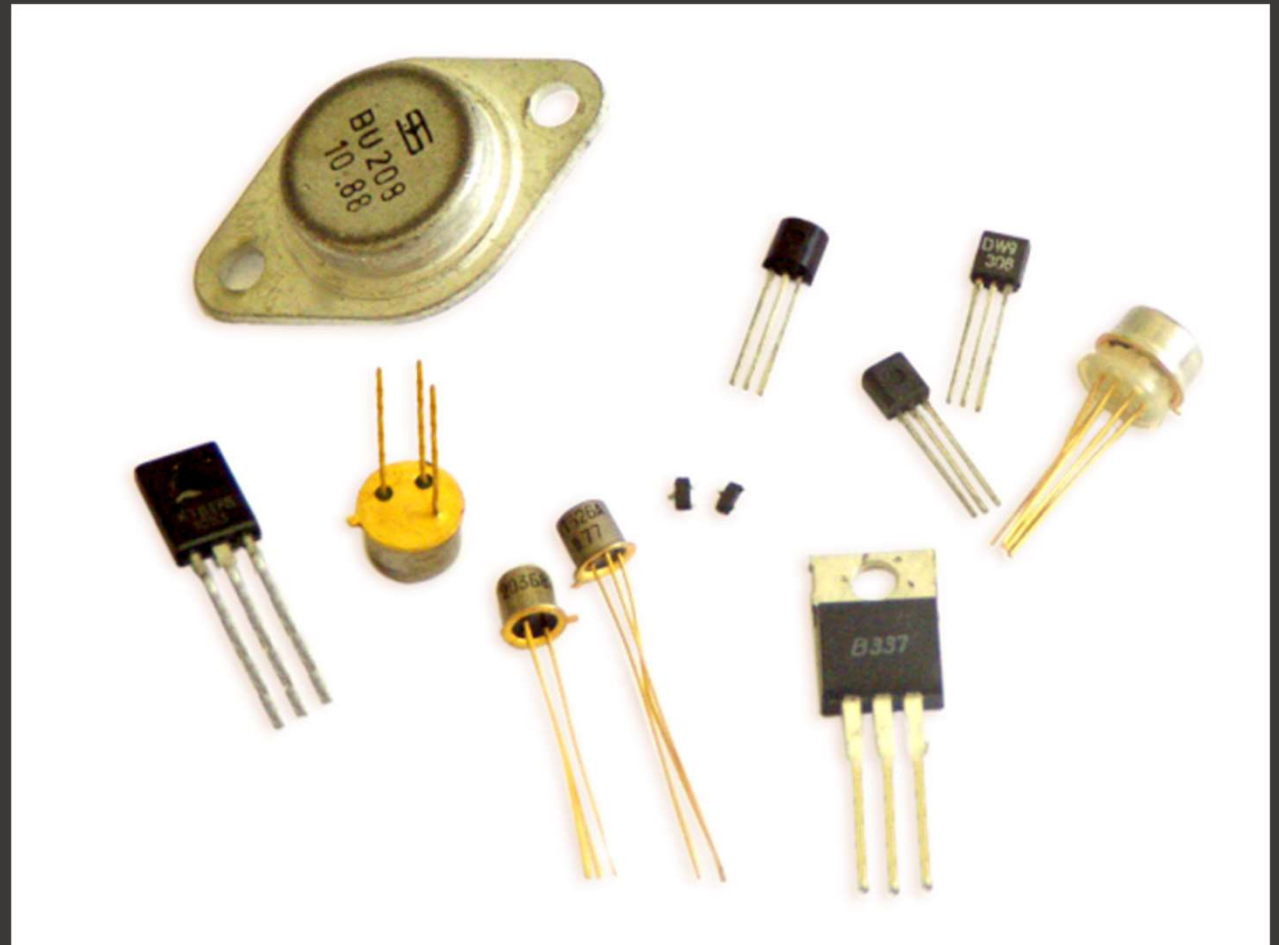


Using, Choosing and Abusing Transistors

Ray Crampton, Feb 2019

Add more practical examples

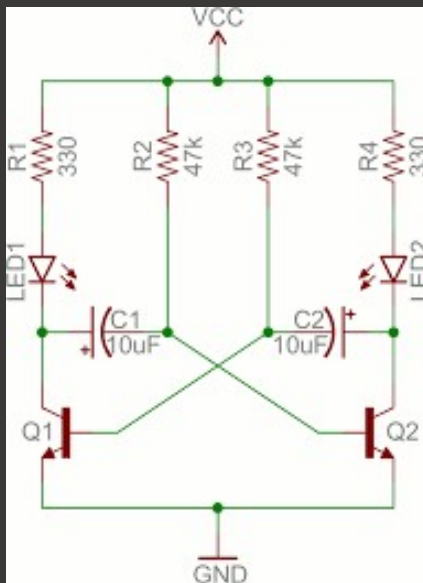

WARNING

WARNING

WARNING

WARNING

WARNING

Rules of thumb, assumptions and mixed-quality analogies to come!




BAD ANALOGIES

JUST BECAUSE ONE ARGUMENT RESEMBLES ANOTHER,
DOESN'T MEAN THAT CATS CAN FLY IN SPACE.


Two major types of transistors

Current controlled & Voltage controlled

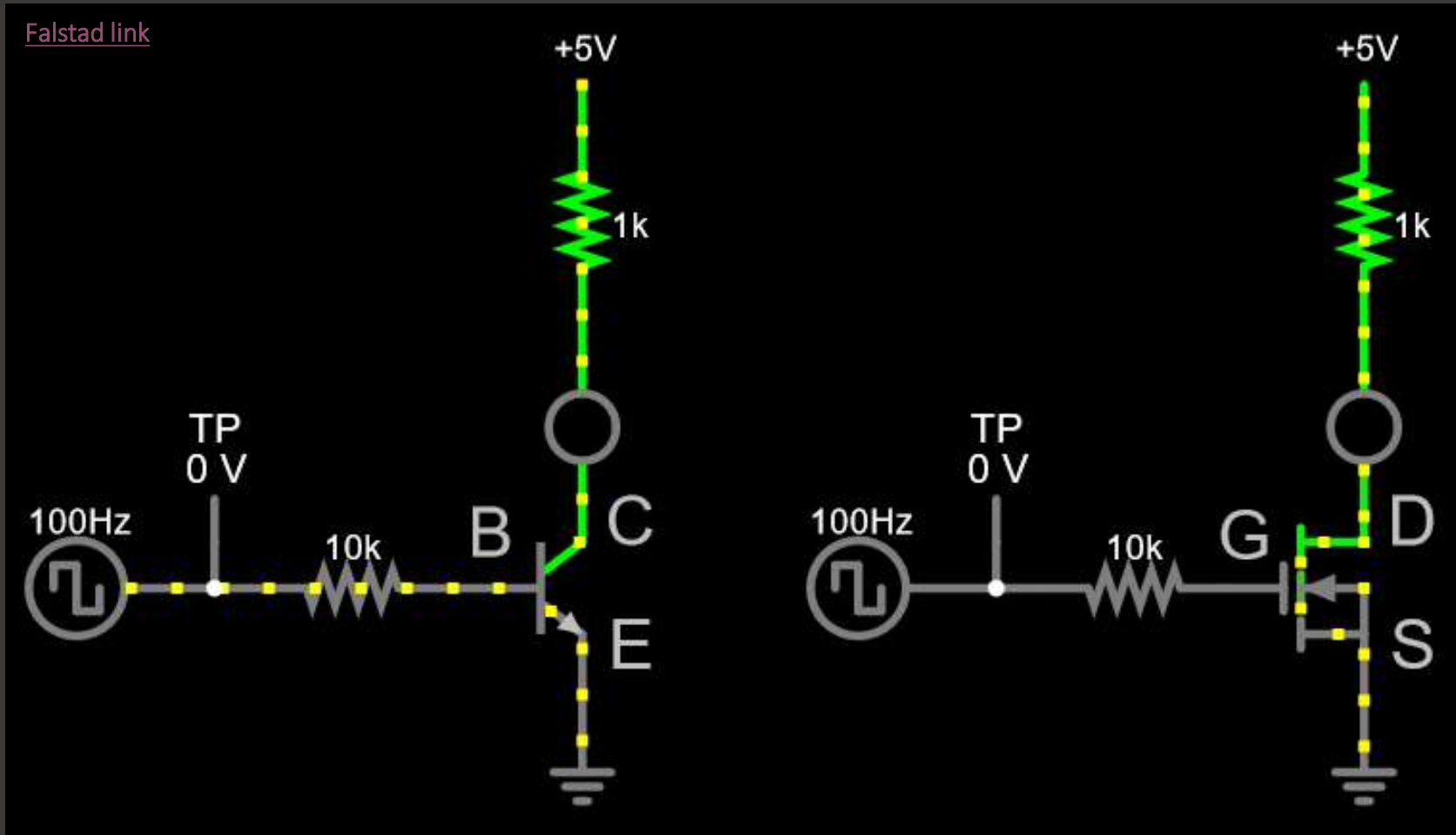


But, voltage drive can be converted into current drive

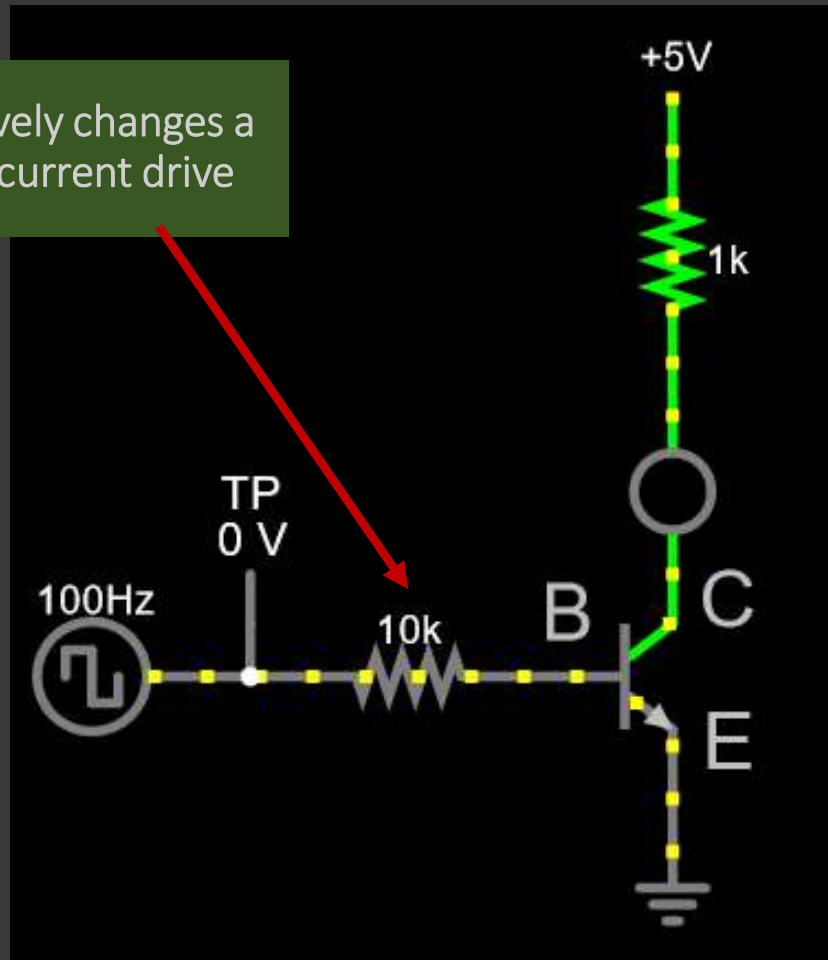The resistor effectively changes a voltage drive to a current drive




Each major type has complementary versions

Falstad link

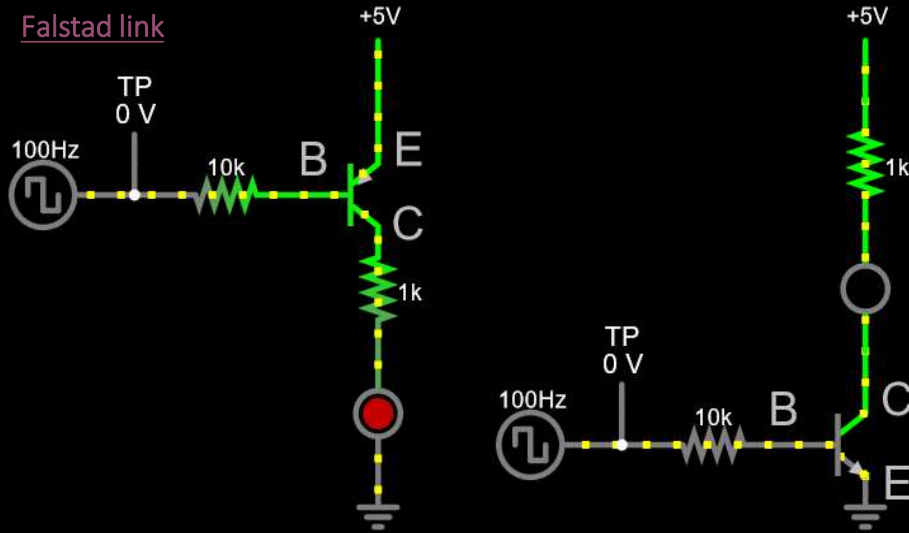


Falstad link

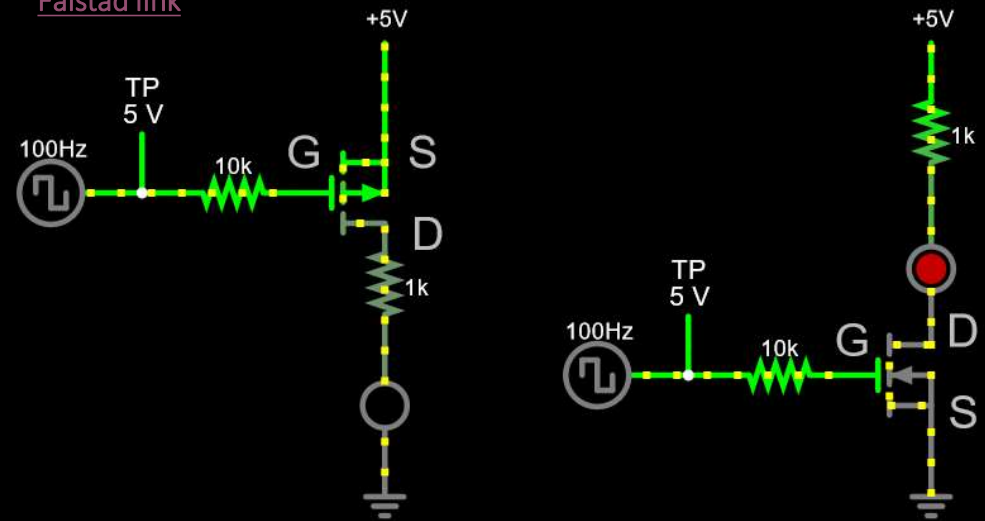


n-type is low side
p-type is high side

“Common Emitter/Source” Inverts

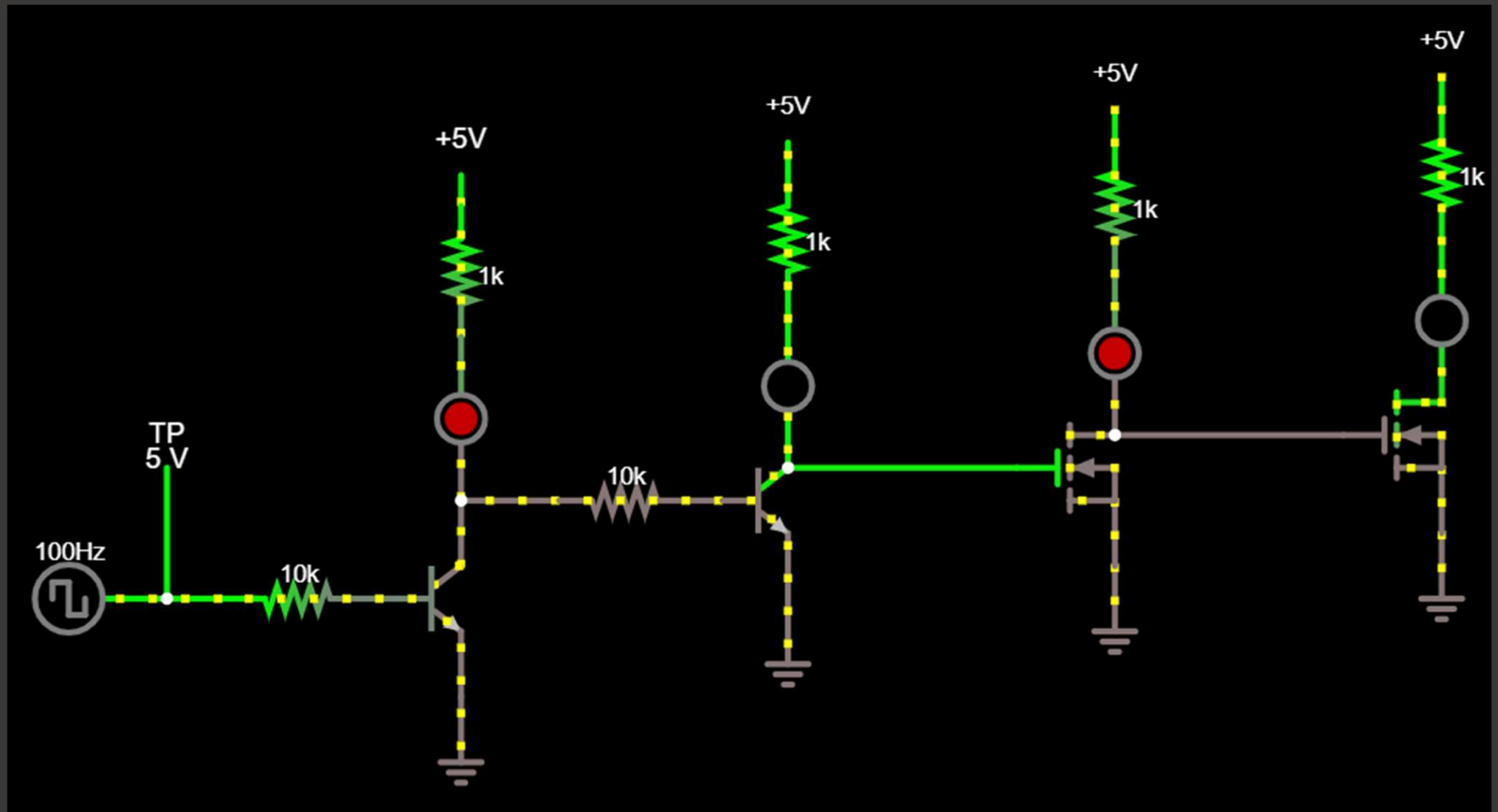


Complementary Bipolar Output

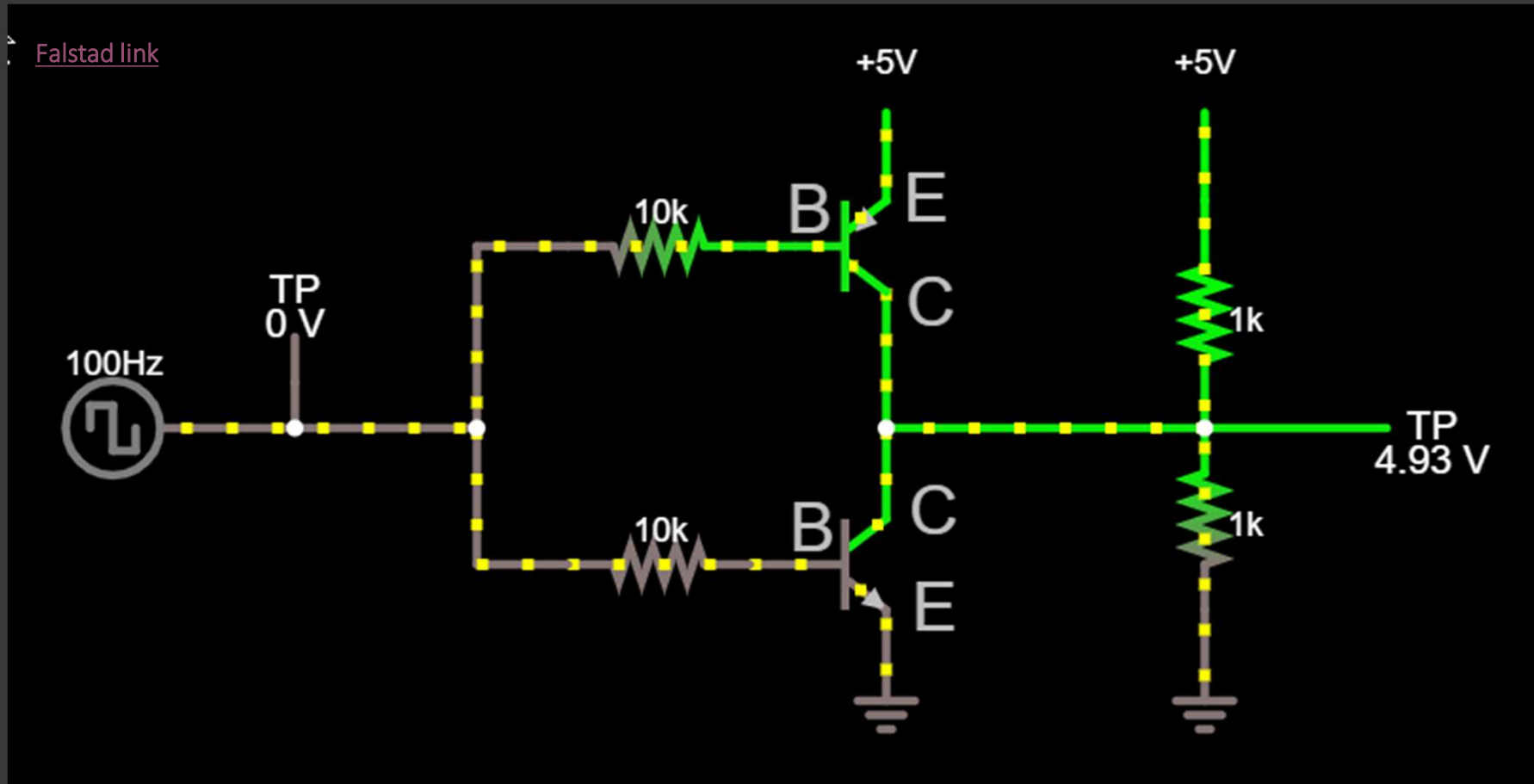



Complementary MOSFET Output

[Falstad link](#)

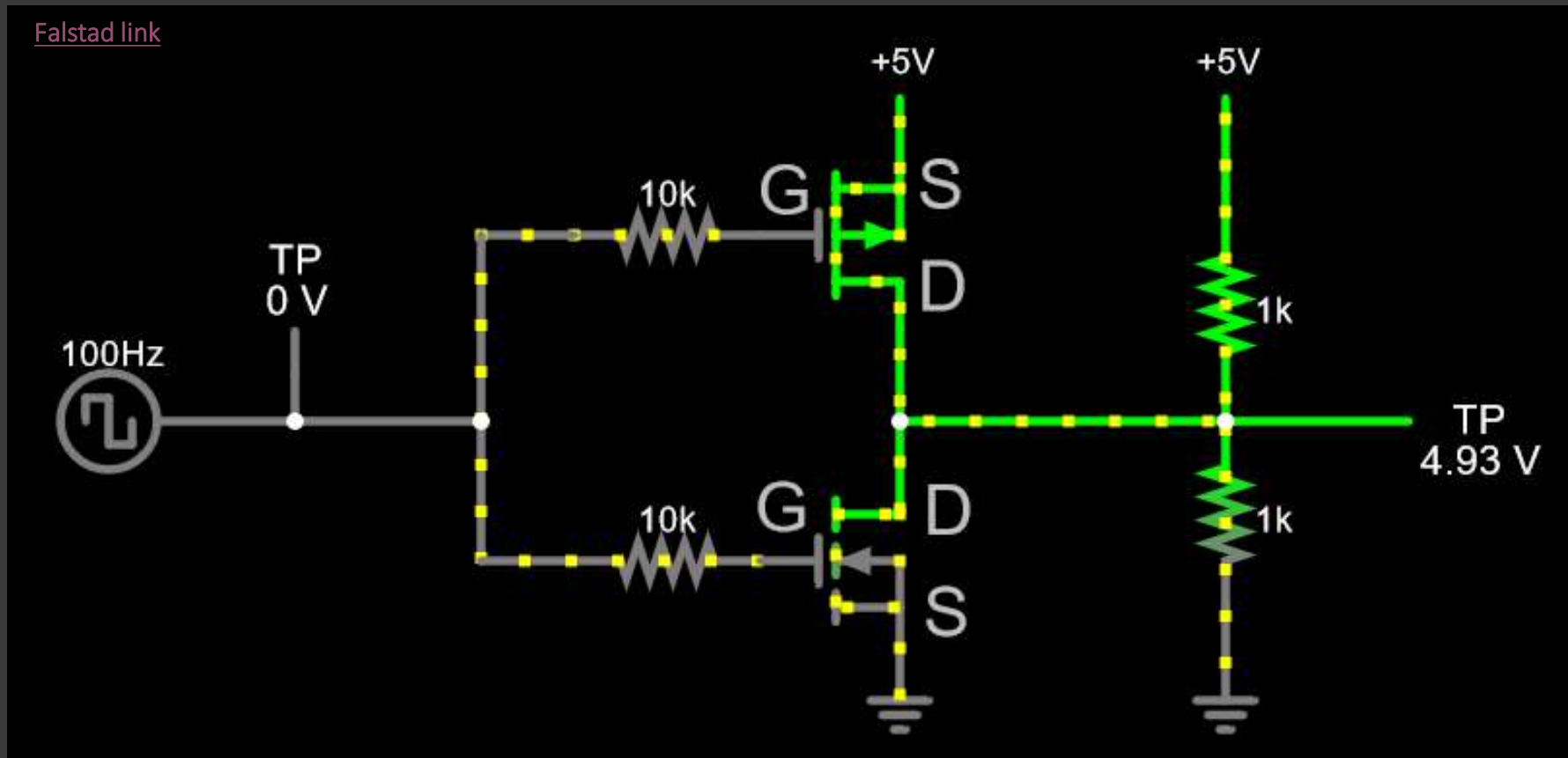


BJT Motor or LED Driver Example

Why is a transistor used here?

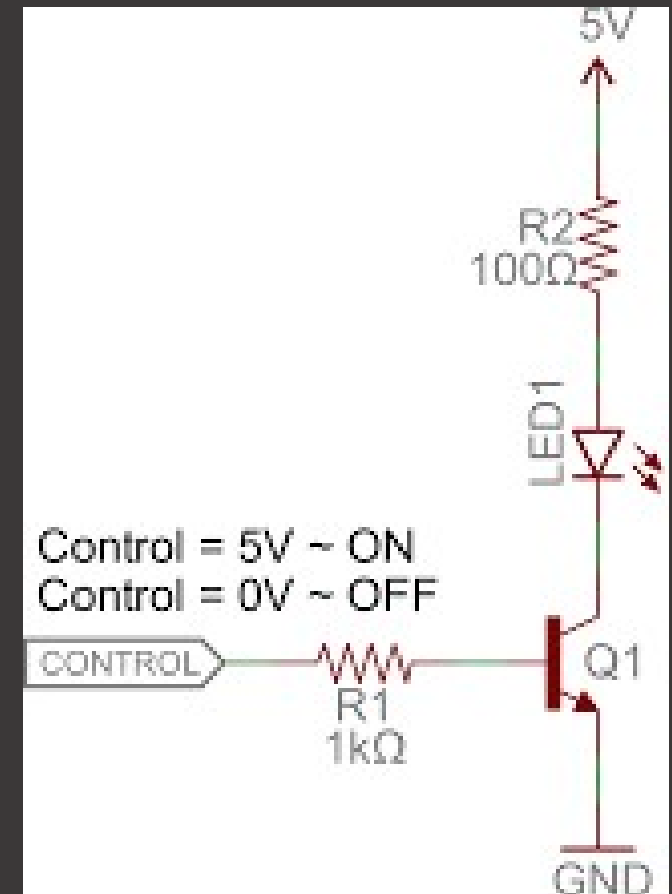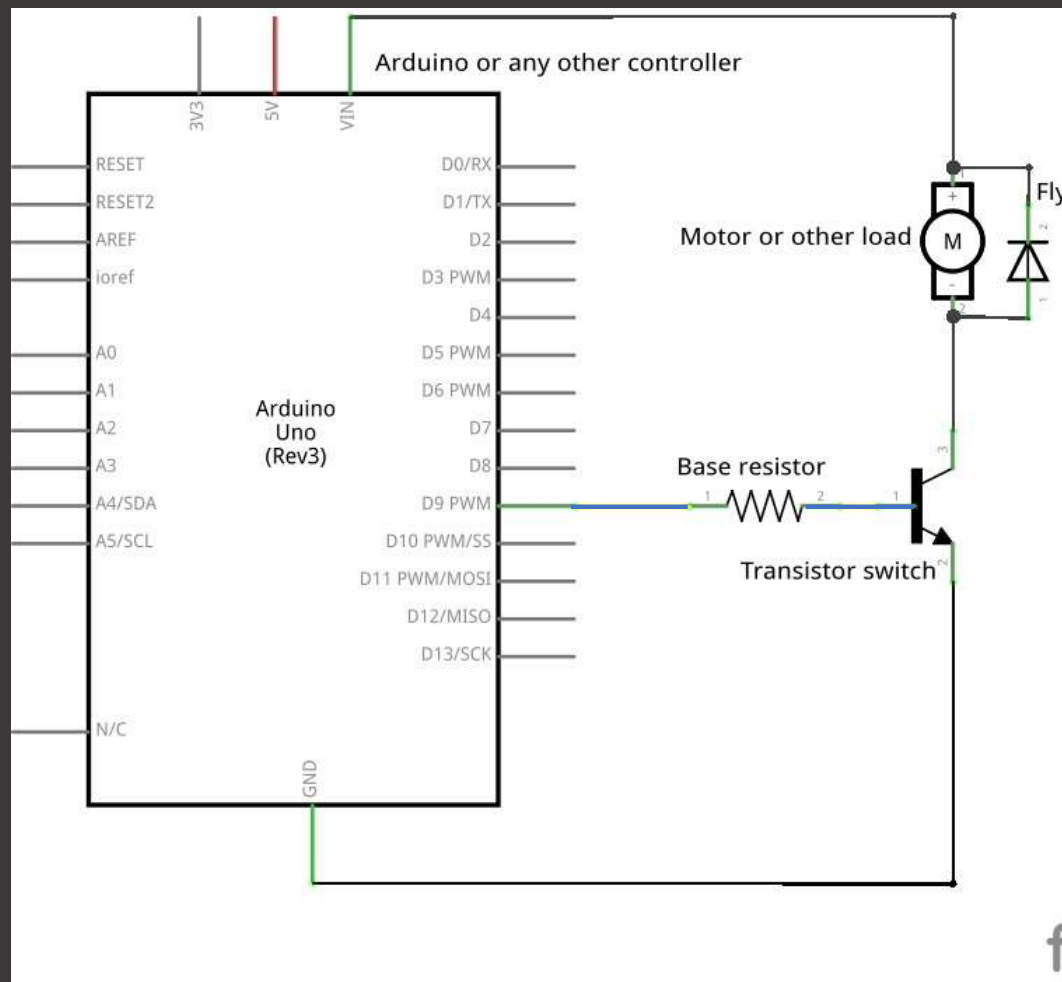


BJT Photodiode Example

Why is a transistor used here?

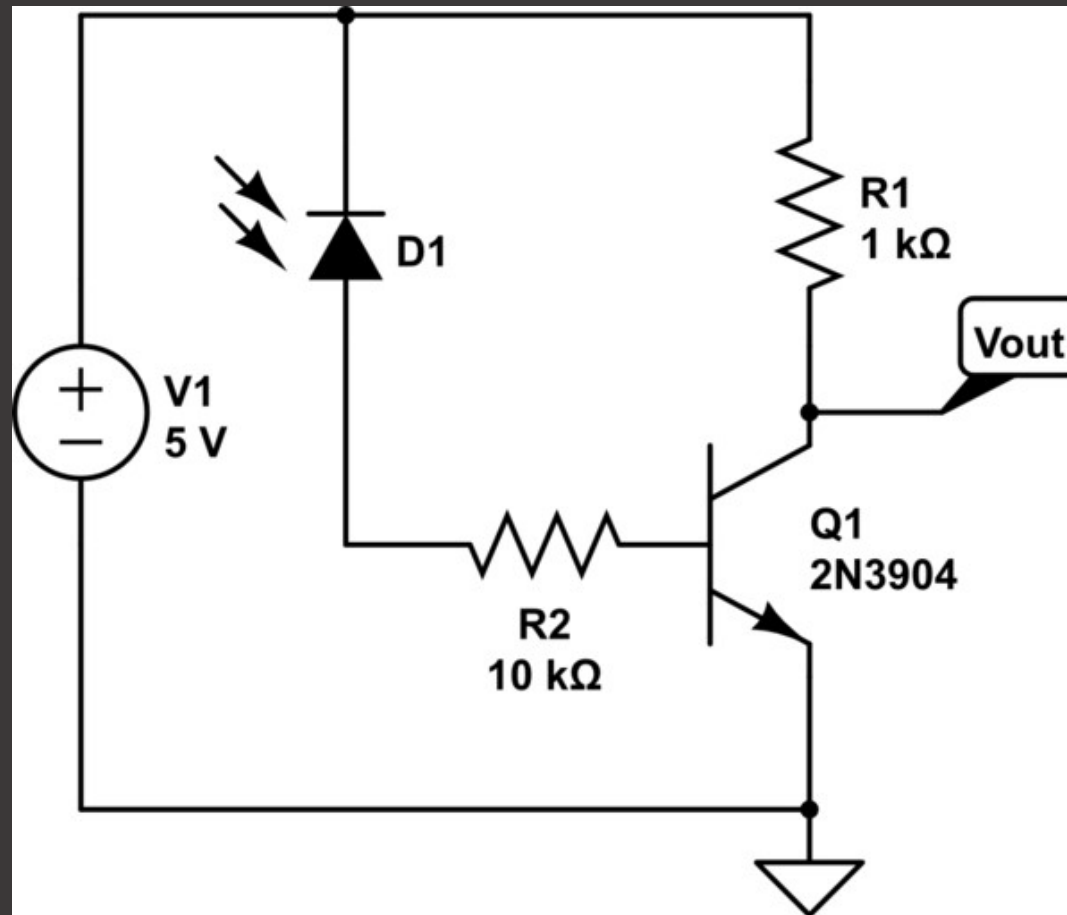


High voltage motor control


Why is a transistor used here?

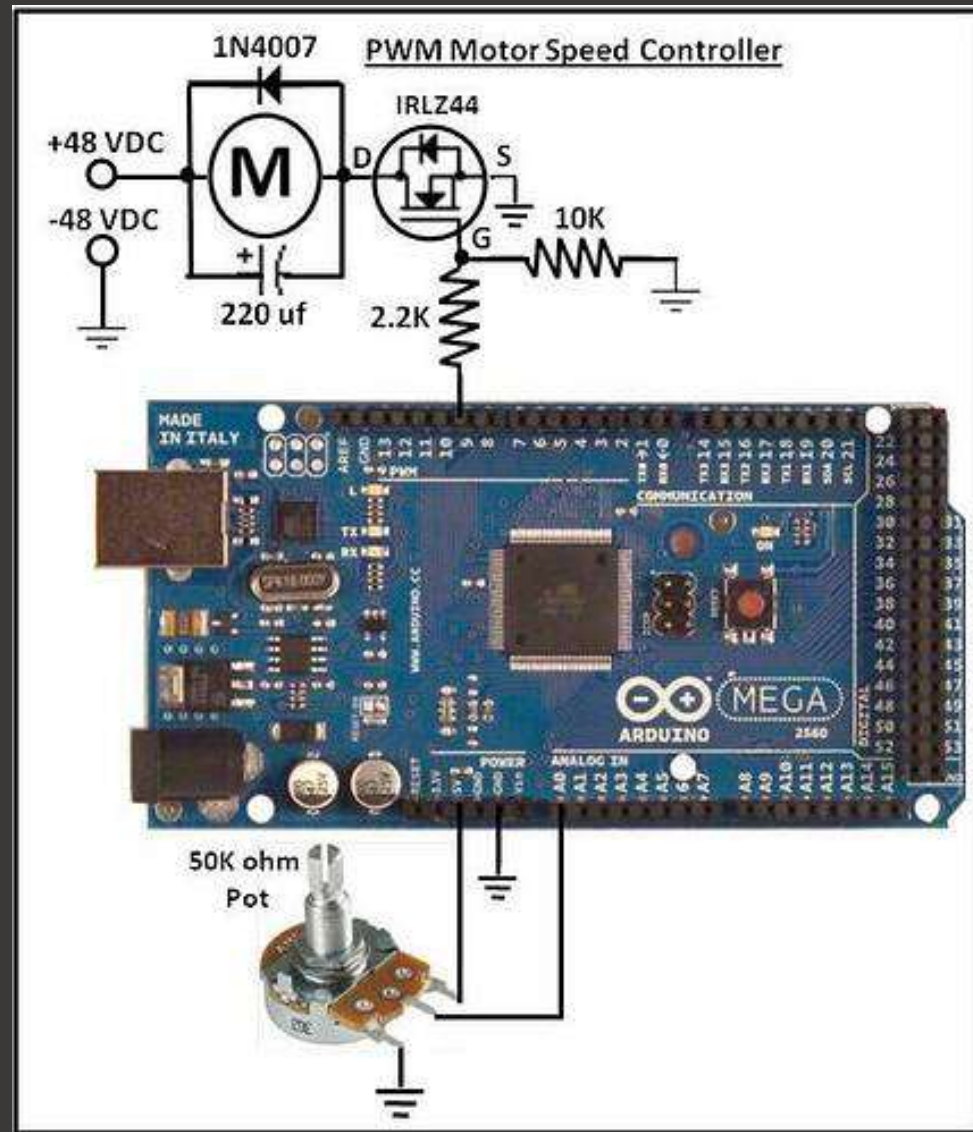

Two transistor oscillator

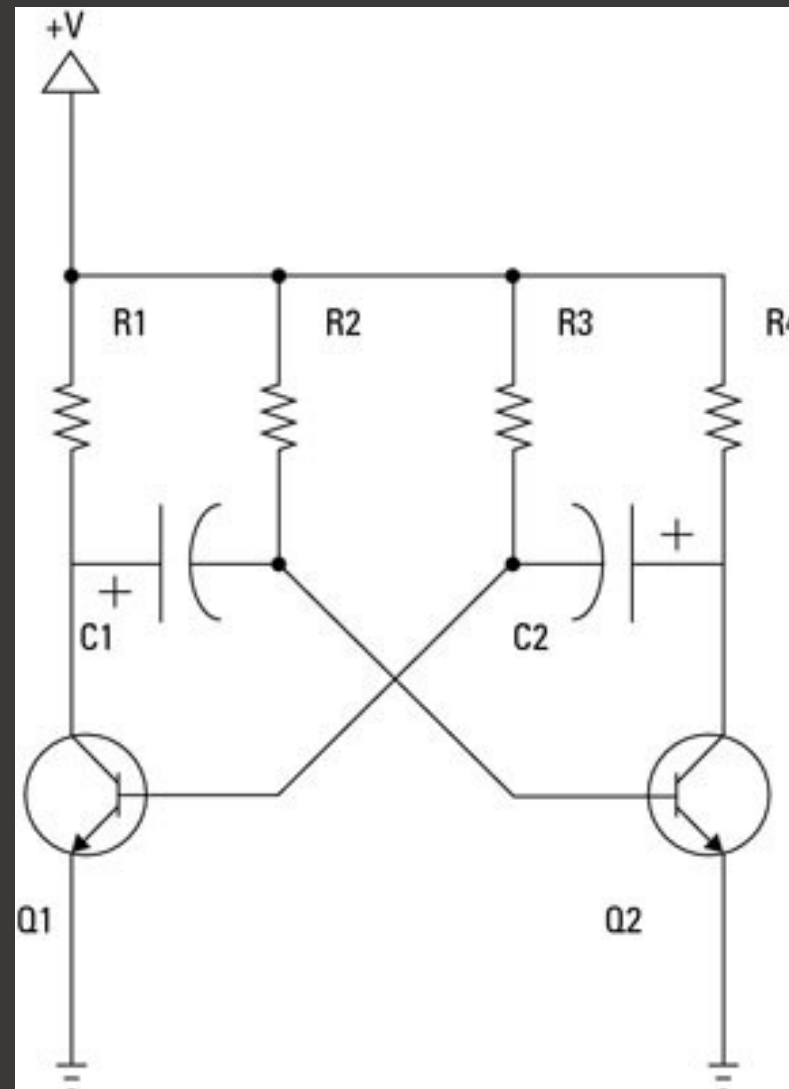


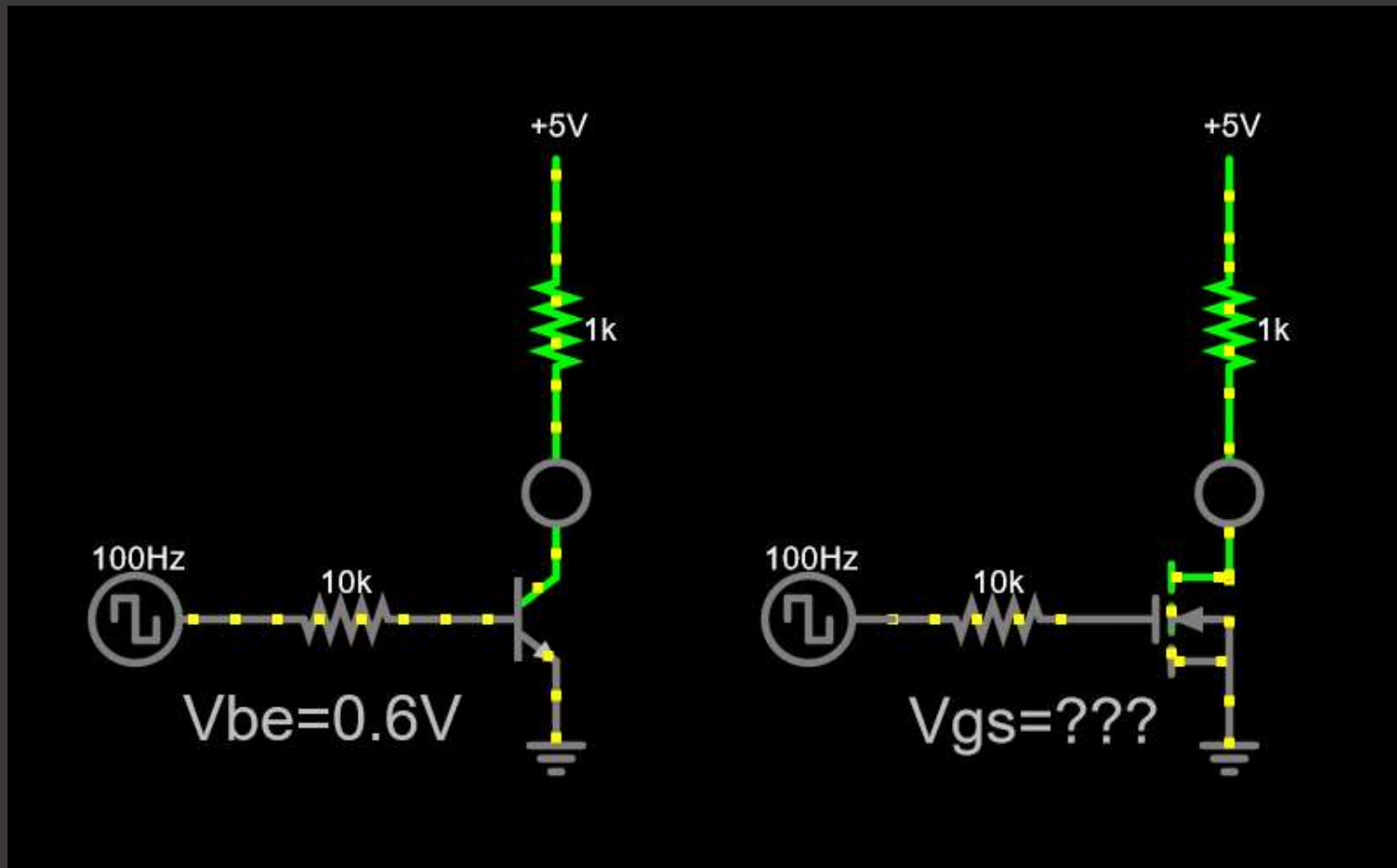If they're the same, why choose one over the other?




BJTs are generally easier to select and use
but... not always

MOSFET Examples

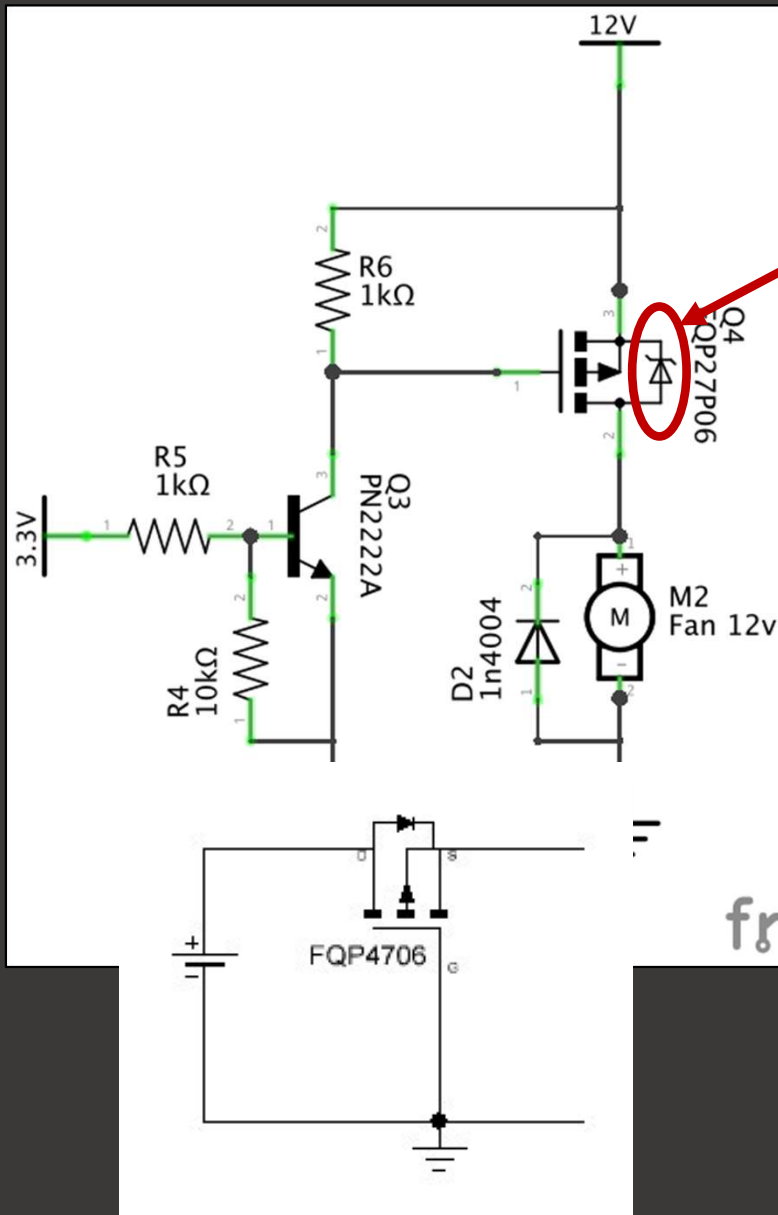

Note the "body diode" which is intrinsic to all MOSFETs


Fault Protected High Side Switch

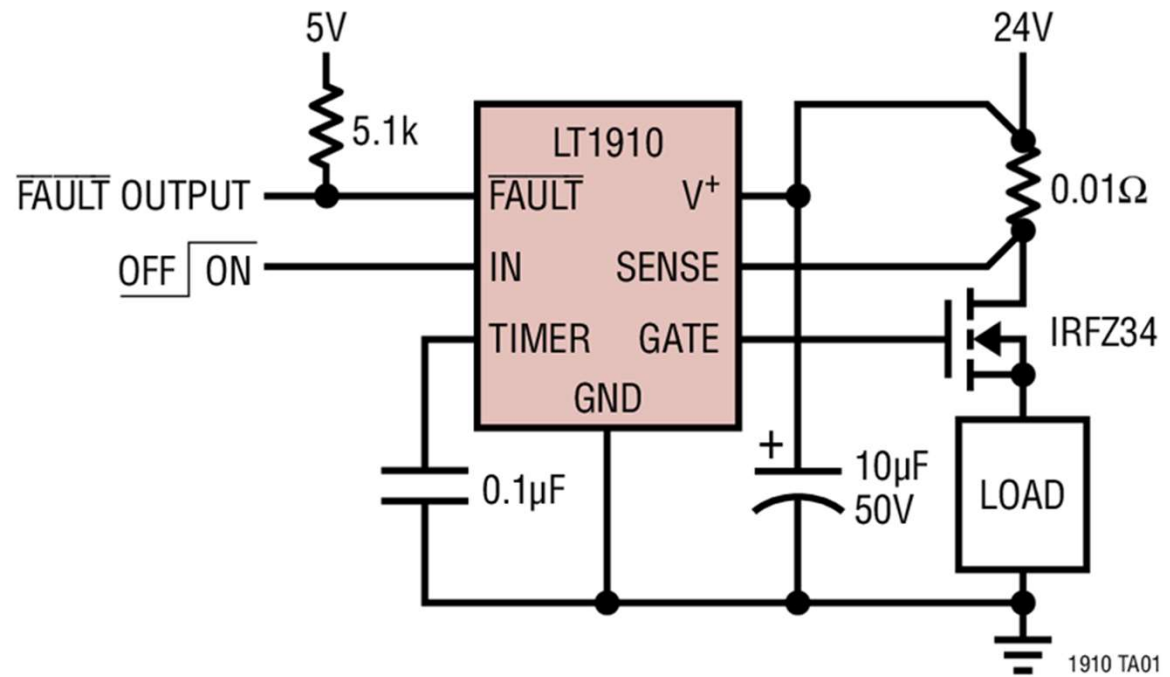

MOSFET, Body Diode Can be Useful

Normal operation is through body diode.

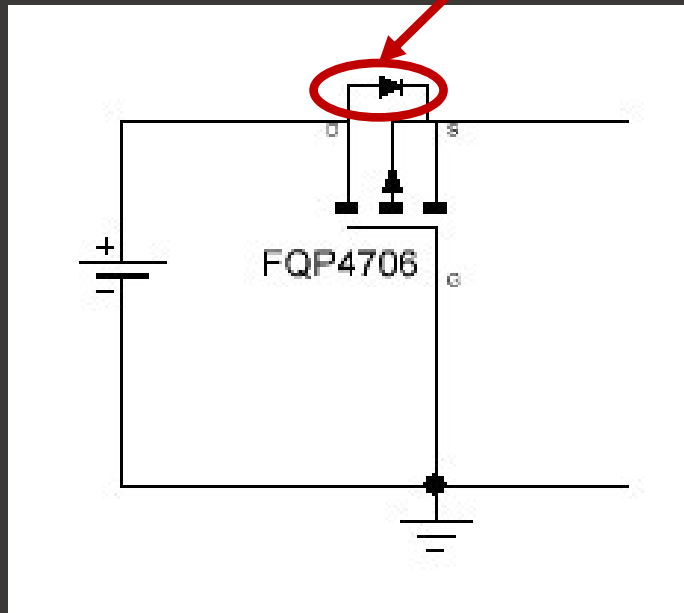During reverse polarity, FET is off and diode blocks current flow



Key Bipolar Transistor Specs

OFF CHARACTERISTICS

Collector – Emitter Breakdown Voltage (Note 2) ($I_C = 1.0 \text{ mAdc}$, $I_B = 0$)	$V_{(BR)CEO}$	40	–	Vdc
---	---------------	----	---	-----

Collector-emitter Breakdown Voltage

- Maximum operating C-E should be 20-50% lower

Collector Current – Continuous	I_C	200	mAdc
--------------------------------	-------	-----	------

Maximum continuous collector current

- You should be below this with some margin ~20%

SMALL-SIGNAL CHARACTERISTICS

Current – Gain – Bandwidth Product ($I_C = 10 \text{ mAdc}$, $V_{CE} = 20 \text{ Vdc}$, $f = 100 \text{ MHz}$)	2N3903 2N3904	f_T	250 300	– –	MHz
---	------------------	-------	------------	--------	-----

f_T – frequency at which gain falls to 1

- Should be $> 100\times$ your operating frequency
- Avoid super high frequency transistors (1GHz!)

Key MOSFET Specs

Characteristic	Symbol	Min	Max	Unit
OFF CHARACTERISTICS				
Drain-Source Breakdown Voltage ($V_{GS} = 0, I_D = 10 \mu A_{dc}$)	$V_{(BR)DSS}$	60	–	Vdc

Drain-Source Breakdown Voltage

- Maximum operating D-S should be 20-50% lower

ON CHARACTERISTICS (Note 1)				
Gate Threshold Voltage ($V_{DS} = V_{GS}, I_D = 1.0 mA_{dc}$)	$V_{GS(th)}$	0.8	3.0	Vdc

Gate threshold voltage

- You should be well above/below this

Static Drain-Source On-Resistance ($V_{GS} = 10 V_{dc}, I_D = 0.5 A_{dc}$) ($V_{GS} = 4.5 V_{dc}, I_D = 75 mA_{dc}$)	$r_{DS(on)}$	– –	5.0 6.0	Ω
Drain-Source On-Voltage ($V_{GS} = 10 V_{dc}, I_D = 0.5 A_{dc}$) ($V_{GS} = 4.5 V_{dc}, I_D = 75 mA_{dc}$)	$V_{DS(on)}$	– –	2.5 0.45	Vdc

On-Voltage (or On-Resistance)

- Should be low enough

MOSFET vs Bipolar Pros/Cons

Bipolar

- Easier to drive voltage-wise
- Rugged

MOSFET

- Can be more efficient
- Can switch faster
- Gate easier to drive current-wise
- Poor selection for 3.3V circuits
- Can be difficult to select proper V_t

Very application dependent:
Switching power supplies
Audio Amplifiers
GPIO LED bias


Practical guidance/tendencies:

- Low power, low voltage -> bipolar
- High current -> FET
- High efficiency switching supplies -> FET

Go-to Transistors

Bipolar – the workhorse for enthusiasts

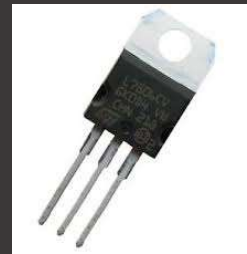- 2N3904 – NPN, 40V, 200mA, 300MHz f_T
- 2N3906 – PNP, -40V, 200mA, 250MHz f_T
- TIP120 – NPN, 60V, 5A





MOSFETs


- Probably don't want to stock FETs
- Wanna play? 2N7000, 2N7002 - NMOS

Common Bipolar Pinouts


TO-92 (Plastic)

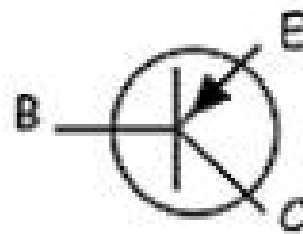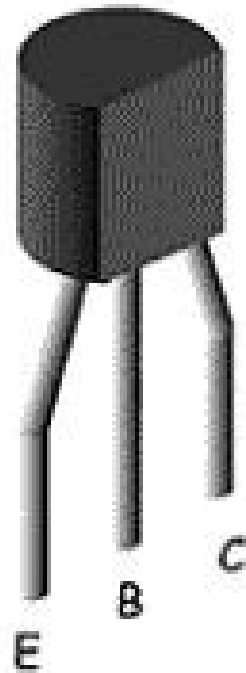



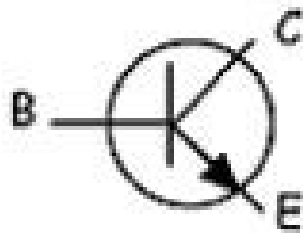



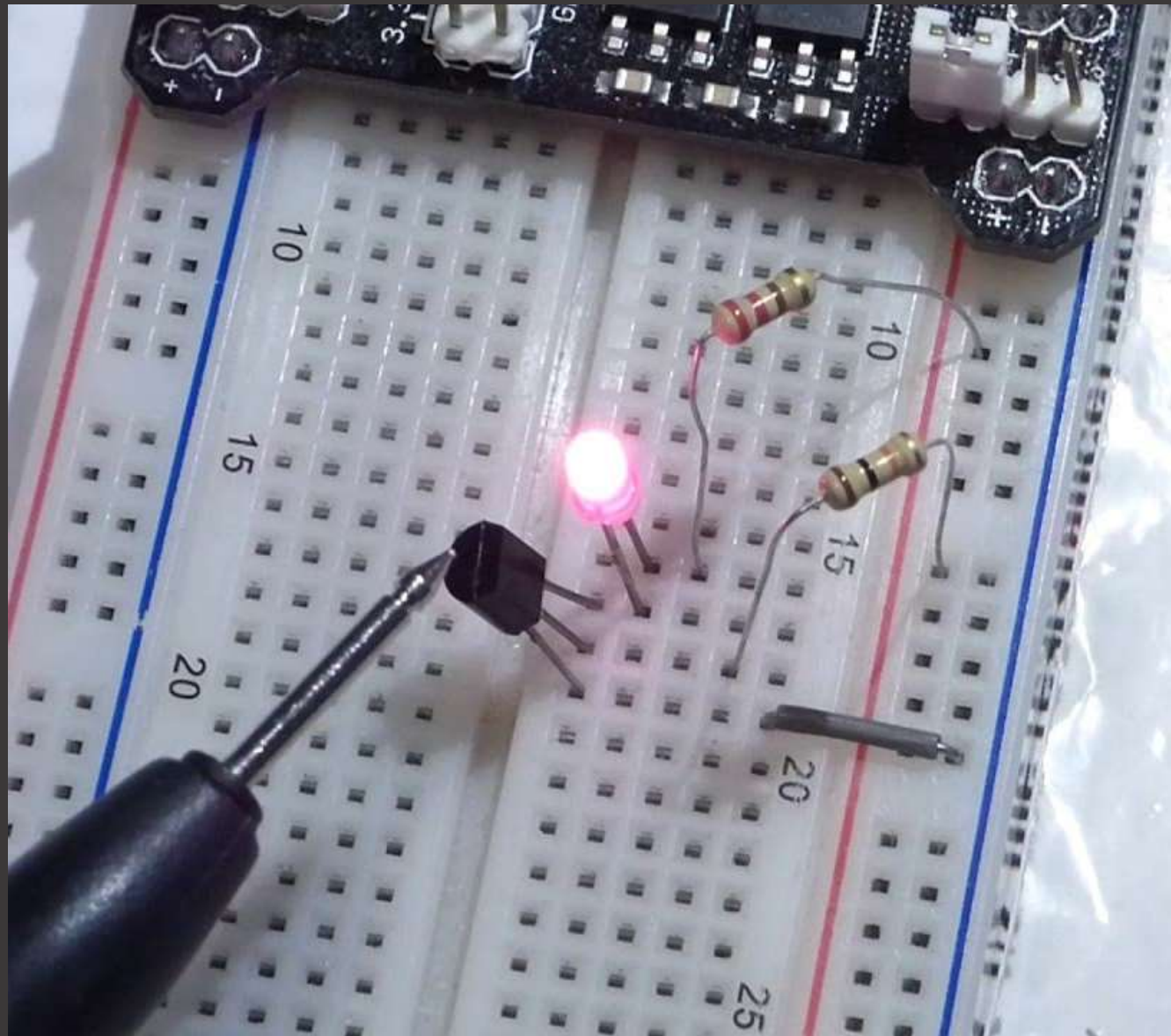

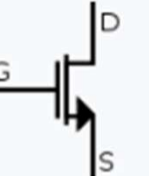

PNP Like 2N3906



NPN Like 2N3904



MOSFET Schematic Symbols

P-channel					
N-channel					
	JFET	MOSFET enh.	MOSFET enh. (no bulk)	MOSFET dep.	

- There are many, many variations on these
- FETs of the same type (P vs N) behave similar to each other
- Be aware but don't fret over it too much


And now
for something
completely different...




Transistors as Amplifiers

A Linear Amplifier


[Falstad Simulation](#)

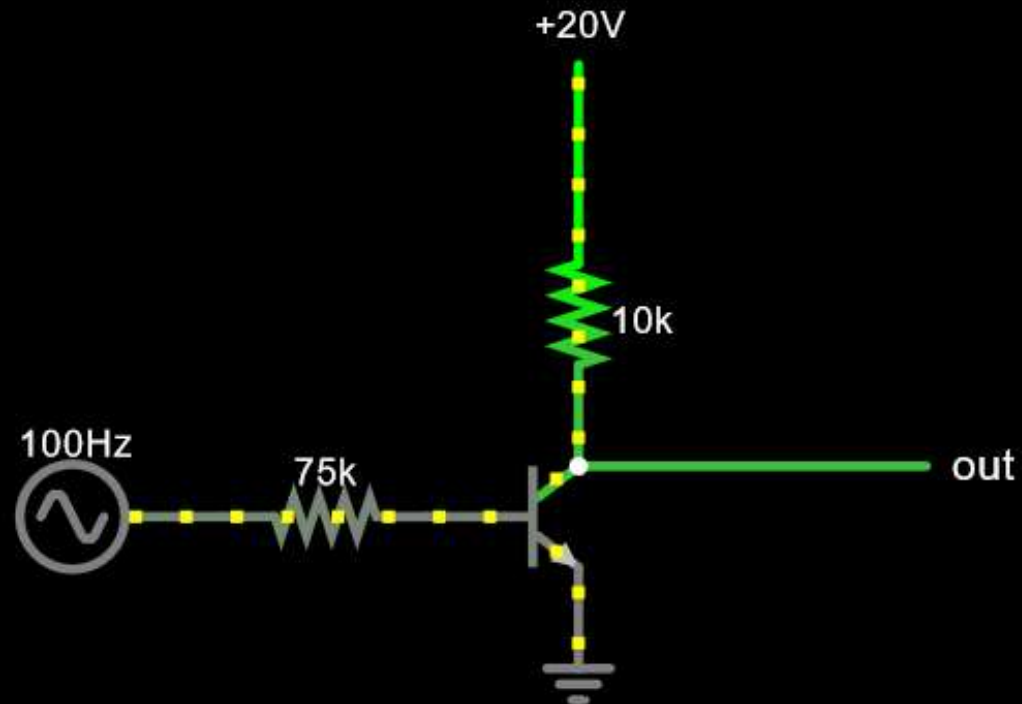

H=5 ms/div ●=2 V/div

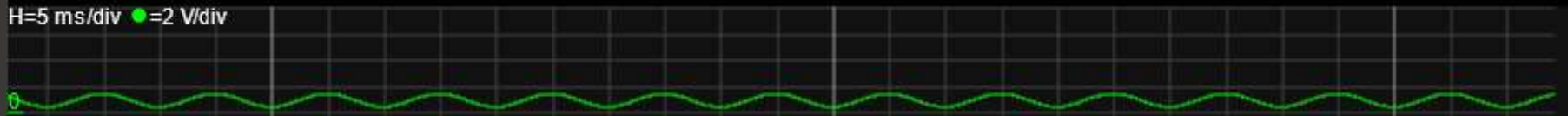


H=5 ms/div ●=2 V/div

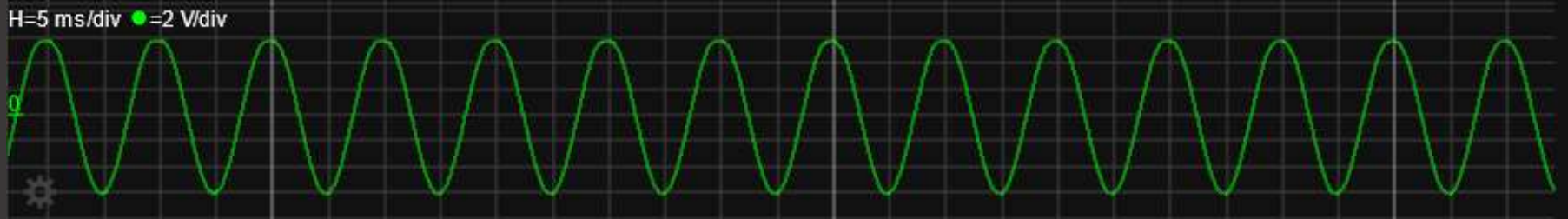

Not a good design


[Falstad Simulation](#)

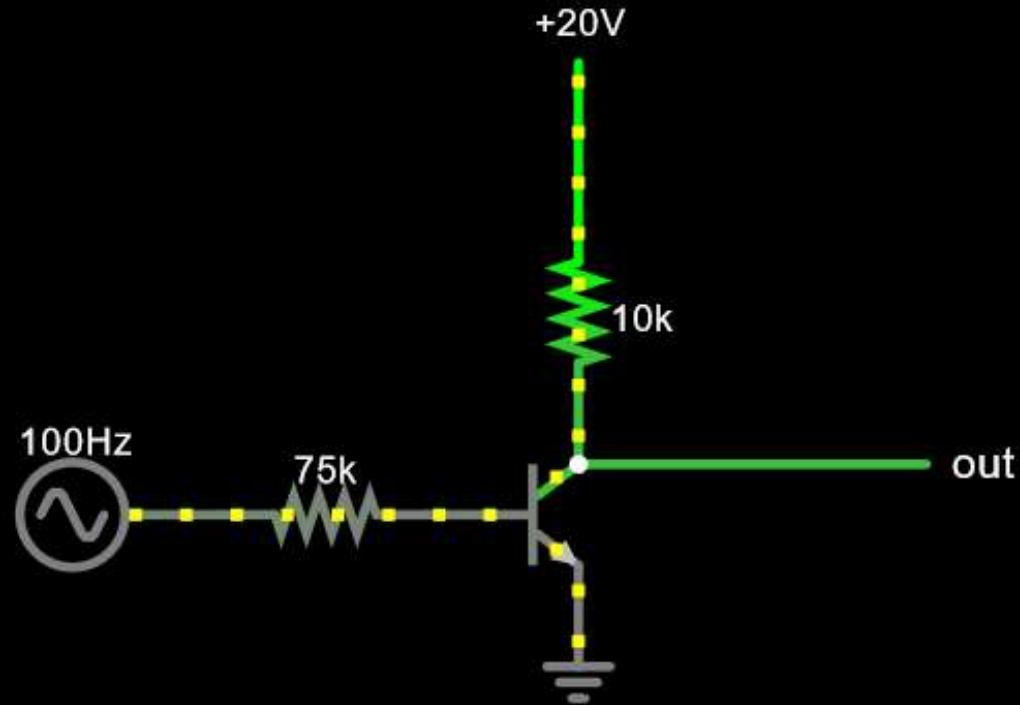

Problems


- Gain will vary too much with β (h_{fe}) variation
- Linearity isn't very good
- Input dynamic range is poor
- Circuit needs fine-tuning per transistor used

A Better Design

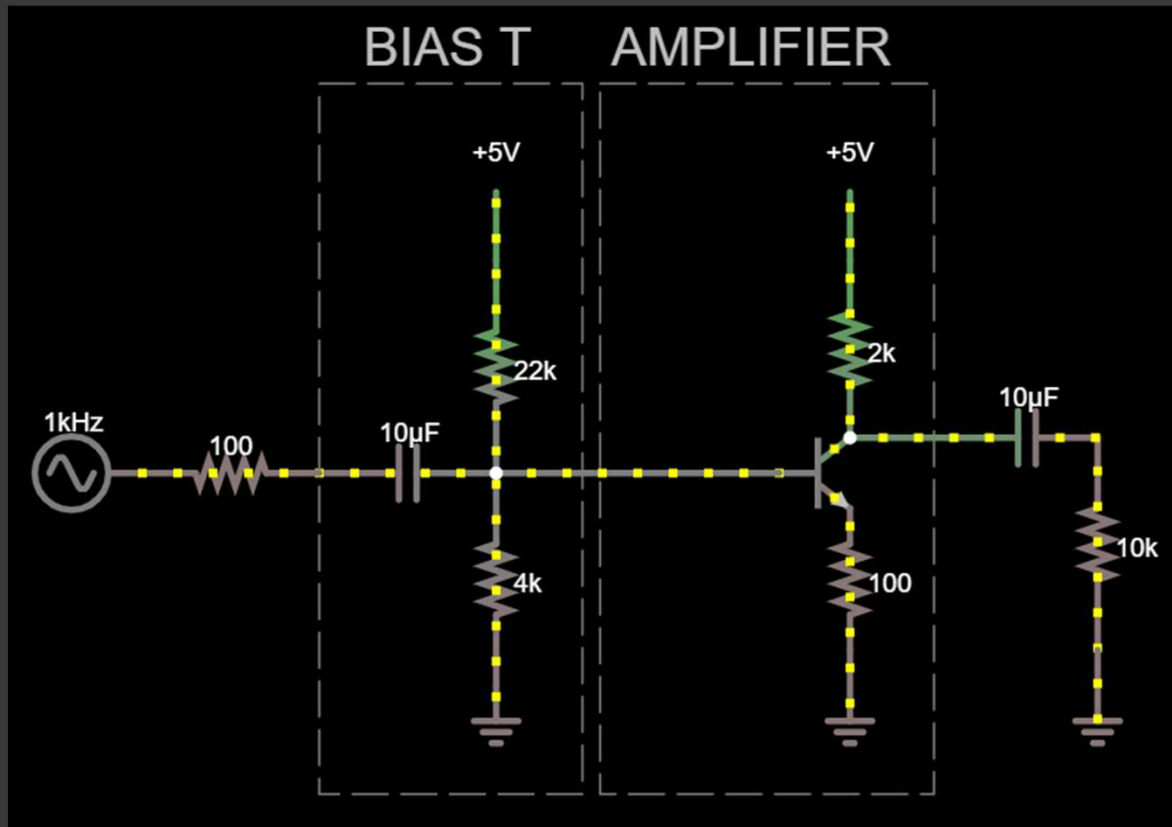



- Gain $\sim -R_c/R_e$
- Improved distortion
- Improved dynamic range
- Less sensitive to individual transistor characteristics

Common Configurations

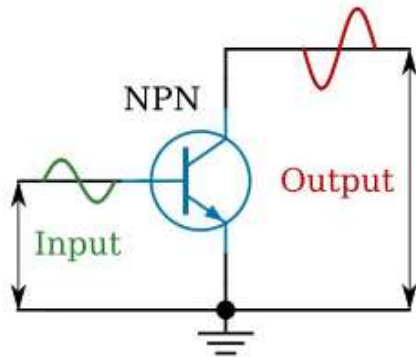



(A)

Common emitter

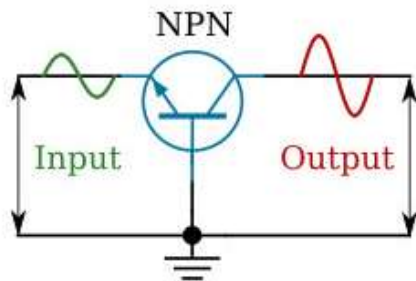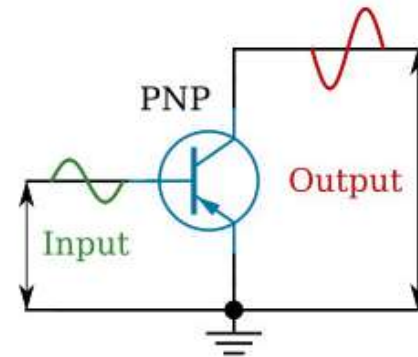


(B)

Common base

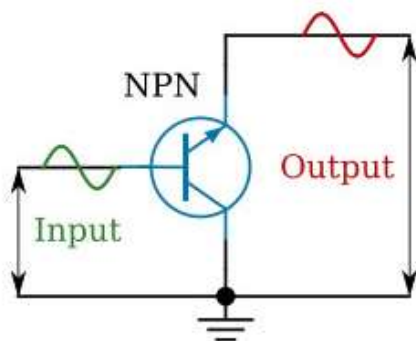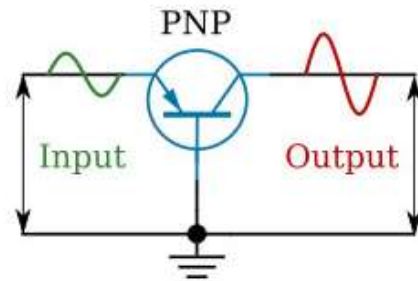

(C)

Common collector

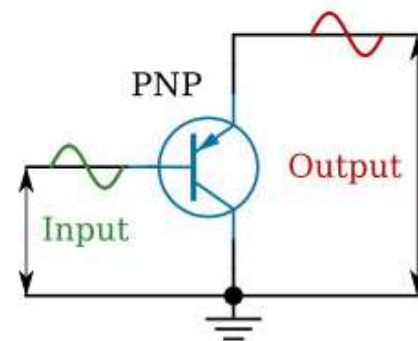


V and I gain
Low input R
Low output R

V gain
Low input R
High output R



I gain
High input R
Low output R

Darlington Pair


Gain is squared
(100 becomes
10,000)

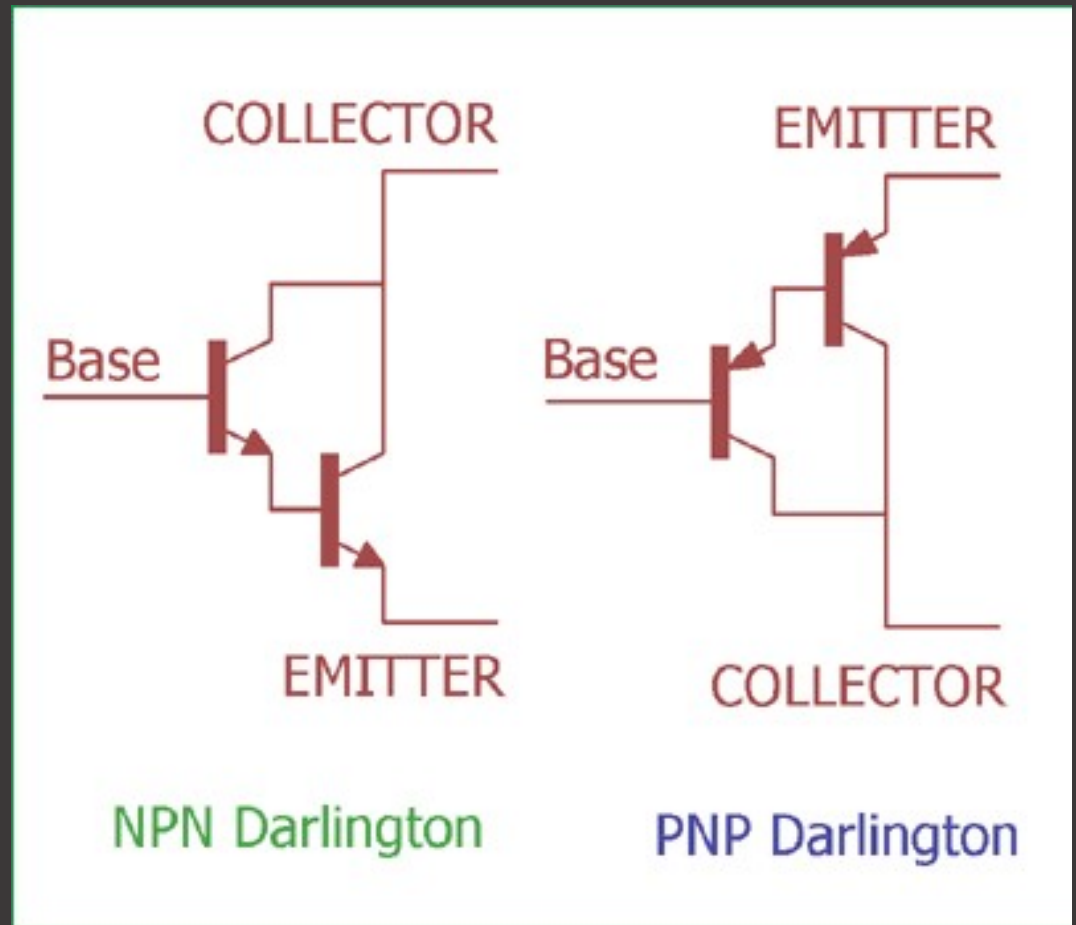

Differential Pair

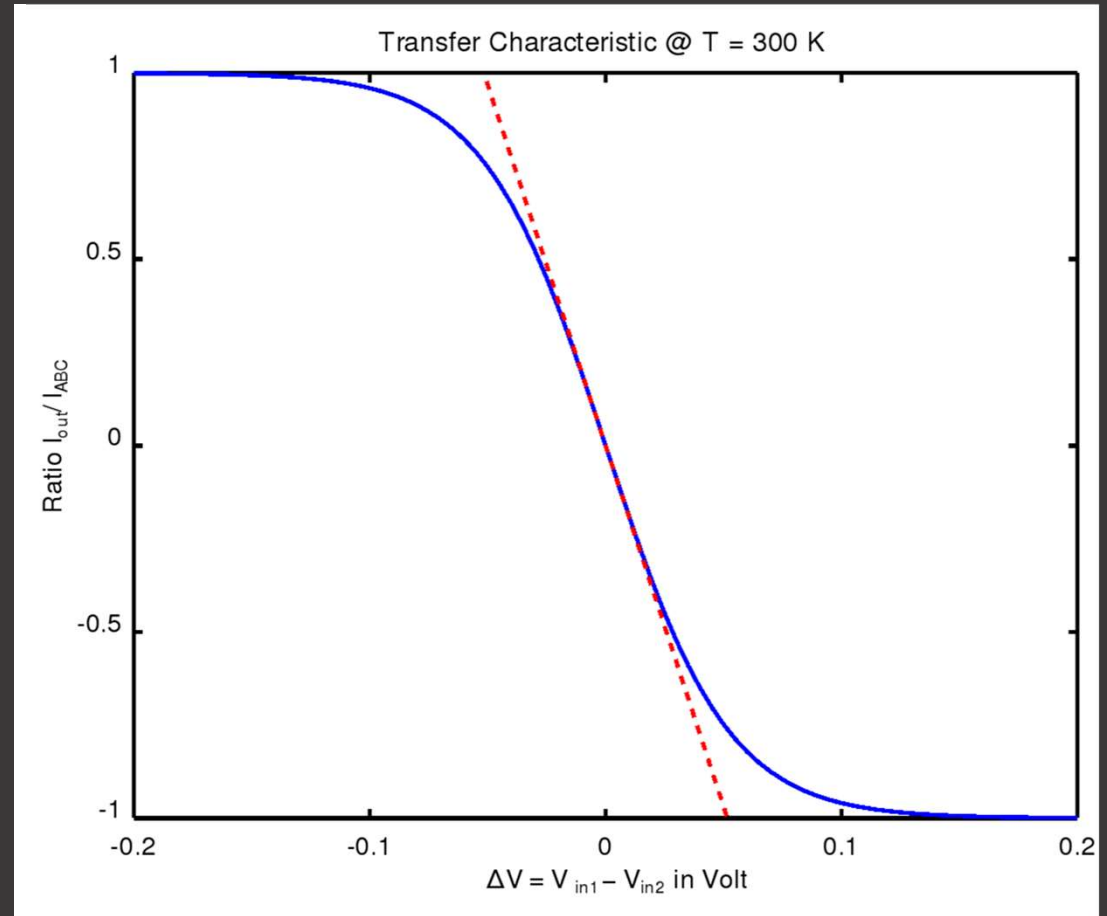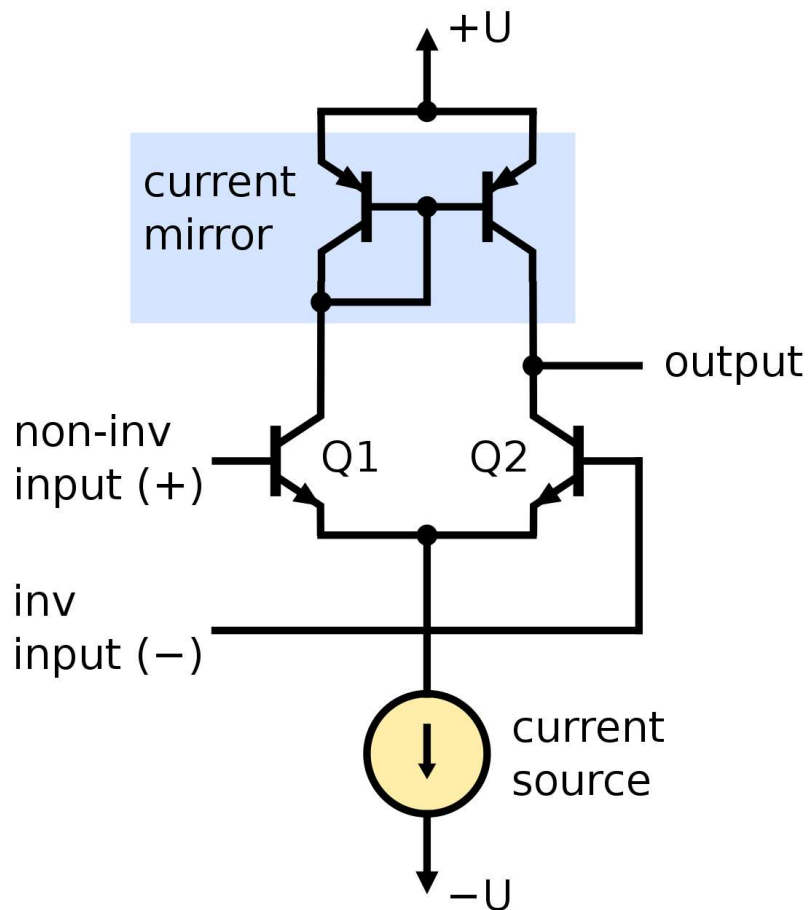

Simple Op-Amp

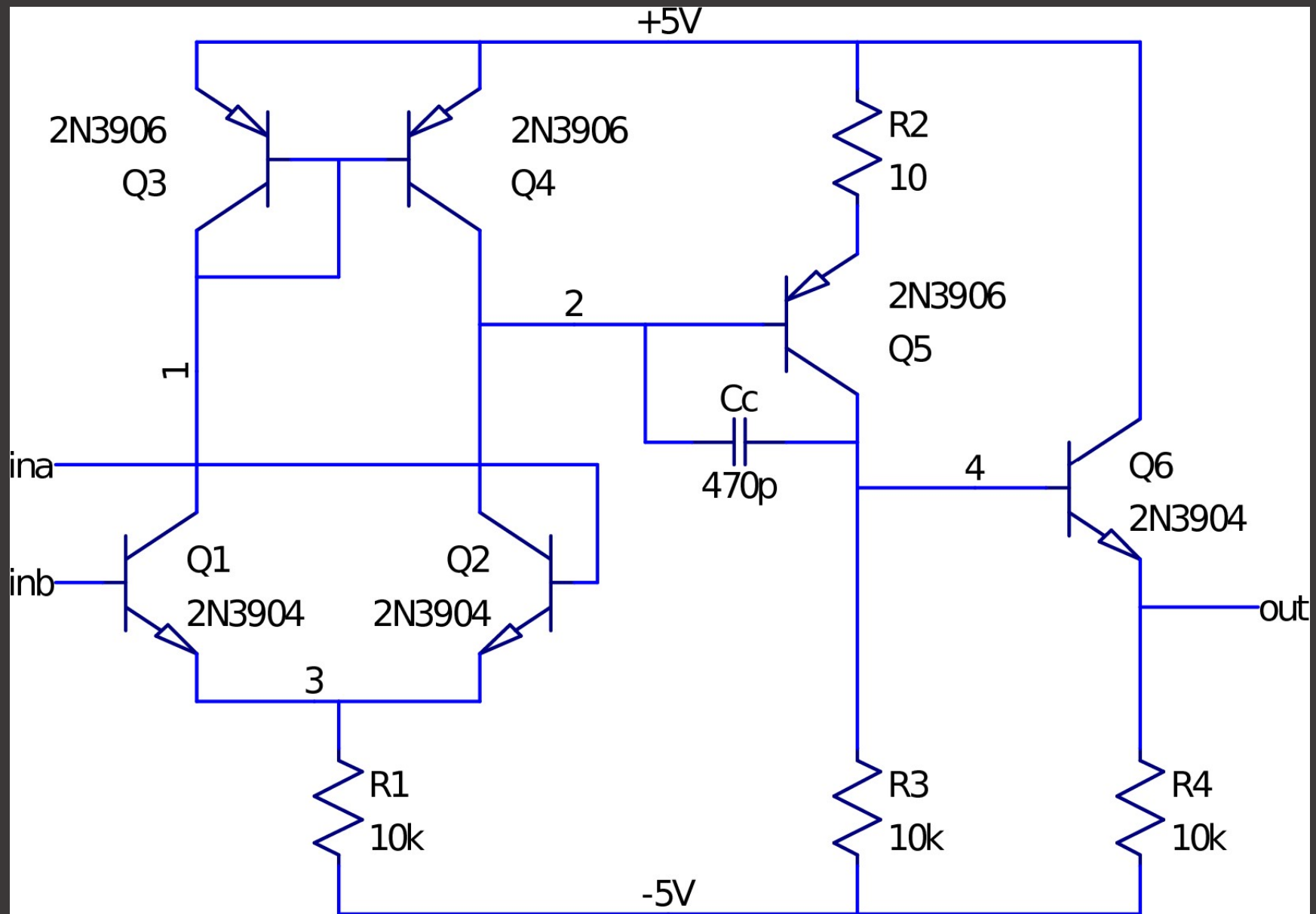

Simple Op-Amp Usage

Simple circuit
Near ideal
performance

