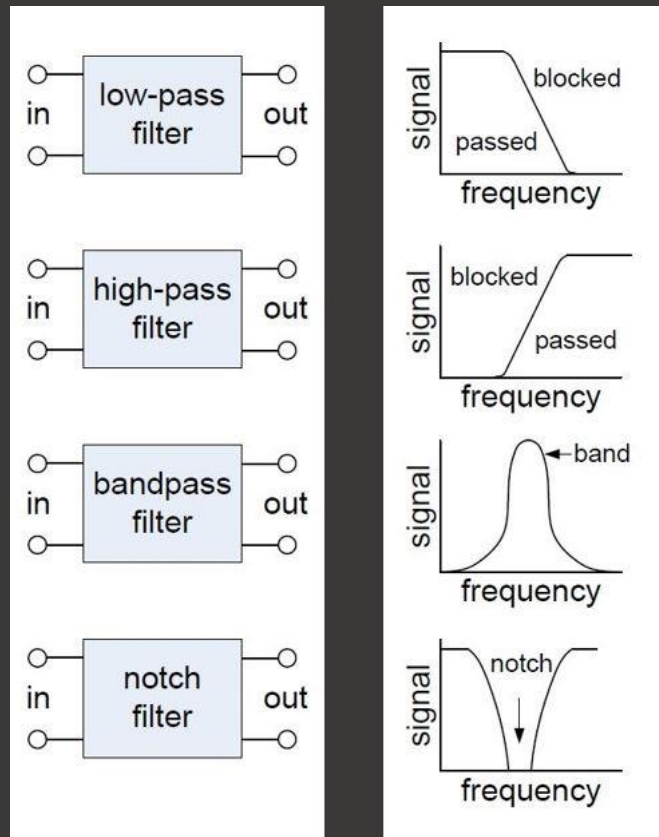


# Filtering and Working in the Frequency Domain

Mar-2019





# Tonight

---


1. Quick Review
2. Look at 38.5kHz PWM filter slides
3. Breadboard/test filter

# Time vs Frequency Domain

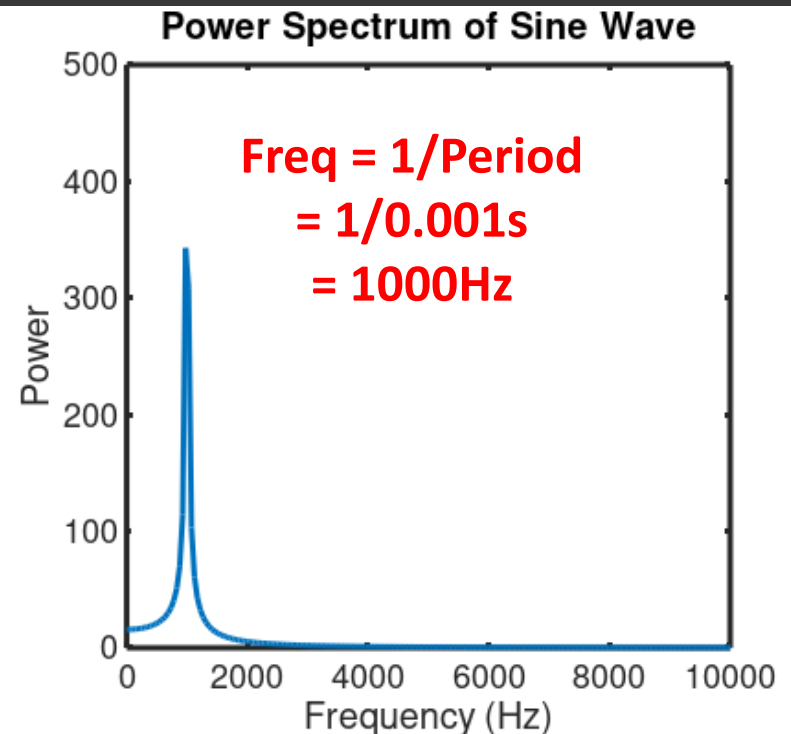
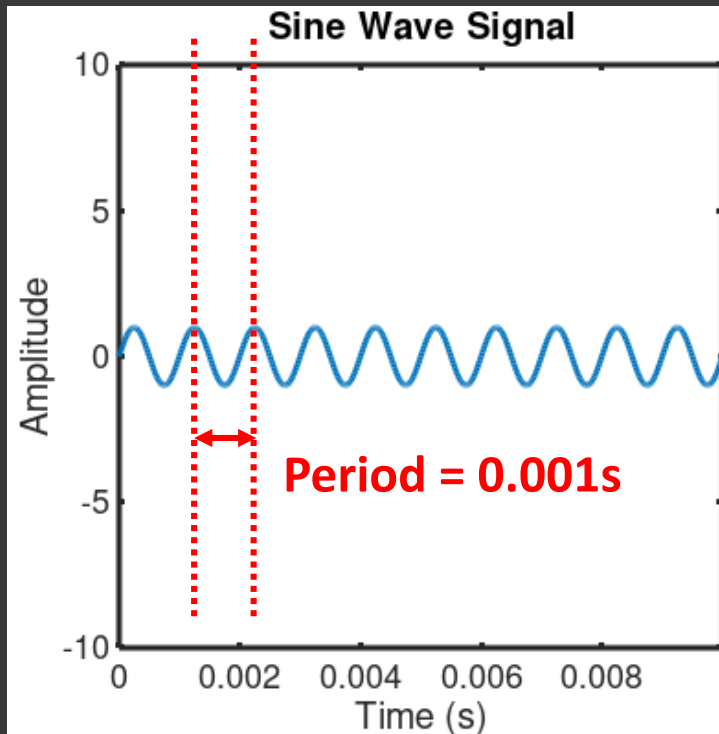


$$\text{Frequency} = 1 / \text{Period}$$

# Square Wave = Odd Harmonics

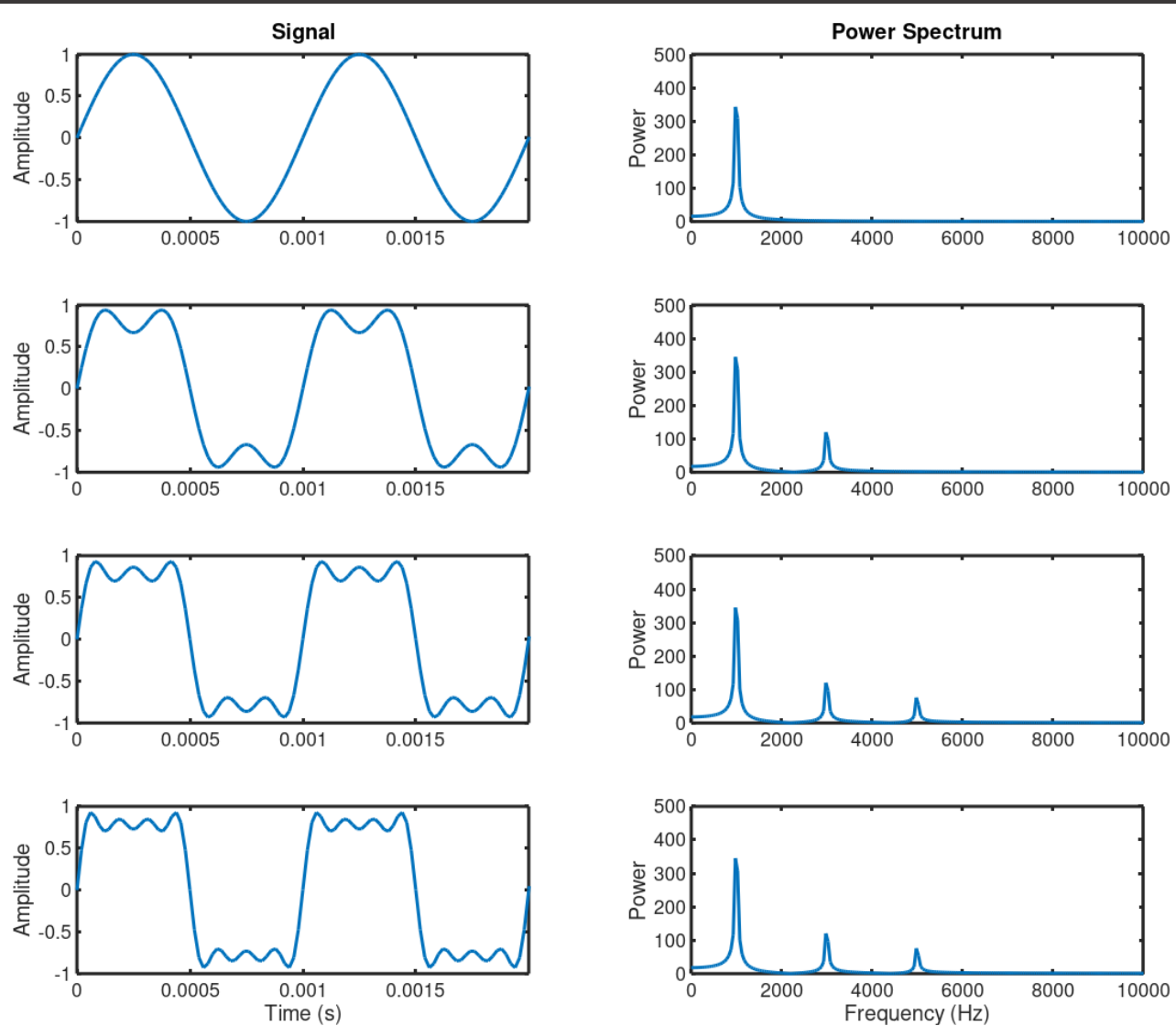

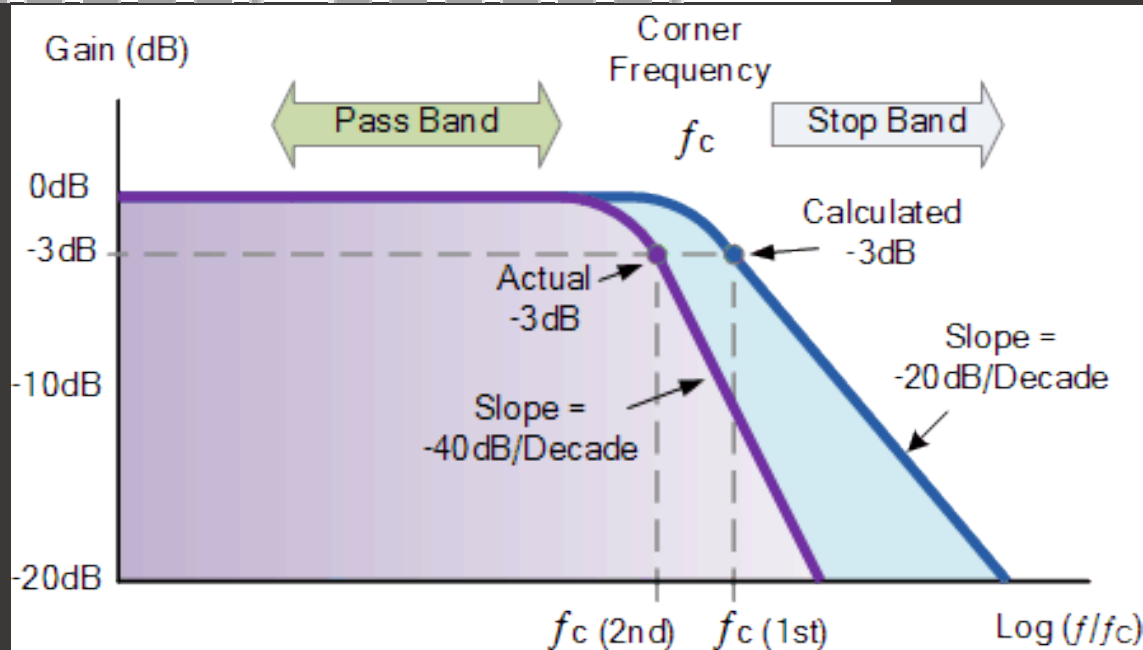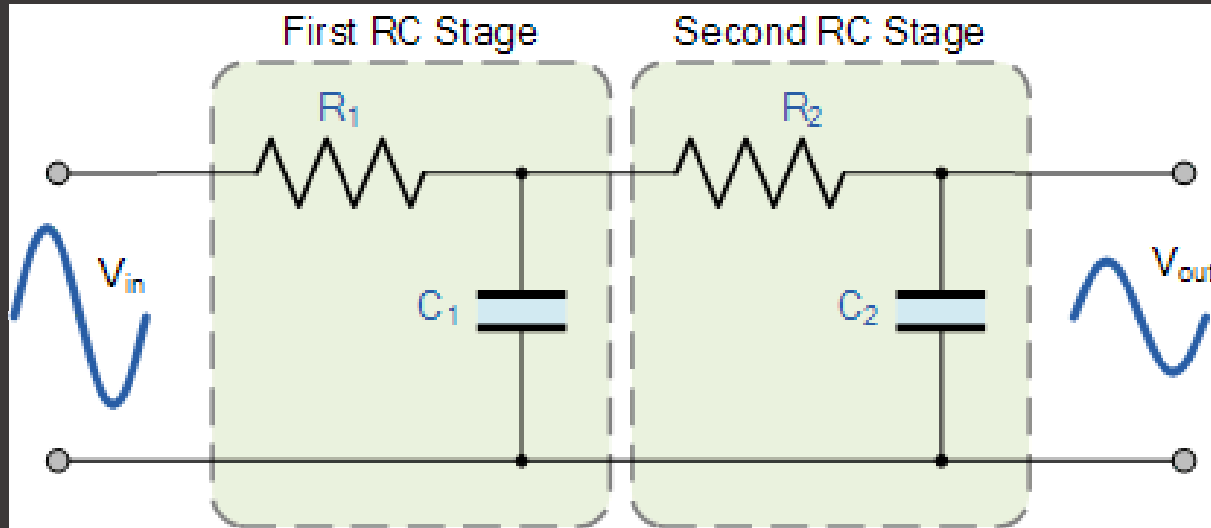
# 1<sup>st</sup> and 2<sup>nd</sup> Order Low Pass Filters





# A Conceptual Low Pass Filter

All-pass

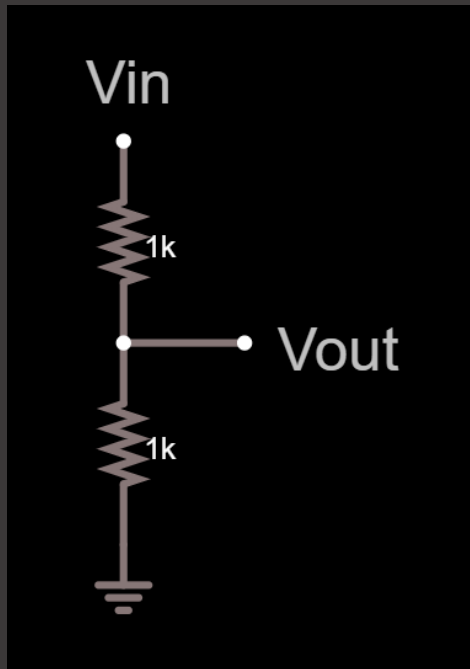

Low-pass

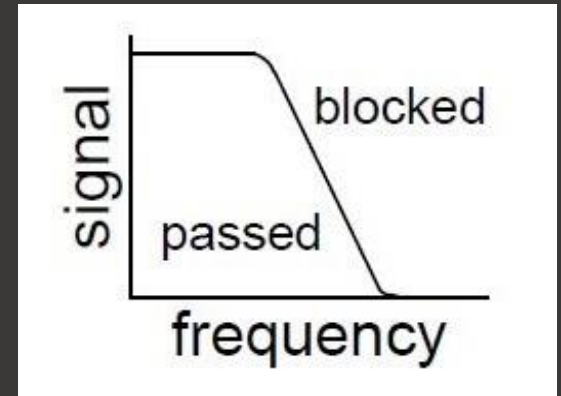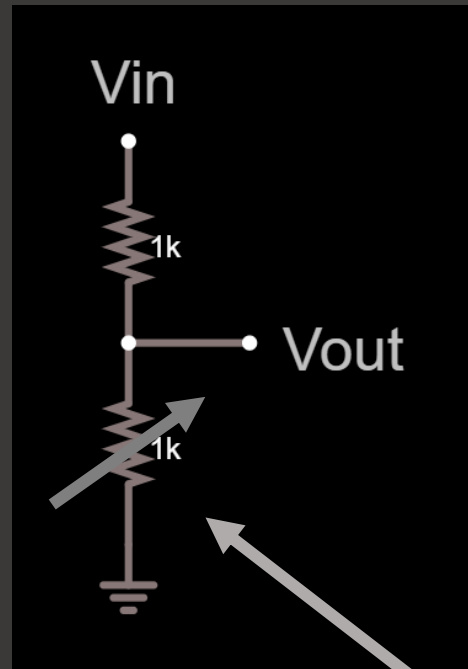


Decreases with  
frequency

# RLC Components vs Frequency


DC Resistance/  
AC Reactance

Change w/ freq?

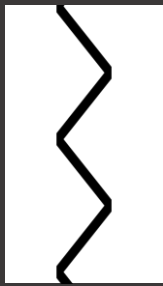


$R$

$=$

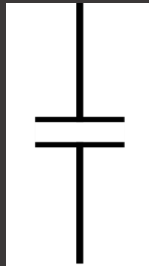

$$X_C \propto \frac{-1}{fC}$$

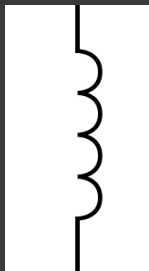


$$X_L \propto fL$$




# RC Filters


## All-Pass

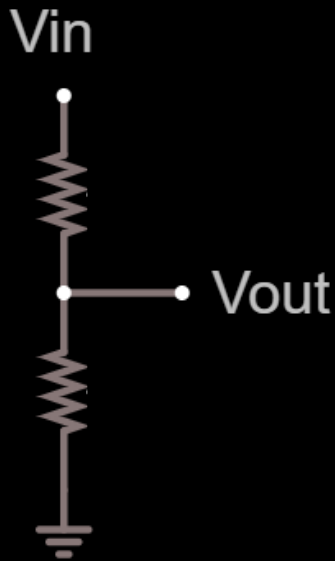



## Low-Pass

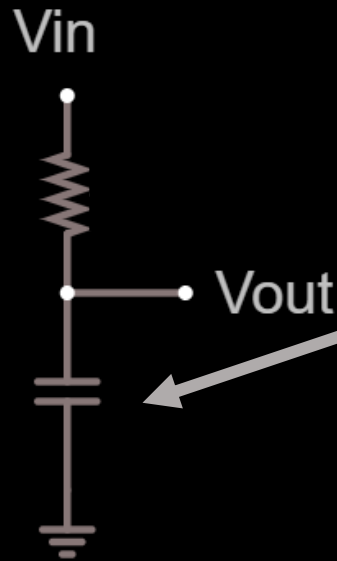

## High-Pass

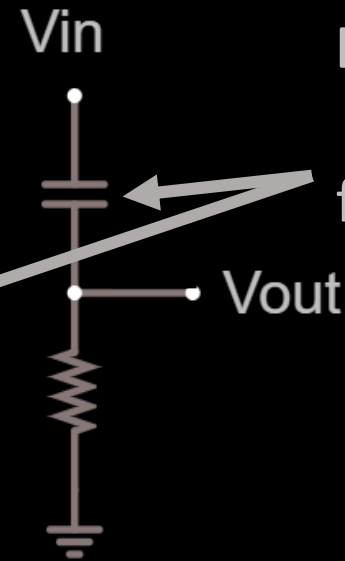


Decreases  
with  
frequency

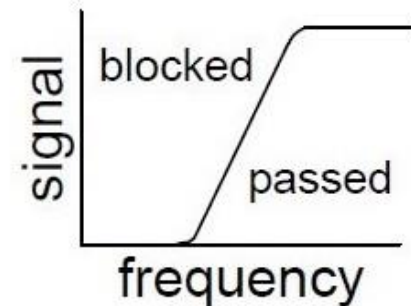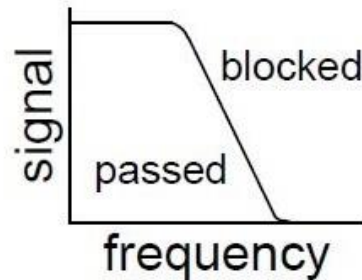




# Other filter topologies

## Common Mode Choke

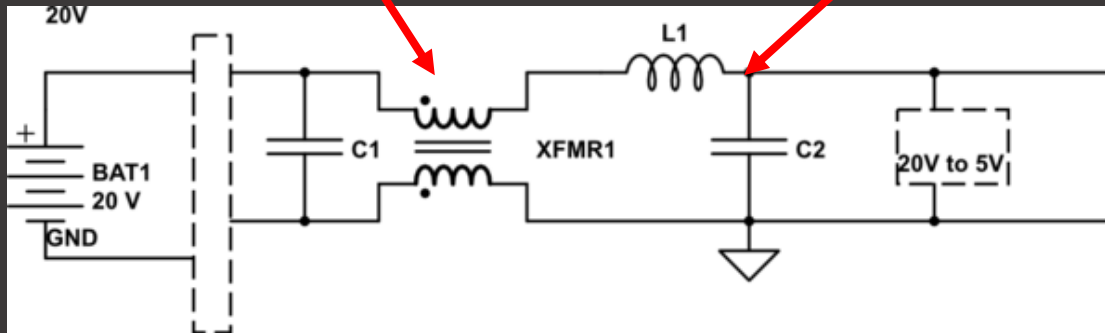


2<sup>nd</sup> order LC filter

## 2<sup>nd</sup> order active filter

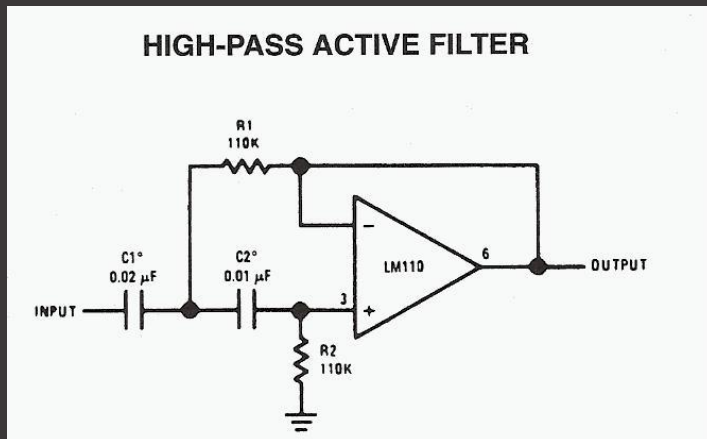


## 11<sup>th</sup> order LC filter

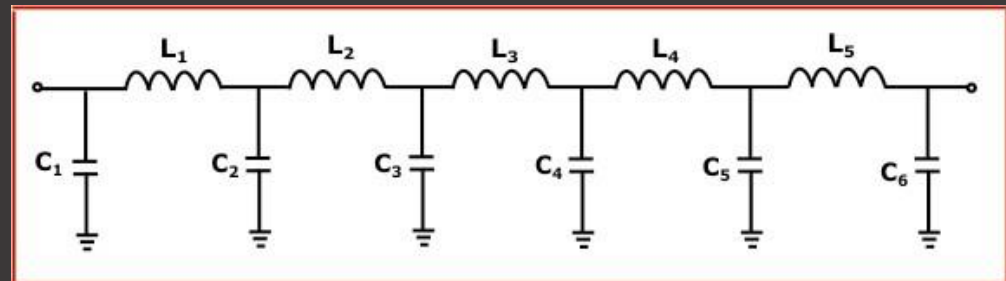

# Other filter topologies
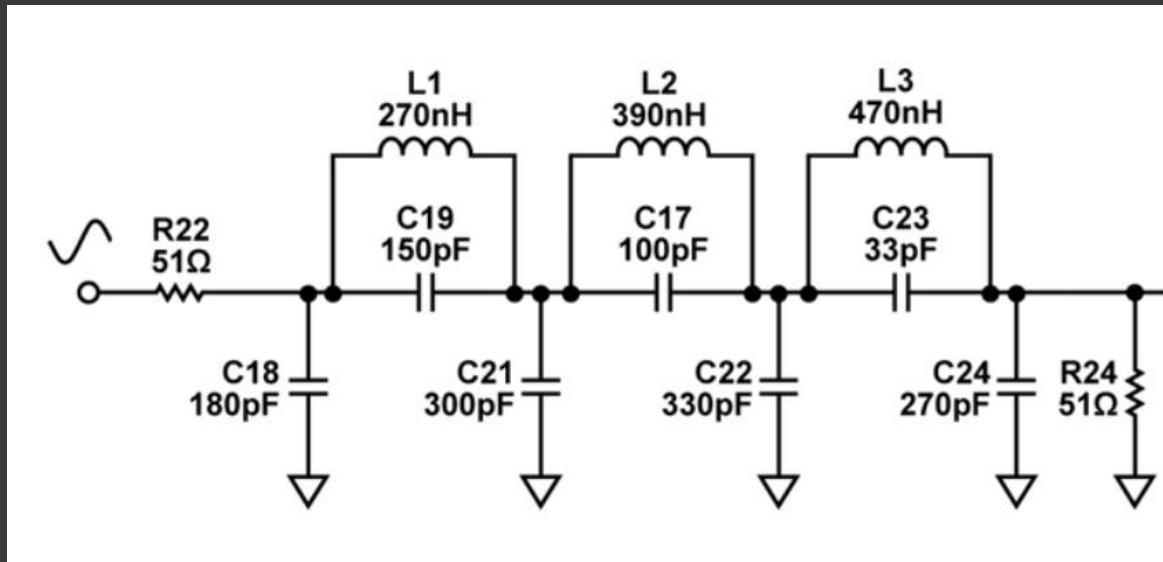
## 7<sup>th</sup> order elliptical filter





2<sup>nd</sup> order active filter


11<sup>th</sup> order LC filter

# Crystal Bandpass Filters

## 4 pole crystal filter

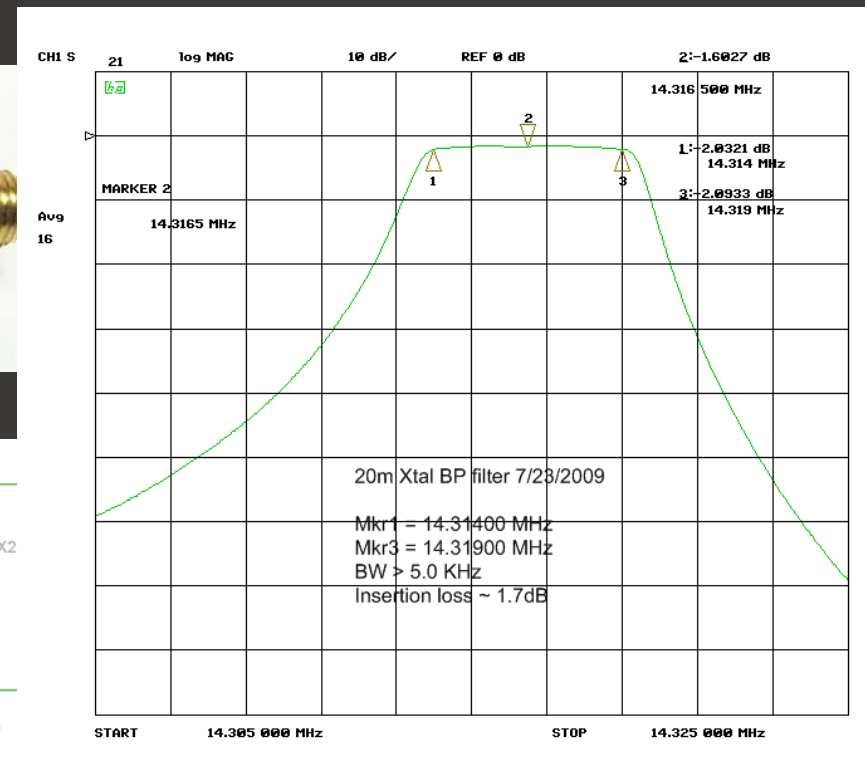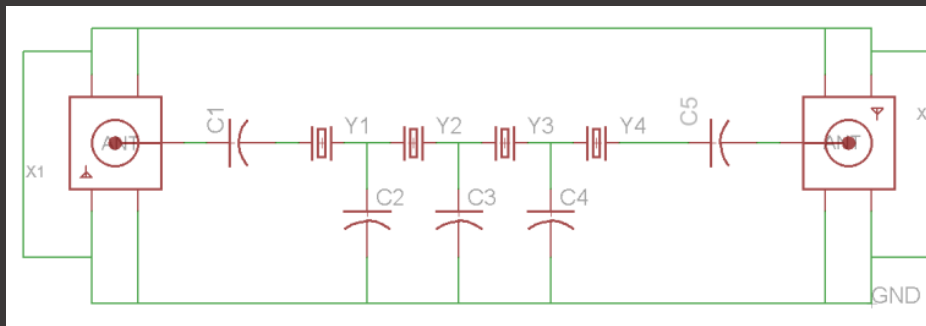

# PWM Freq Components

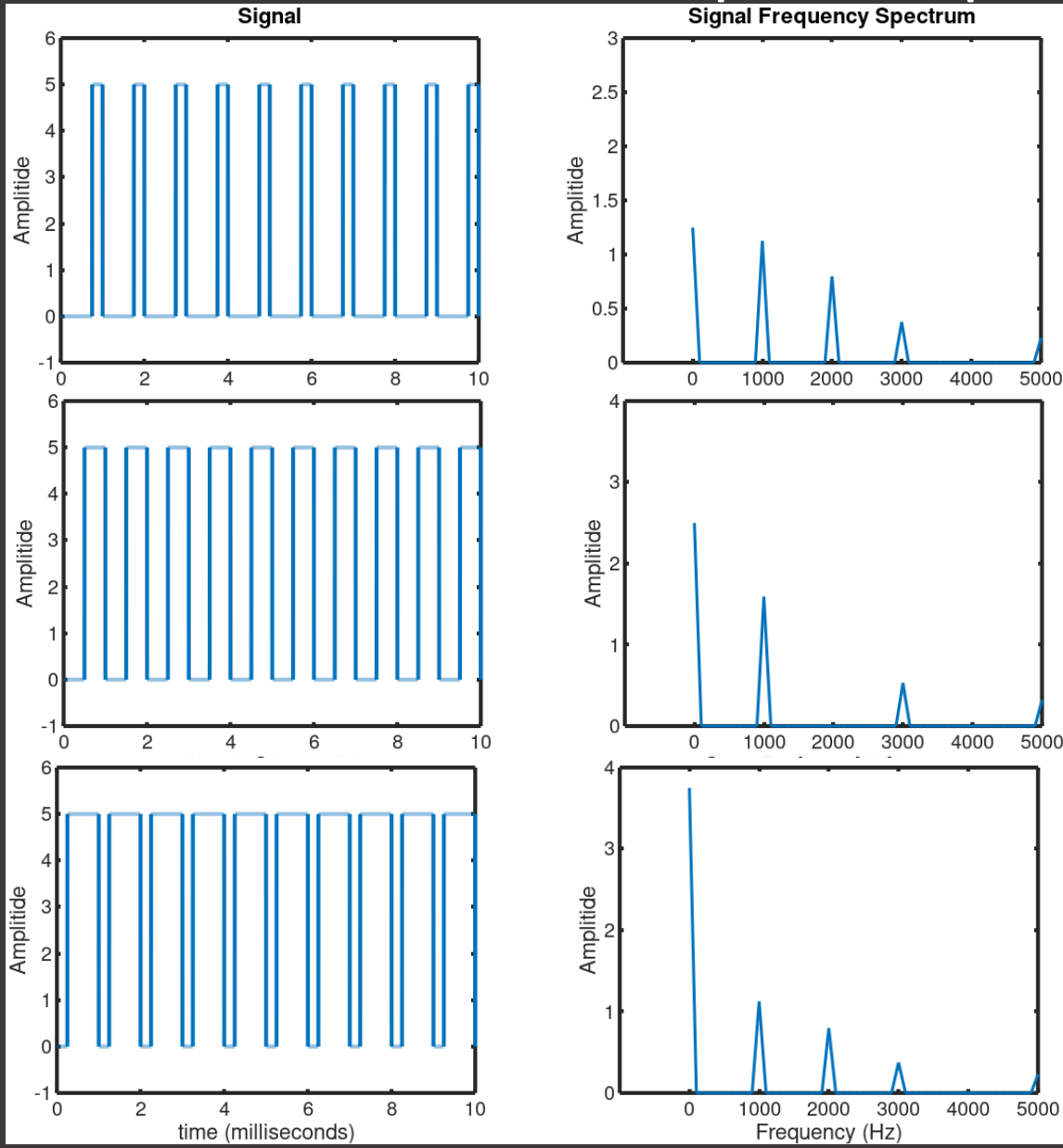


25% Duty Cycle

50% Duty Cycle

75% Duty Cycle


# Example PWM Filters

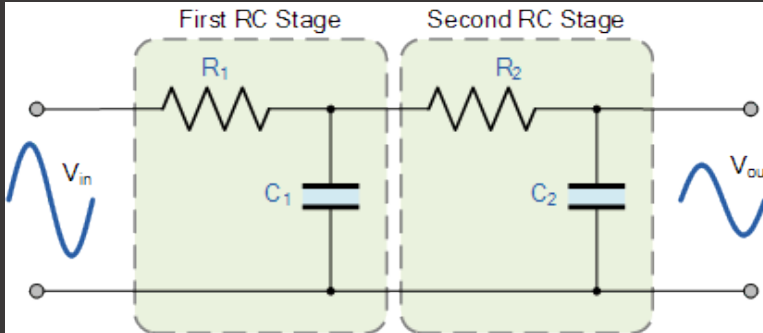


$$R1 = R2 = 470 \text{ Ohms}$$

$$C1 = C2 = 0.1 \mu\text{F}$$

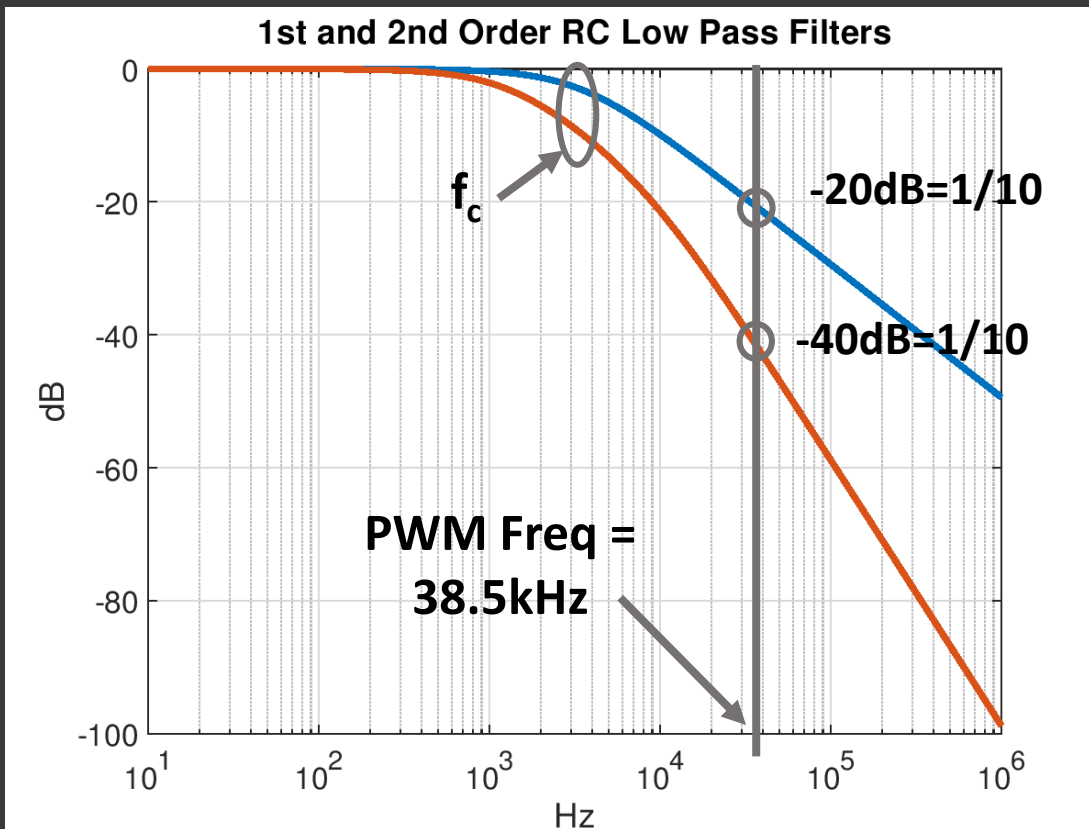
$$1^{\text{st}} \text{ order } f_c = 1/(2\pi RC) = 3.39\text{kHz}$$




# PWM Signal – 4%, 50%, 98%

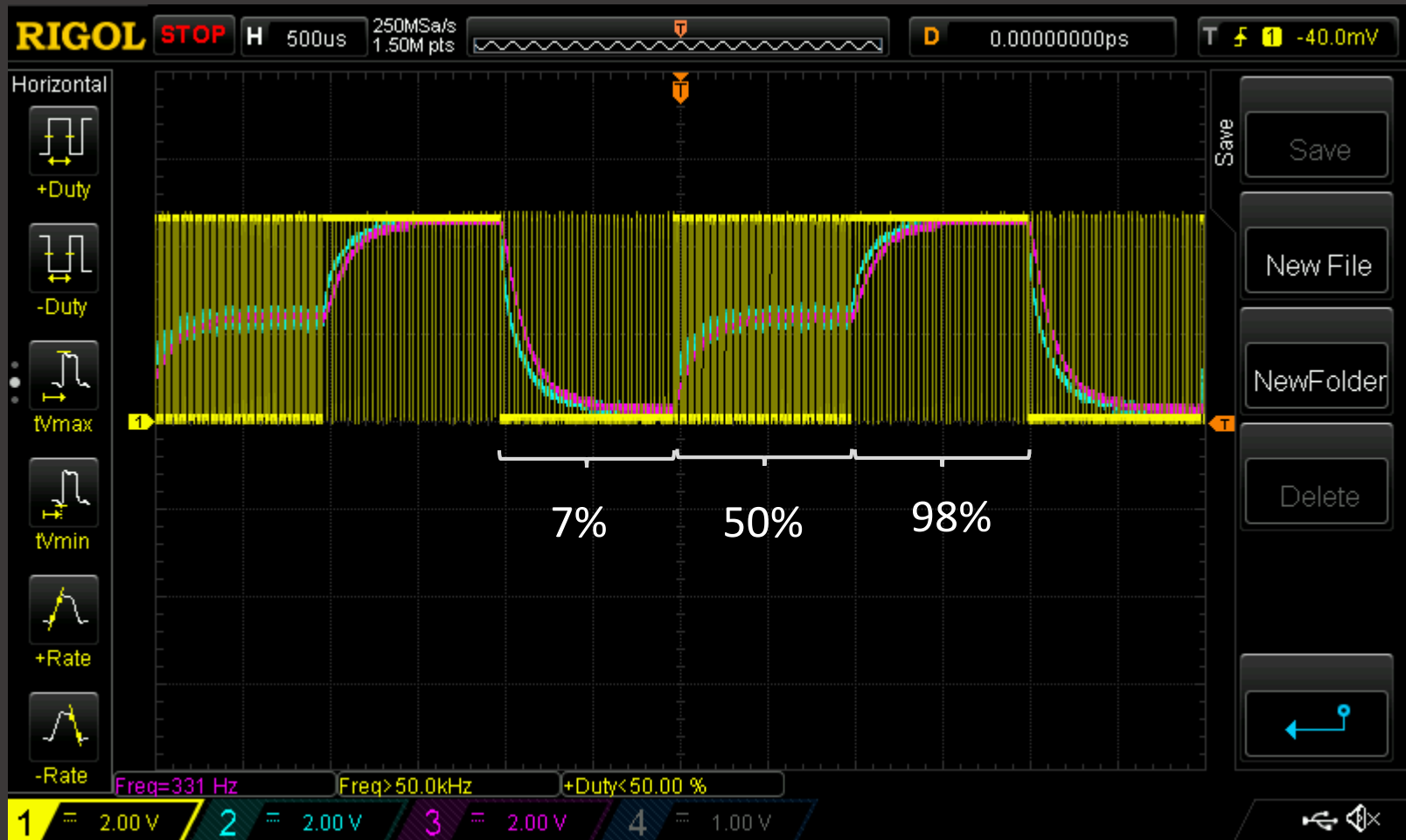

# PWM Signal – 50%

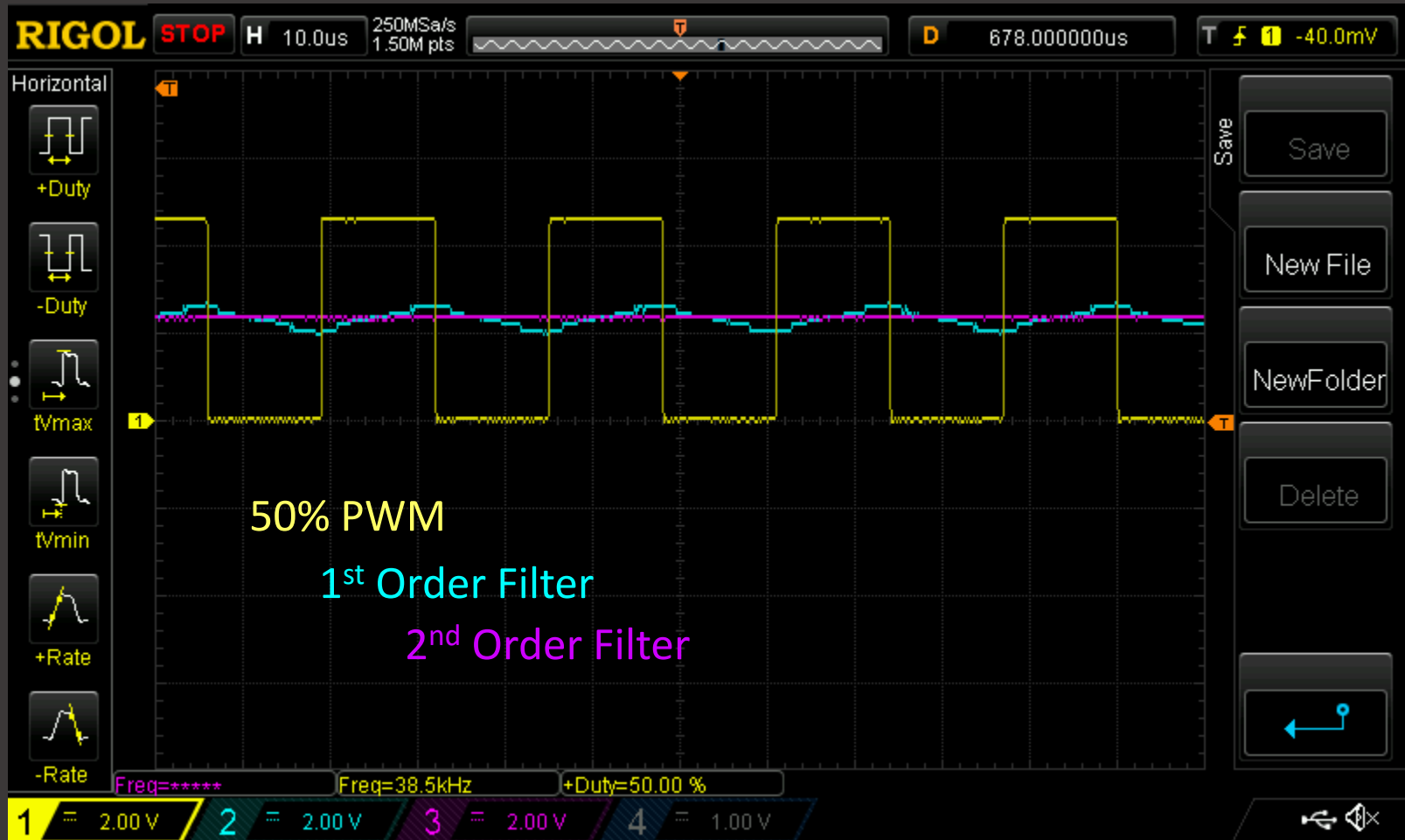

# PWM Signal – 4%

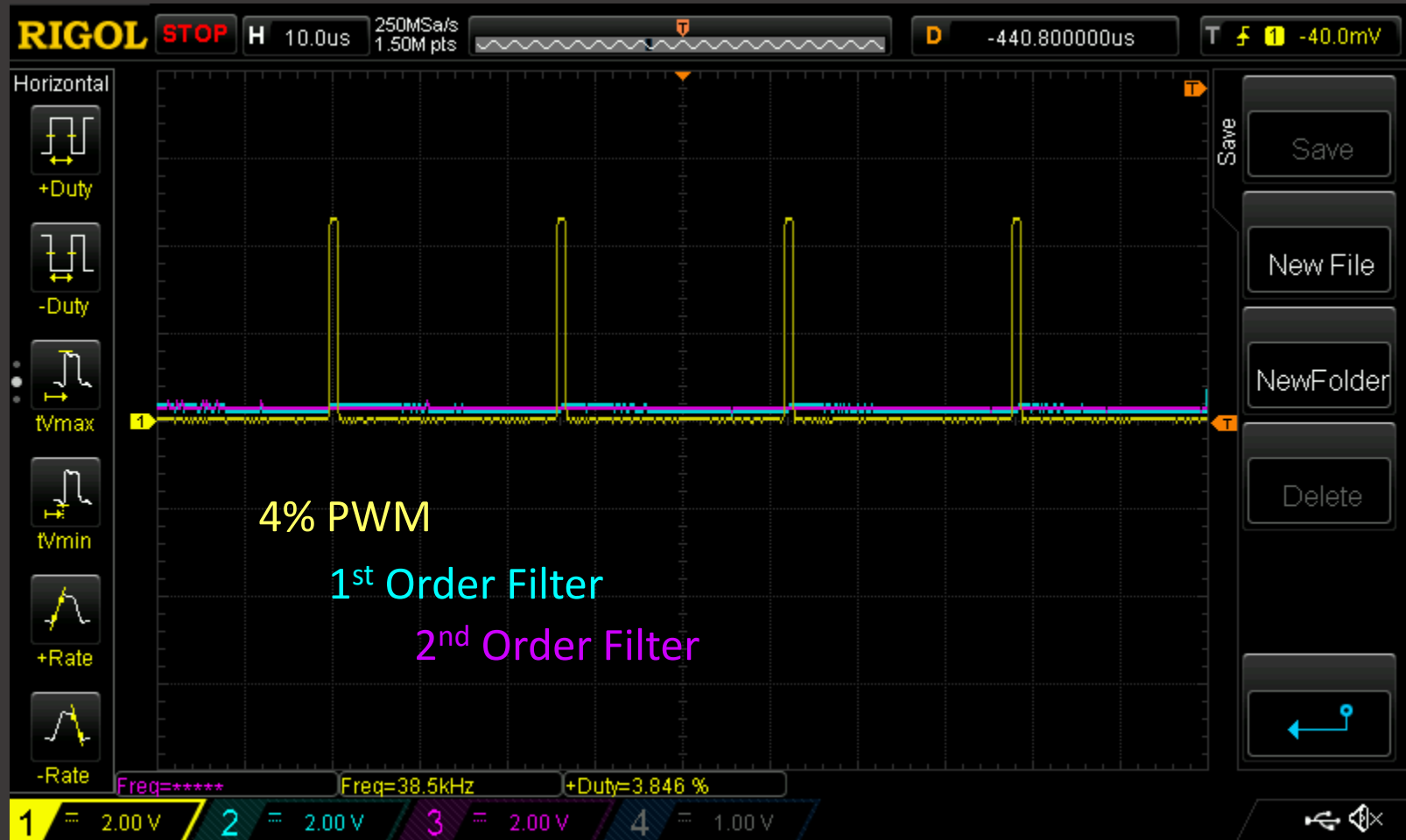



# PWM Transition – 98% to 4%

