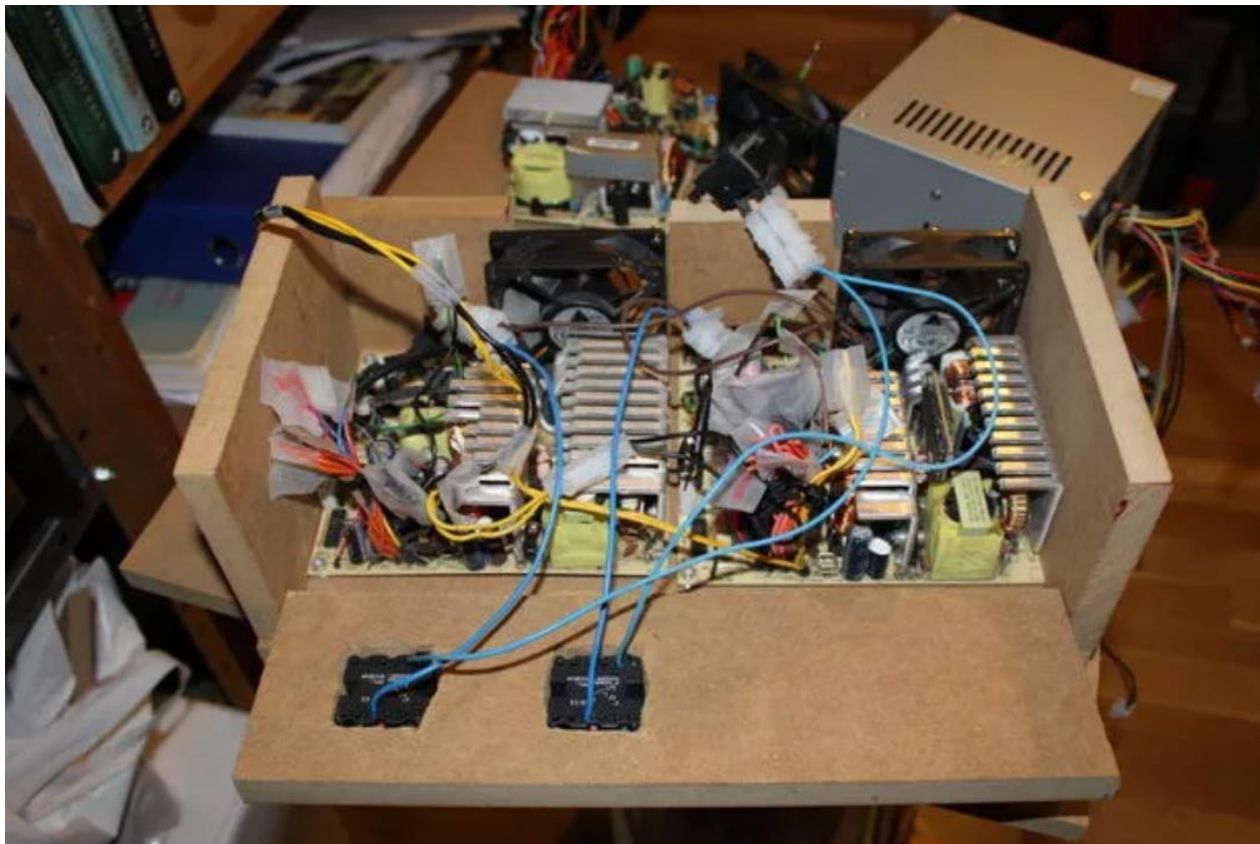



Power Supplies 101

DC-DC Converters




10-Feb-2018



Using Fixed Voltage Linear Regulators

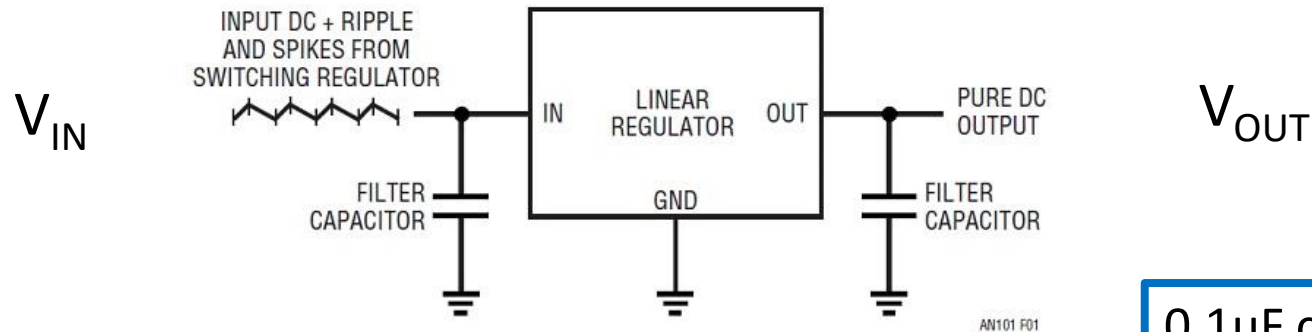


LM7805 PINOUT DIAGRAM

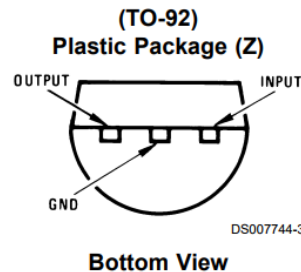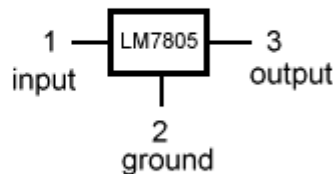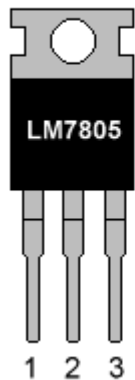

0.1uF ceramic caps are good, easy choices

Try a 1uF electrolytic, too, watch polarity!

Using the LM317 Adjustable Regulator

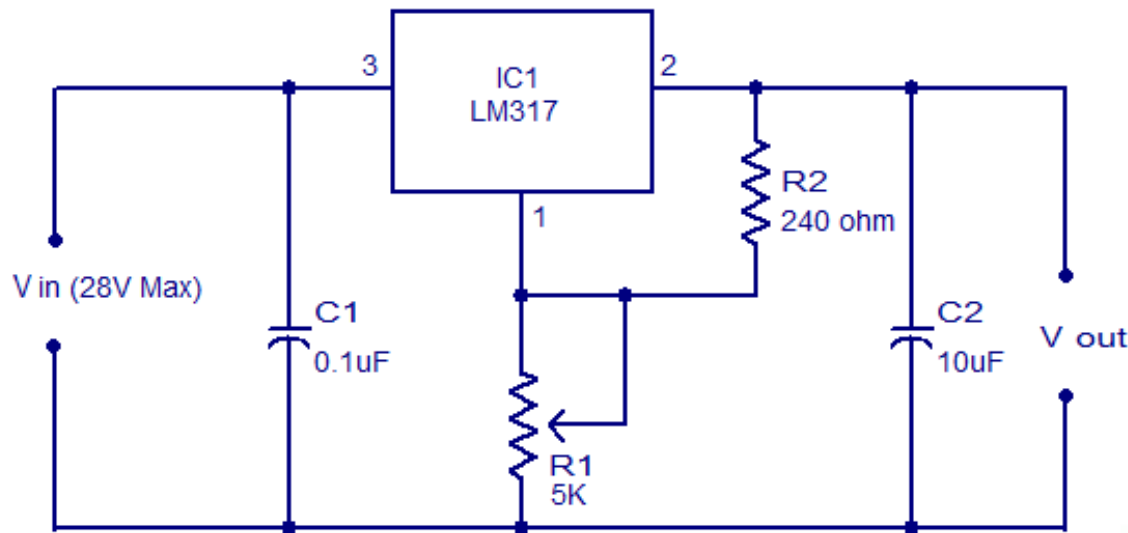


Typical adjustable regulator using LM317

www.circuitstoday.com

$$V_{out} = 1.25V (1 + (R2/R1)) + (I_{adj} \times R2)$$

Vout (Volt)	R2 (Ohm)	R1 (Ohm)
12.00	860	100
9.00	620	100
6.00	380	100
5.00	300	100
3.00	140	100
1.50	20	100

LM317
Pin Arrangement

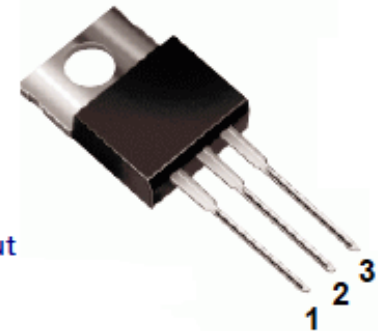


1. Adjust

2. Vout


3. Vin

Heatsink is connected to pin 2

(TOP VIEW)

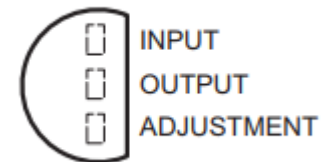


Using the LM1117 Adjustable Regulator

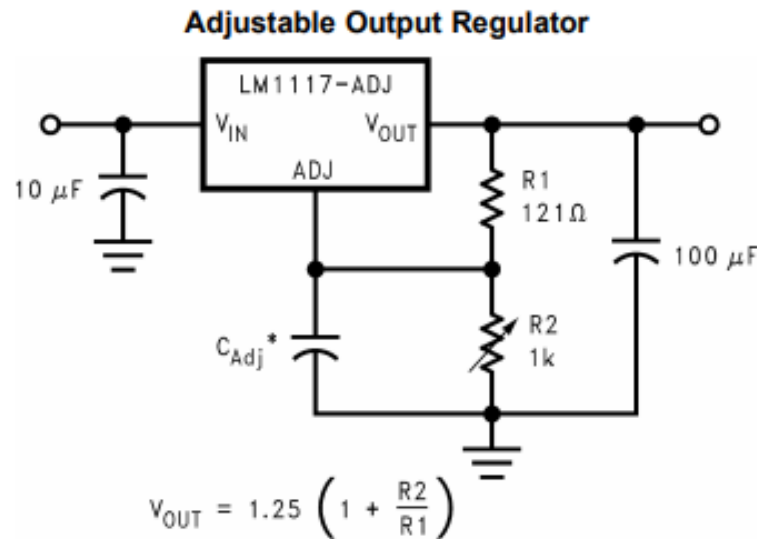


* C_{Adj} is optional, however it will improve ripple rejection.



Voltage	R1	R2	Error	Use
3.3V	1.2k	1.8k	3%	3.3V IC
5V	270	820	2%	5V IC
6V	180	680		Servos
9V	560	3.3k	2%	
12V	510	4.3k	1%	
15V	62	680	1%	
24V	560	10k	1%	

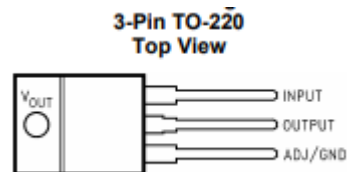

Zener Supply

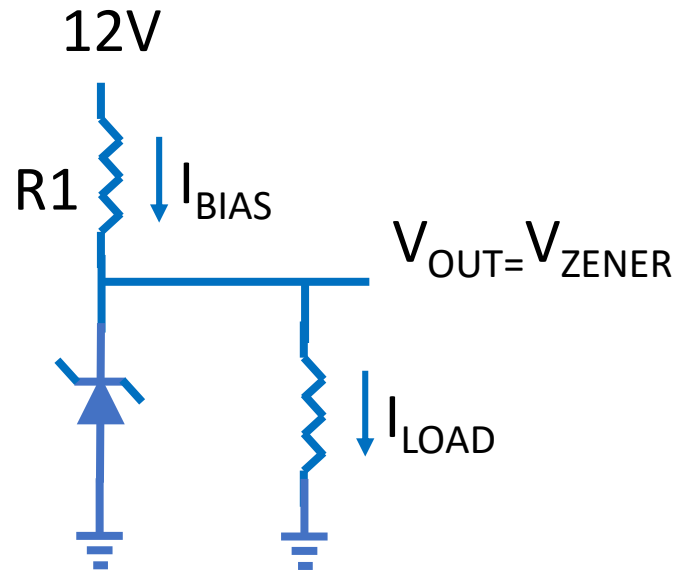

Zener with Transistor Supplies

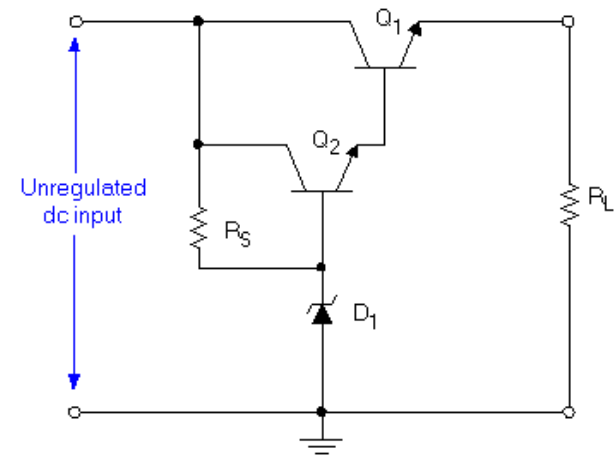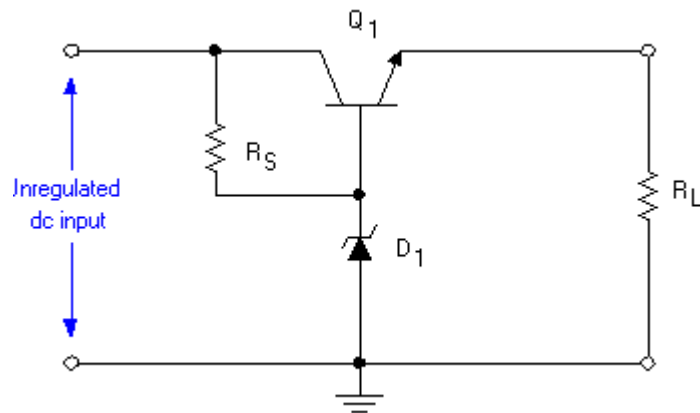

Discrete Linear Regulator

