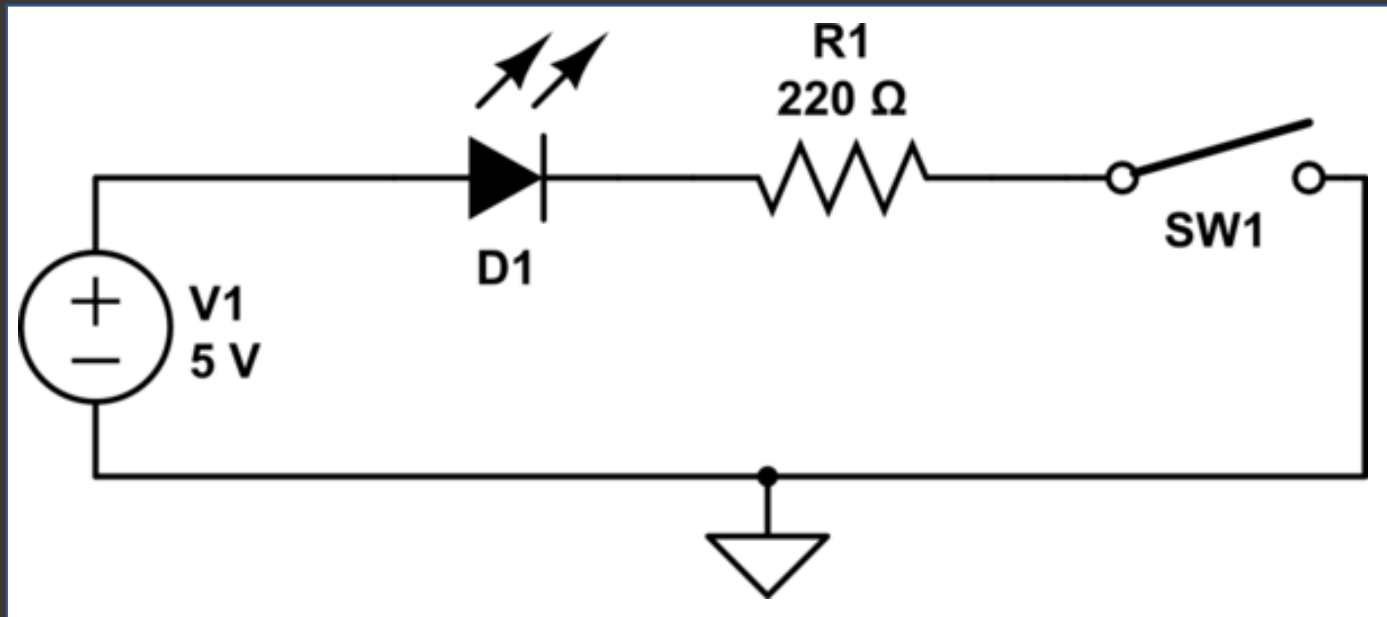


Sept-2019




What's a Schematic?

A diagram showing electrical components and their connections




Drawn from logical/signal flow point of view


LM386 Minimal Amplifier

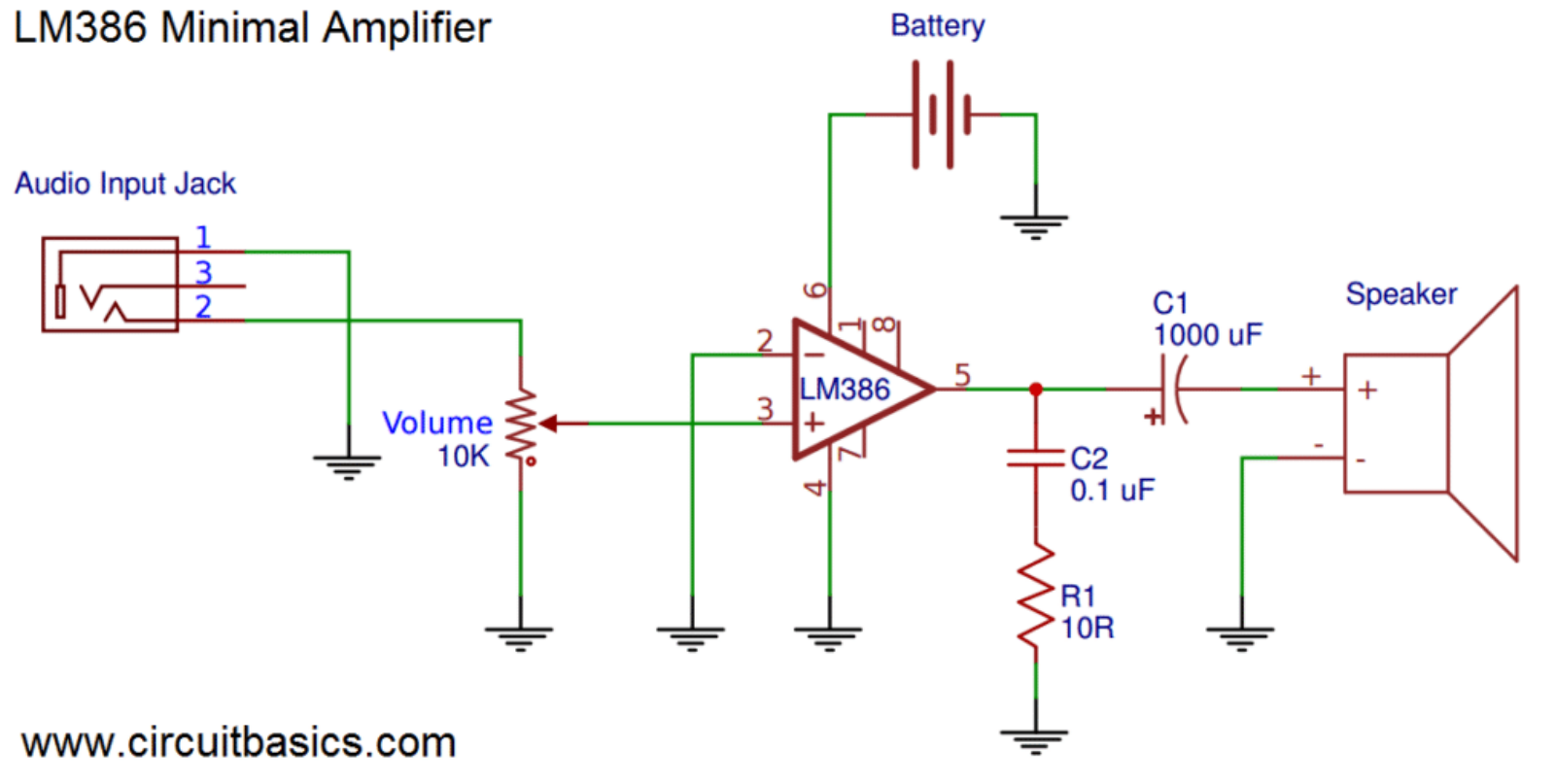

Power Supply

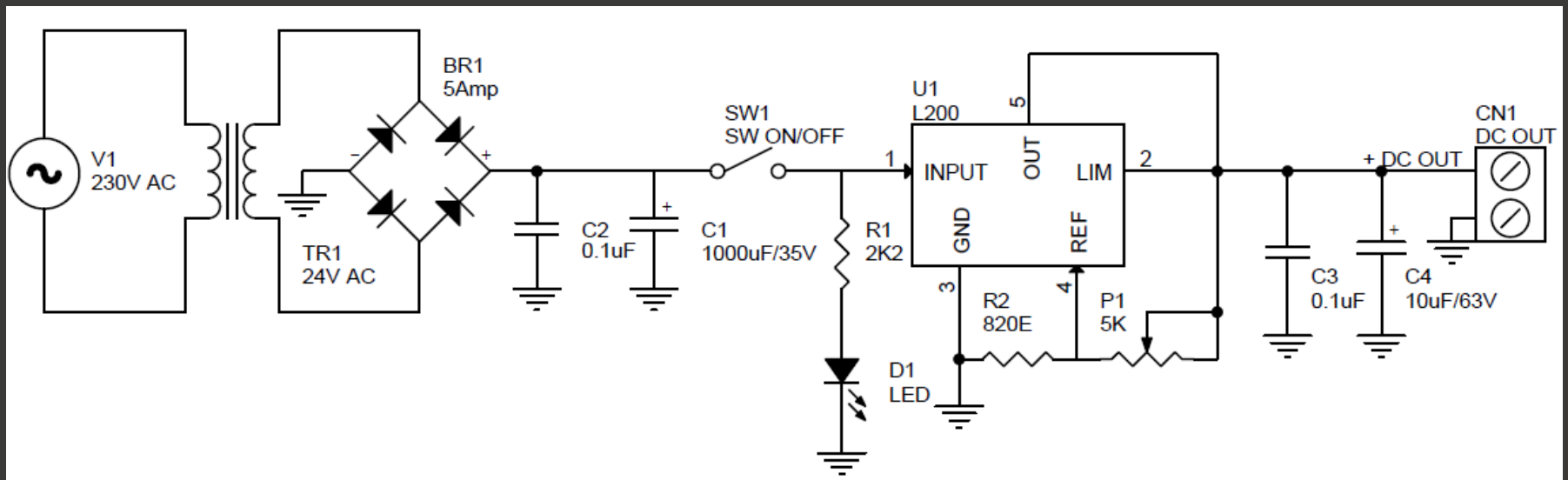


Schematic Usually has a BOM

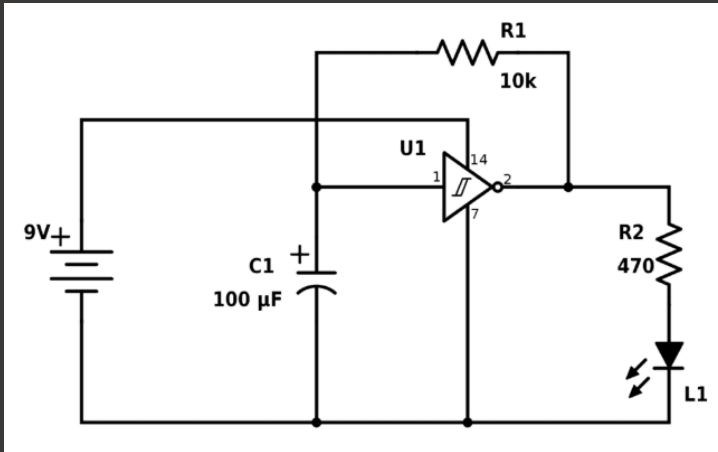

Part	Value	Note
-	-	Breadboard
U1	74C14	Hex Schmitt Trigger Inverter
C1	100μF	Polarized capacitor
R1	10 kΩ	Standard Resistor
R2	470 Ω	Standard Resistor
LED	-	Standard output light-emitting diode



Typical Schematic/BOM Issues

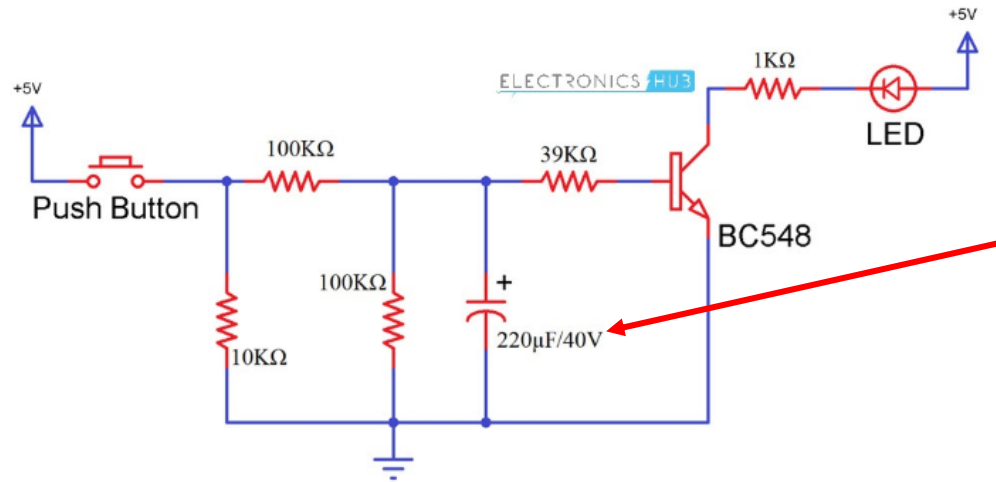

Components Required

- Capacitor – 220μF
- Resistors
 - 2 X 100KΩ
 - 10KΩ
 - 39KΩ
 - 100Ω
- BC 548 (any NPN Transistor)
- LED
- ON/OFF switch (Push Button)
- Mini Breadboard
- 5V Power Supply
- Connecting Wires

40V? 6V would be fine

Resistor power rating?

What kind of LED?


What kind of switch?

Power supply current?


Wall wart?

Lab supply?

Practicality of Breadboarding

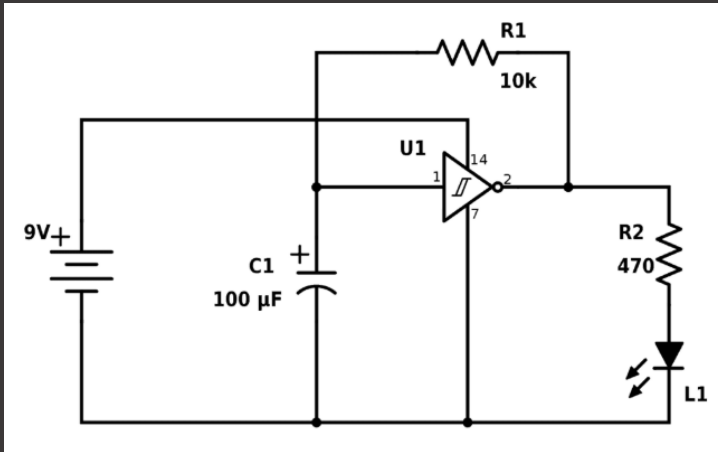


Part	Value	Note
-	-	Breadboard
U1	74C14	Hex Schmitt Trigger Inverter
C1	100μF	Polarized capacitor
R1	10 kΩ	Standard Resistor
R2	470 Ω	Standard Resistor
LED	-	Standard output light-emitting diode

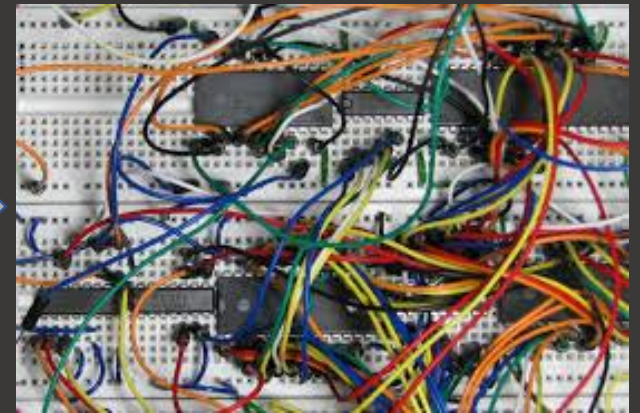

Resistors

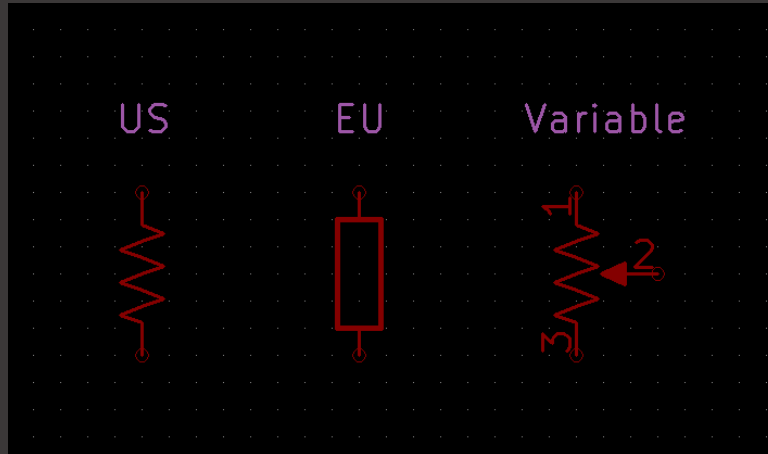If not otherwise specified,
 $\geq 1/8W$ of these work



Fixed Value




RESISTOR COLOUR CODES

	1st Digit	2nd Digit	Multiplier	Tolerance
Black	0	0	$\times 1$	Silver $\pm 10\%$
Brown	1	1	$\times 10$	Gold $\pm 5\%$
Red	2	2	$\times 100$	
Orange	3	3	$\times 1000$	
Yellow	4	4	$\times 10000$	
Green	5	5	$\times 100000$	
Blue	6	6	$\times 1000000$	
Violet	7	7		
Grey	8	8		
White	9	9		


Example Shown :
 Yellow Violet Red Gold
 4 7 $\times 100$ $\pm 5\%$
 47k $\Omega \pm 5\%$

© Byjus.com

Variable/Potentiometer


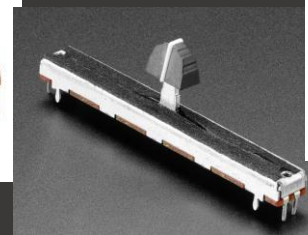


Capacitors

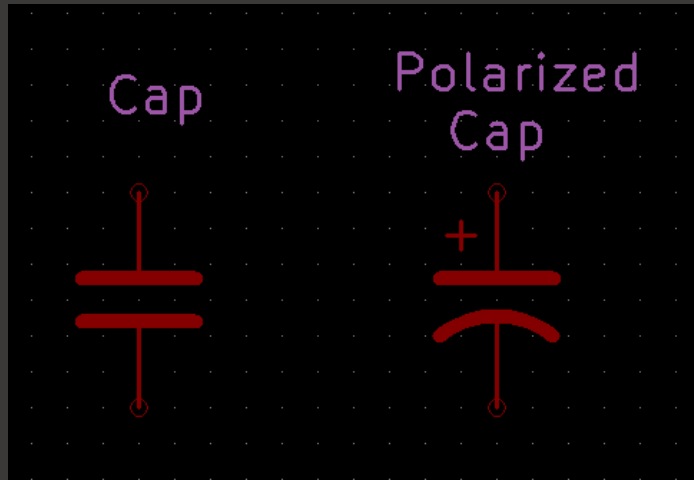


Polarity:

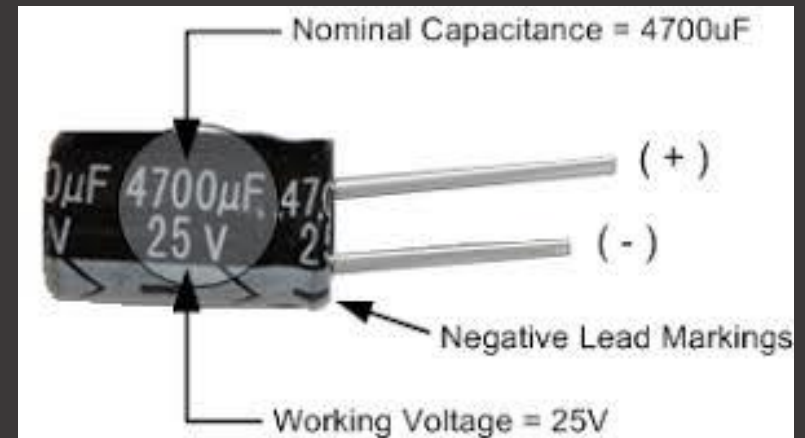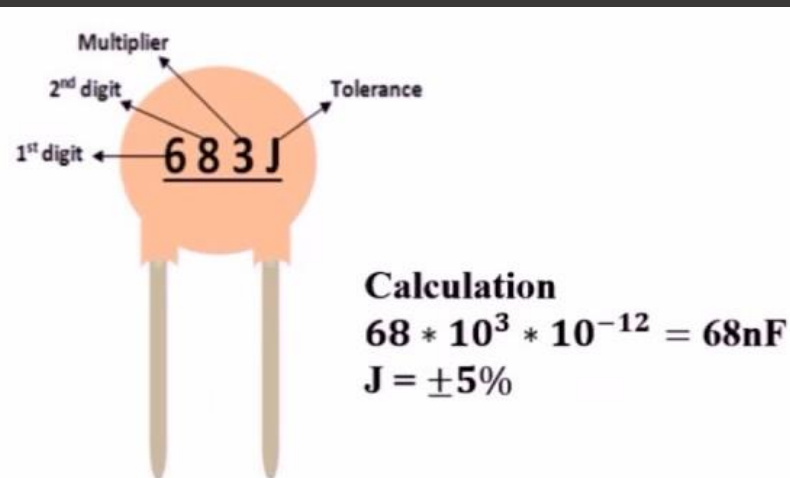- Stripe
- Lead Length (short is negative)
- Other marking




Diodes (Always Polarized)

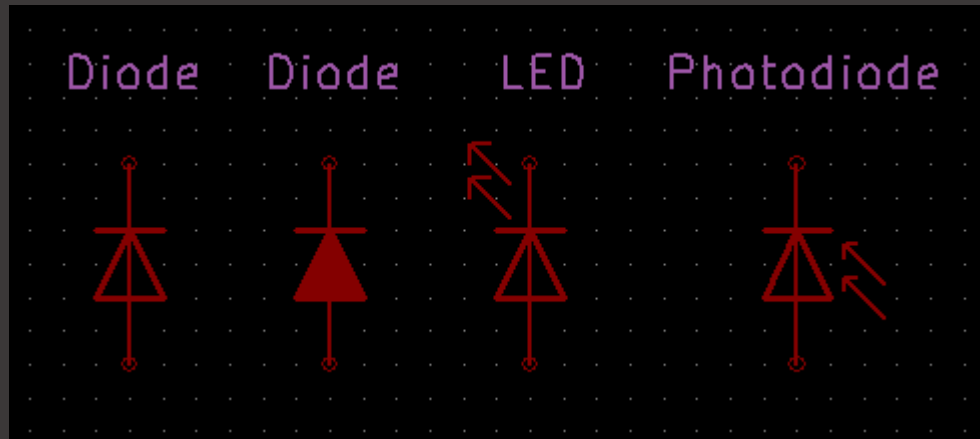


Polarity:


- Band
- Lead Length
- Flat Edge

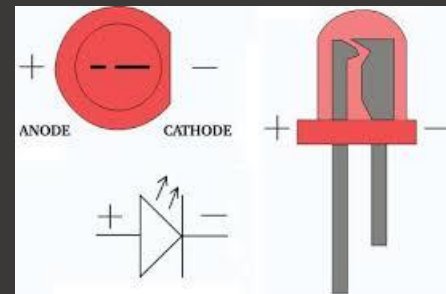


ICs (Always Polarized)

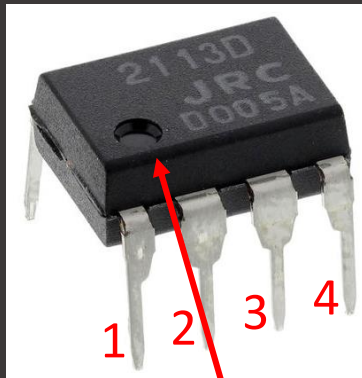

Dot or
Round Depression

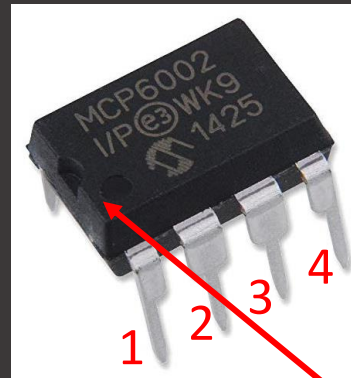


Semicircle
Depression



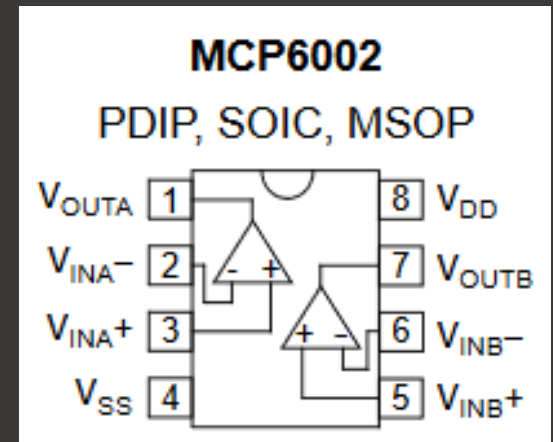


Other Common Schematic Symbols

Grounds (Used Imprecisely)

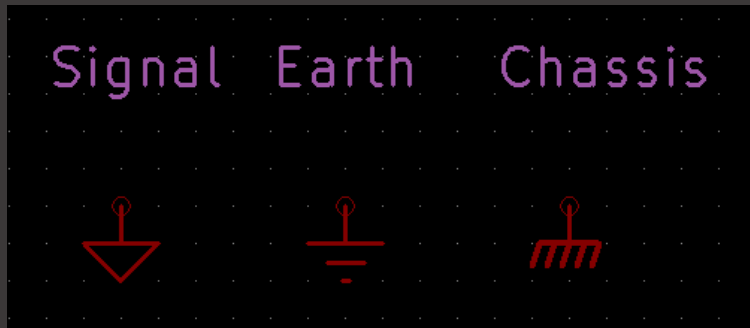




Sources (Used Imprecisely)

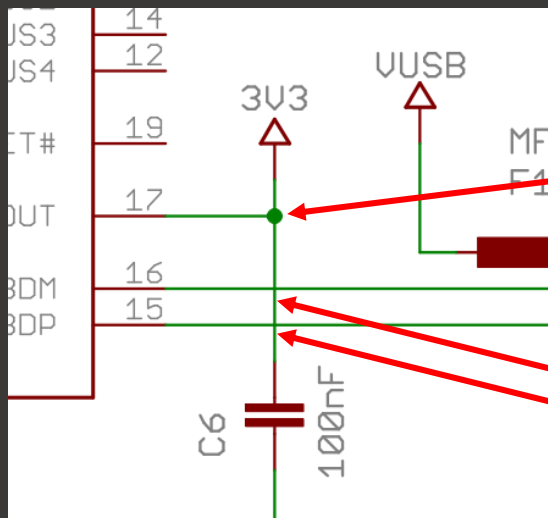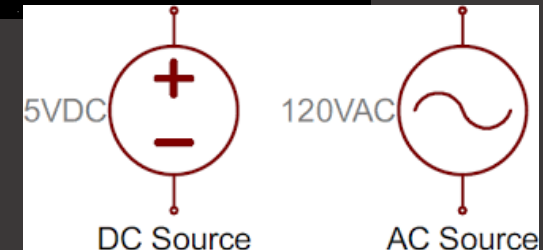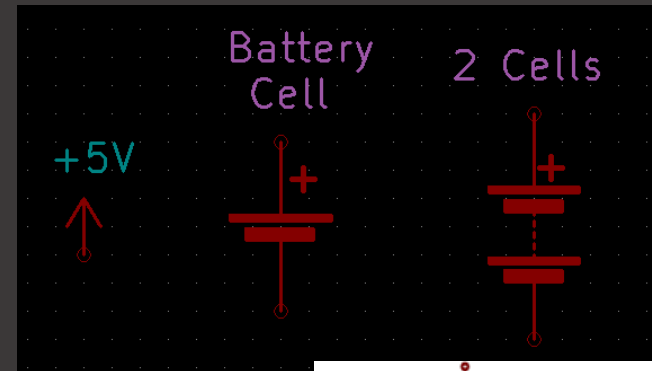




Connected

Not Connected

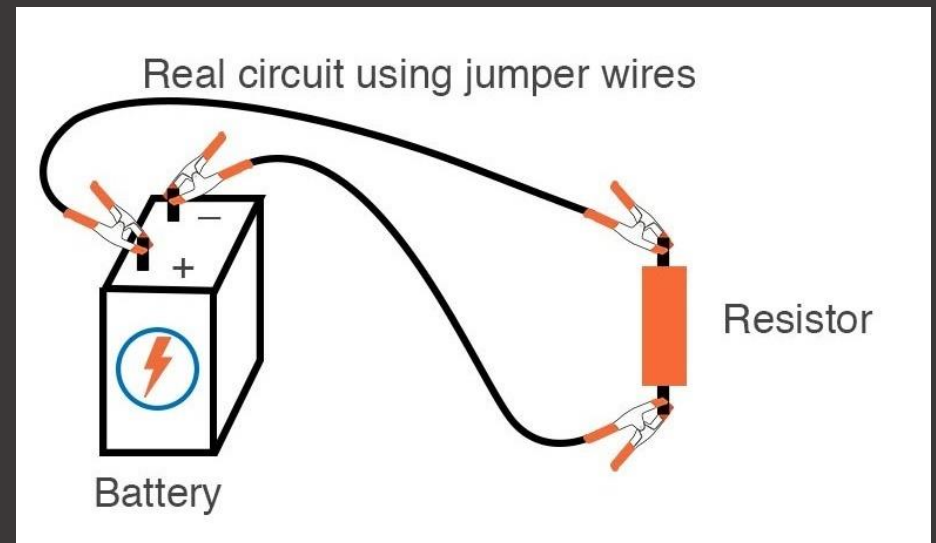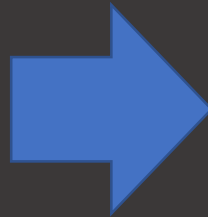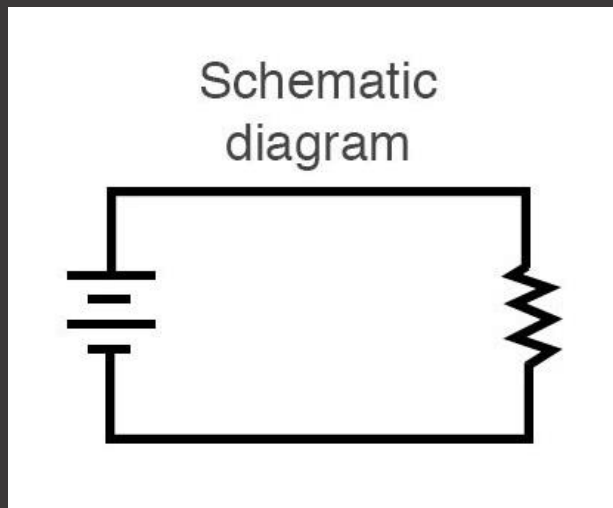
What's a Schematic ISN'T: Physical Implementation



Prototyping Techniques

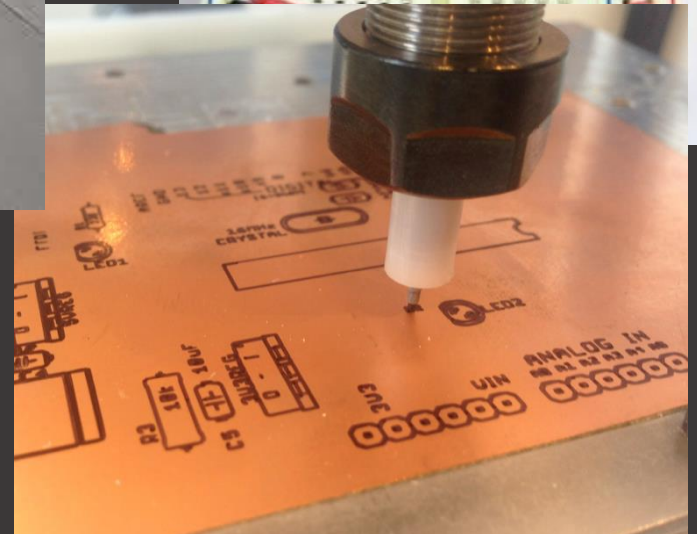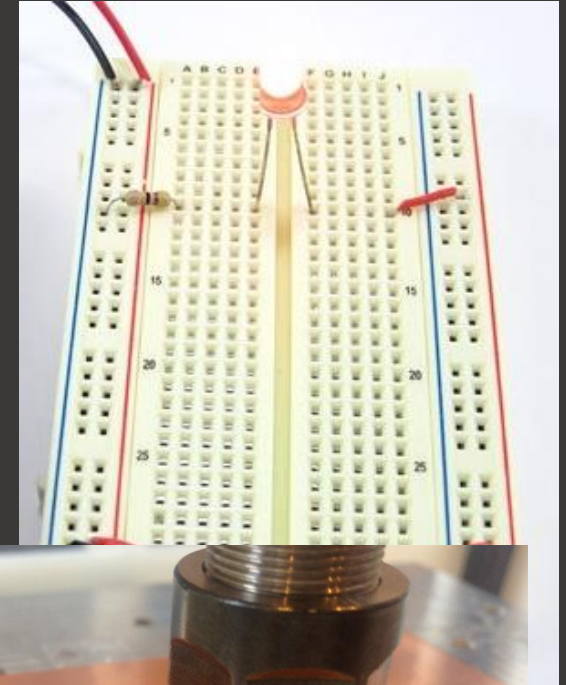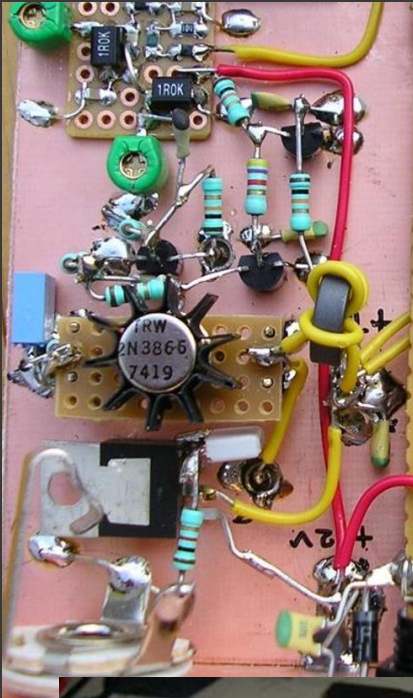

Using a Solderless Breadboard

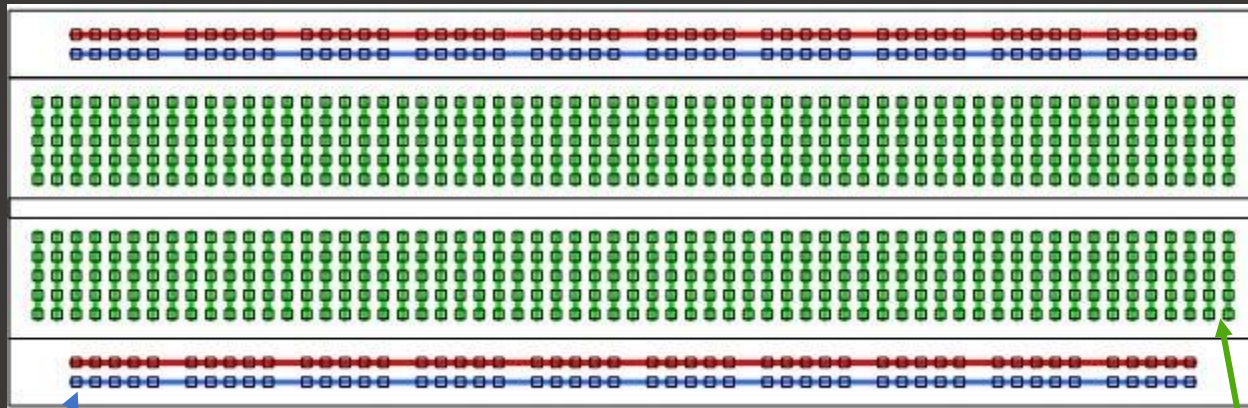


Power Supply Buses


Circuit Connections

Things You Need for Breadboarding


Breadboard

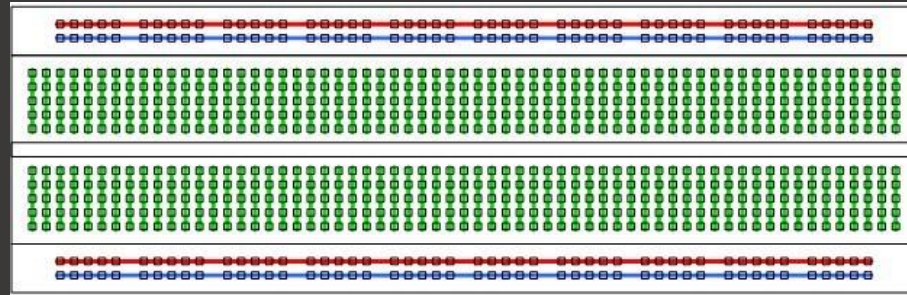



Jumper Wire Kit

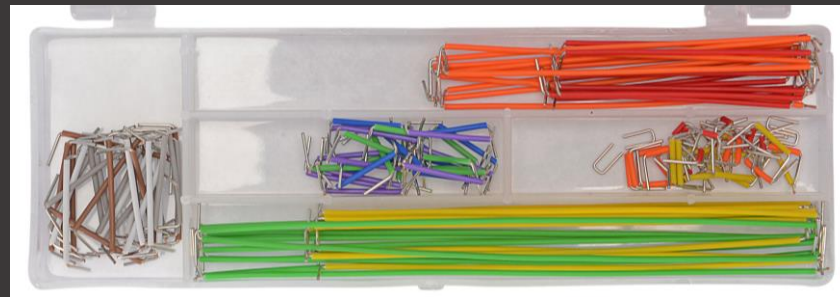



Power supply(ies)

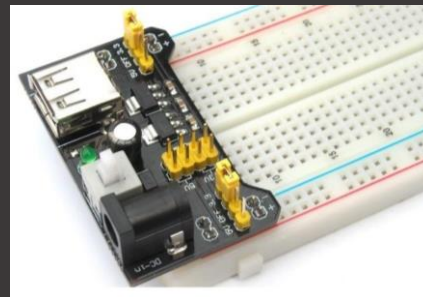


Let's Build a Circuit

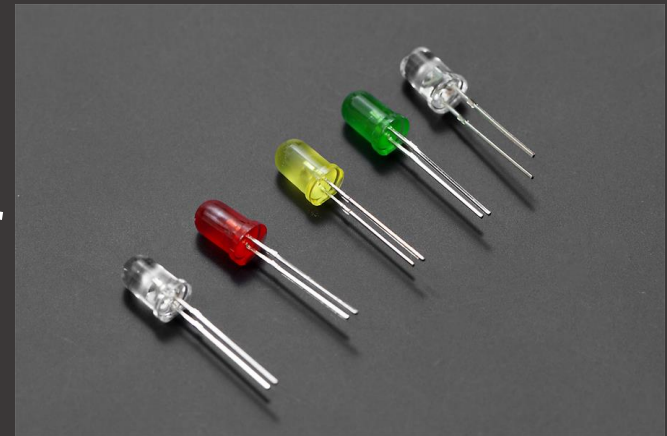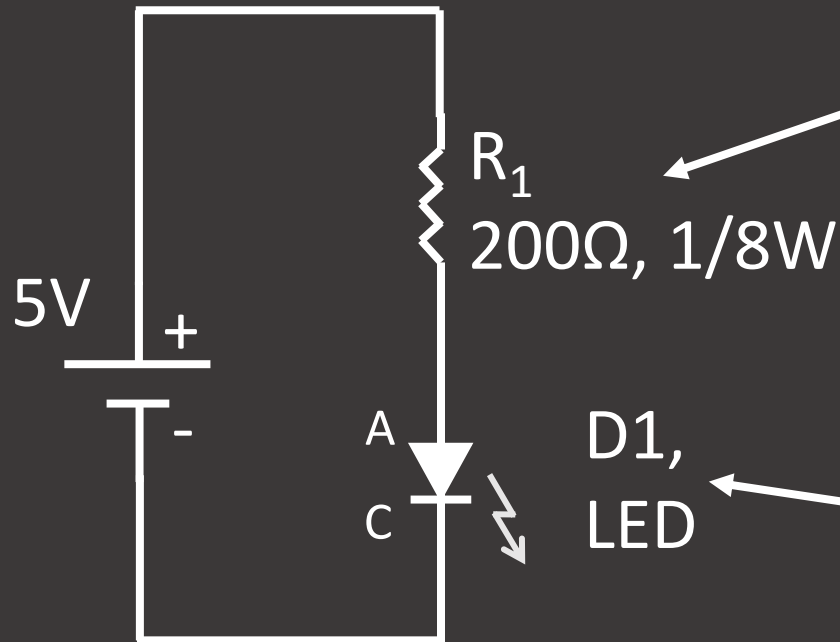

Let's Build a Circuit

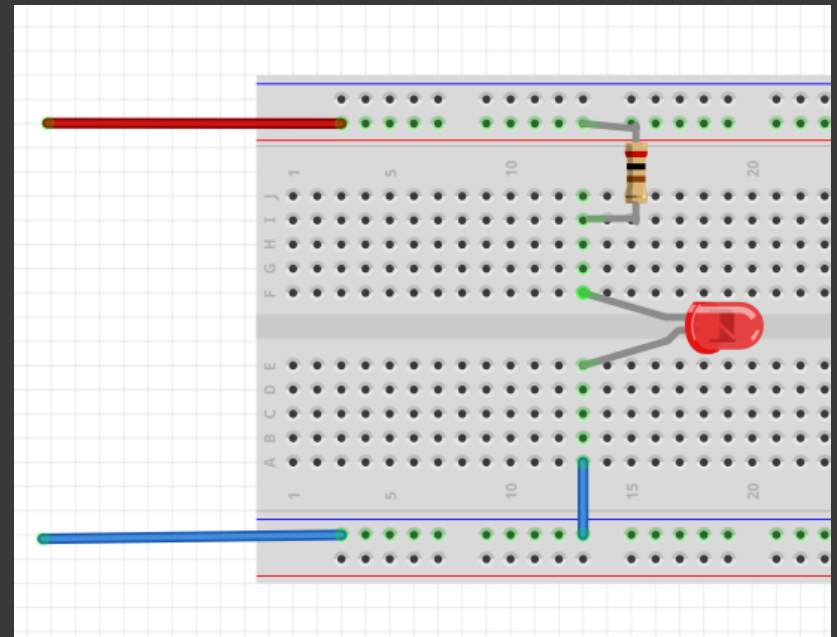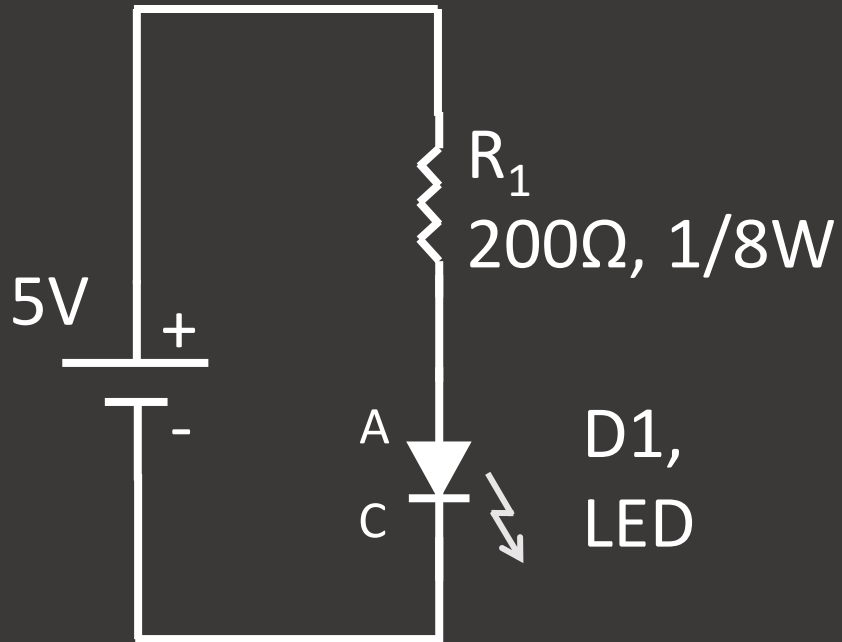

Build an Oscillating Blinker

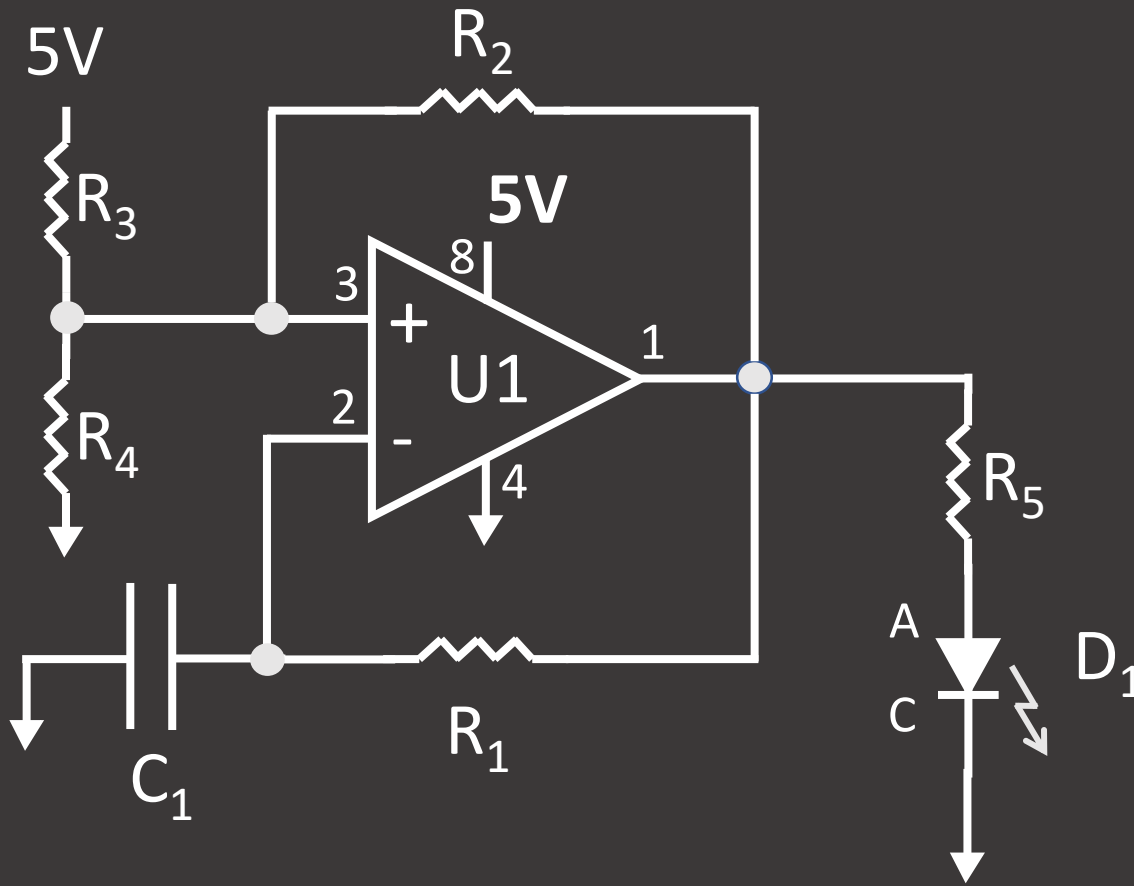

$$C_1 = 1\mu\text{F}$$

$$D_1 = \text{LED}$$

$$R_1 = 120\text{k}\Omega$$

$$R_{2,3,4} = 47\text{k}\Omega$$

$$R_5 = 200\Omega$$

$$U_1 = \text{MCP6002}$$


$$f \approx 1/(2R_1C_1)$$

Set Up Power Supply Rails


10 μ F cap where
supply enters

0.1 μ F capacitors near
integrated circuits

Tie alike colored
supply rails
together

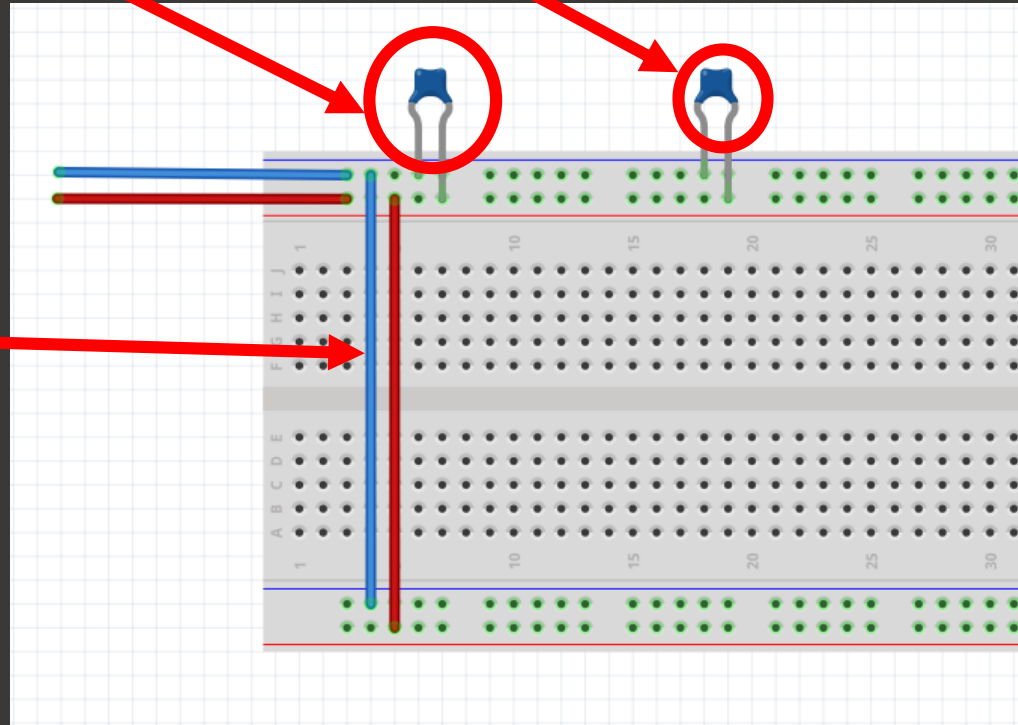

Build an Oscillating Blinker

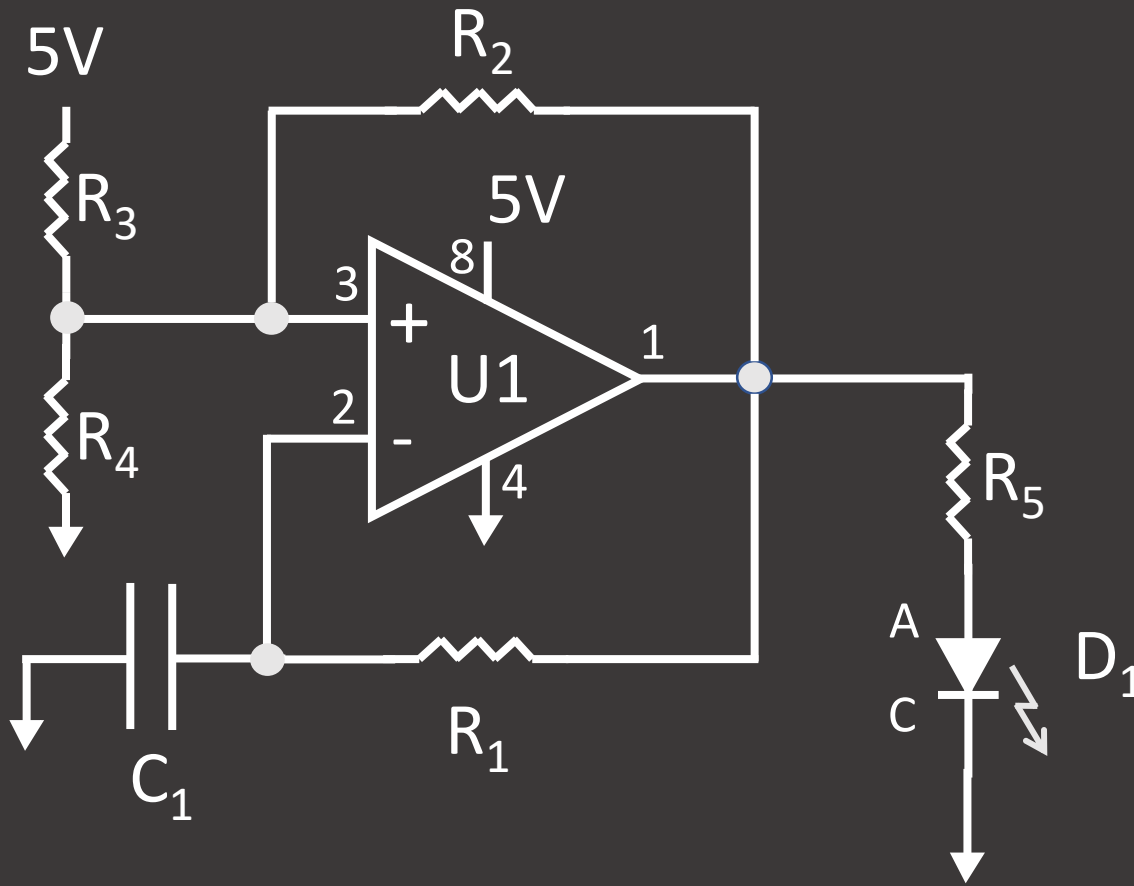

$$C_1 = 1\mu\text{F}$$

$$D_1 = \text{LED}$$

$$R_1 = 120\text{k}\Omega$$


$$R_{2,3,4} = 47\text{k}\Omega$$

$$R_5 = 200\Omega$$

$$U_1 = \text{MCP6002}$$



$$f \approx 1/(2R_1C_1)$$

Build a x3 Amplifier

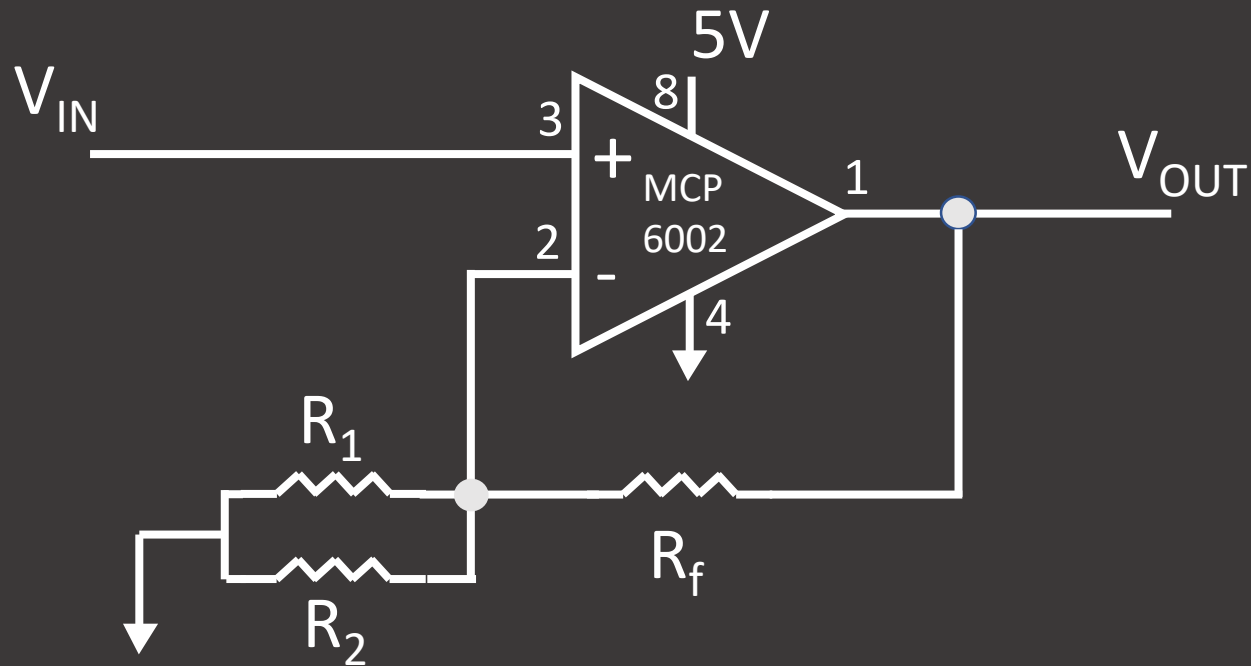

More Hints and Tips

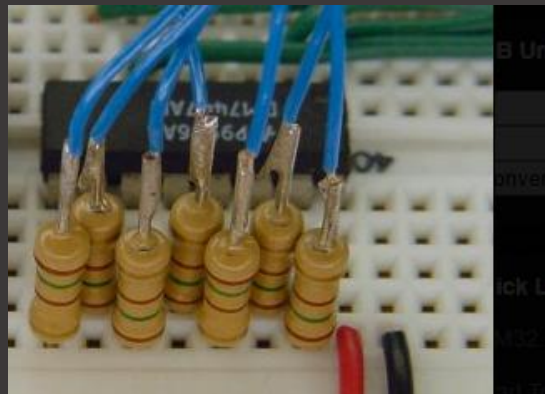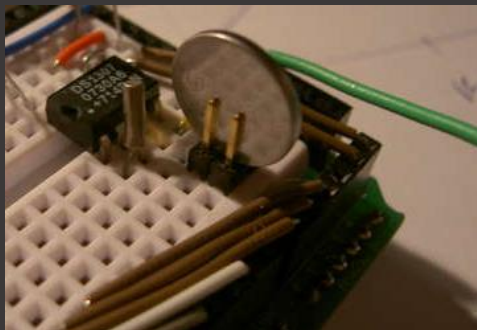- Power Supplies
 - Watch power supply polarity!
 - Connect the two power rails to each other
 - Add a large (10F) bypass where power comes in
 - Add 0.1 μ F bypass to each rail, near supply pins
- Trim component leads so they don't short into each other
- Dupont wires make cheap, long jumpers
- Drop an LED and resistor on the board to use as a logic probe





"That's all Folks!"

l s b e r g[®]